

HW 6– Chapter 7

<1>

7.12 A network is supplied by a 120 V rms, 60-Hz voltage source. An ammeter and a wattmeter indicate that 12 A rms is drawn from the source and 800 W is consumed by the network. Determine:

- The network power factor.
- The network phase angle.
- The network impedance.
- The equivalent resistance and reactance of the network.

<2>

7.13 For the following numeric values, determine the average power, P , the reactive power, Q , and the complex power, S , of the circuit shown in Figure P7.13. *Note:* Phasor quantities are rms.

- $v_S(t) = 650 \cos(377t)$ V
 $i_o(t) = 20 \cos(377t - 10^\circ)$ A
- $\tilde{V}_S = 460 \angle 0^\circ$ V rms
 $\tilde{I}_o = 14.14 \angle -45^\circ$ A rms
- $\tilde{V}_S = 100 \angle 0^\circ$ V rms
 $\tilde{I}_o = 8.6 \angle -86^\circ$ A rms
- $\tilde{V}_S = 208 \angle -30^\circ$ V rms
 $\tilde{I}_o = 2.3 \angle -63^\circ$ A rms

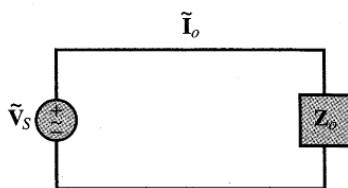


Figure P7.13

Hint) a. is amplitude, b,c,d are in rms value.

7.16 For the circuit shown in Figure P7.16, assume $C = 265 \mu\text{F}$, $L = 25.55 \text{ mH}$, and $R = 10 \Omega$. Find the instantaneous real and reactive power if:

- $v_S(t) = 120 \cos(377t)$ V (i.e., the frequency is 60 Hz)
- $v_S(t) = 650 \cos(314t)$ V (i.e., the frequency is 50 Hz)


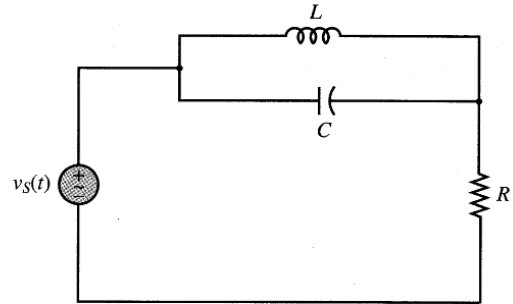


Figure P7.16

<4>

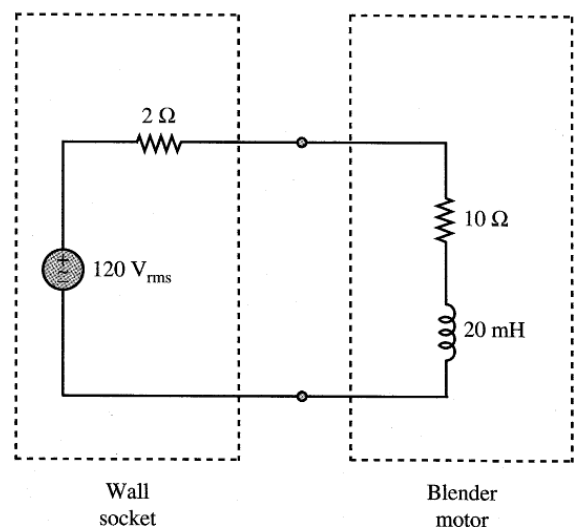7.21 The motor inside a blender can be modeled as a resistance in series with an inductance, as shown in Figure P7.21. The wall socket source is modeled as an ideal 120 V rms voltage source in series with a 2- Ω output resistance. Assume the source frequency is $\omega = 377 \text{ rad/s}$.

- What is the power factor of the motor?
- What is the power factor seen by the voltage source?
- What is the average power, P_{AV} , consumed by the motor?
- What value of capacitor when placed in parallel with the motor will change the power factor seen by the voltage source to 0.9 lagging?



Hint) problem d, find the capacitor value, which makes the pf to be 0.9.

<5>

- 7.26** Find the real and reactive power supplied by the voltage source shown in Figure P7.26 for $\omega = 5$ rad/s and $\omega = 15$ rad/s. Let $v_s = 15 \cos(\omega t)$ V, $R = 5 \Omega$, $C = 0.1$ F, $L_1 = 1$ H, $L_2 = 2$ H.

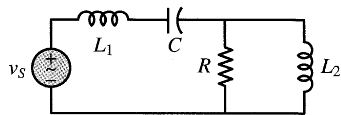


Figure P7.26

<6>

- 7.28** For the circuit shown in Figure P7.28, assume $f = 60$ Hz, $\tilde{V}_s = 90 \angle 0^\circ$ V rms, $R = 25 \Omega$, $X_L = 70 \Omega$, and $X_C = -8 \Omega$. Calculate:
- The capacitance C and the inductance L .
 - The power factor seen by the voltage source.
 - The new capacitance required to correct that power factor to unity.

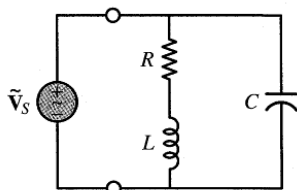


Figure P7.28

<7>

- 7.43** For the circuit shown in Figure P7.43, assume that $\tilde{V}_g = 80 \angle 0^\circ$ V rms, $R_g = 2 \Omega$, and $R_o = 12 \Omega$. Assume an ideal transformer. Find:
- The equivalent resistance seen by the voltage source.
 - The power P_{source} supplied by the voltage source.

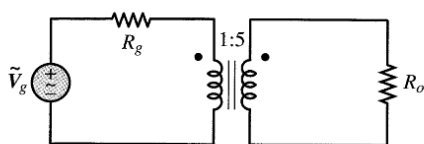


Figure P7.43

<8>

- 7.47** For Figure P7.47, assume the transformer is ideal. Find the step-down turns ratio $M = n$ that provides maximum power transfer to R_o . Let $R_{in} = 1,200 \Omega$, $R_o = 100 \Omega$, and $v_{in}(t) = V_{pk} \cos(\omega t)$.

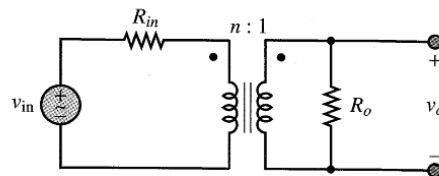


Figure P7.47

<9>

- 7.59** The phase currents in a four-wire wye-connected load, such as that shown in Figure 7.49, are:

$$\tilde{I}_{an} = 22 \angle 0^\circ \text{ A rms} \quad \tilde{I}_{bn} = 10 \angle \frac{2\pi}{3} \text{ A rms} \quad \tilde{I}_{cn} = 15 \angle \frac{\pi}{4} \text{ A rms}$$

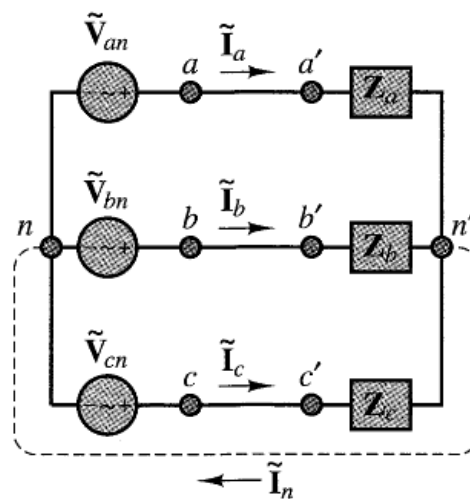


Figure 7.49 Balanced three-phase AC circuit (redrawn)

- 7.61** For the three-phase network shown in Figure P7.61, find the current in each wire and the real power consumed by the wye network. Let $\tilde{V}_R = 110\angle 0^\circ$ V rms, $\tilde{V}_W = 110\angle 2\pi/3$ V rms, and $\tilde{V}_B = 110\angle 4\pi/3$ V rms. $R = 50\ \Omega$, $L = 120$ mH, $C = 133\ \mu\text{F}$, $f = 60$ Hz.

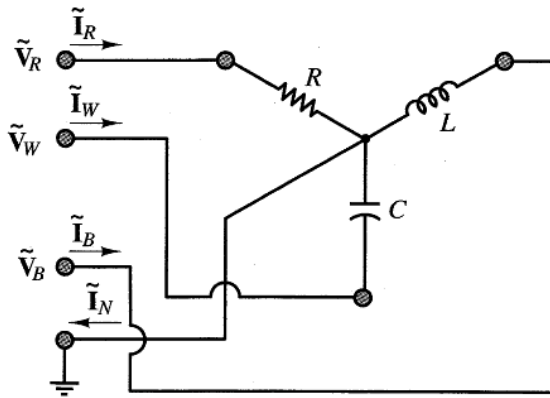


Figure P7.61