

## Electrical Engineering

### HW 5 – Chapter 6, Solution

<1>

$$\frac{v_{out}}{v_{in}}(j\omega) = \frac{R_2 \parallel R_3 + j\omega L + \frac{1}{j\omega(C_1 + C_2)}}{R_1 + R_2 \parallel R_3 + j\omega L + \frac{1}{j\omega(C_1 + C_2)}} = \frac{1 - 0.0008\omega^2 + j(0.05)\omega}{1 - 0.0008\omega^2 + j(0.11)\omega}$$


a)

$$\left| \frac{v_{out}}{v_{in}}(j\omega) \right| = \frac{\sqrt{(1 - \omega^2 0.0008)^2 + ((0.05)\omega)^2}}{\sqrt{(1 - \omega^2 0.0008)^2 + ((0.11)\omega)^2}}$$


$$\angle \frac{v_{out}}{v_{in}}(j\omega) = \arctan\left(\frac{(0.05)\omega}{1 - \omega^2 0.0008}\right) - \arctan\left(\frac{(0.11)\omega}{1 - \omega^2 0.0008}\right)$$

The plots obtained using Matlab are shown below:


b)

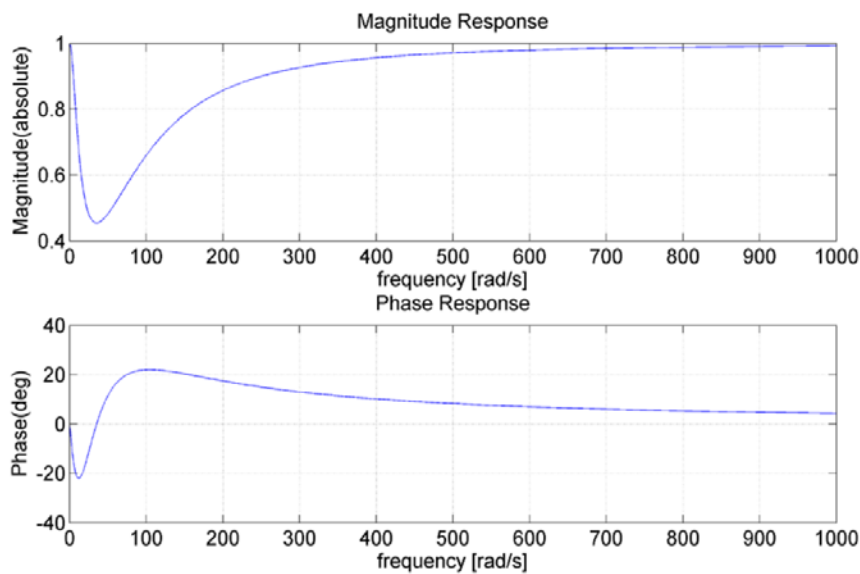

c)

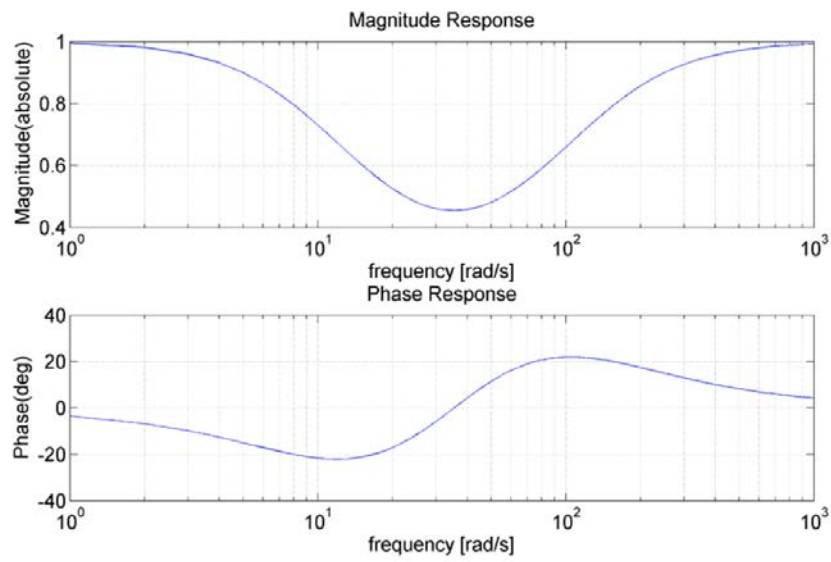

d)

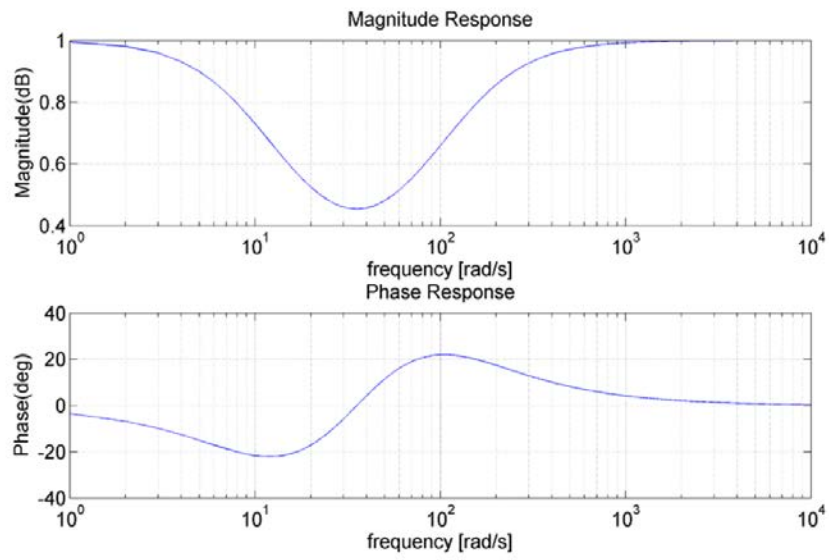

<2>

**Assume:**

The values of the resistors and of the capacitor in the circuit of Figure P6.12:

$$R_1 = 16 \, \Omega \quad R_2 = 16 \, \Omega \quad C = 0.47 \, \mu\text{F}$$


**Analysis:**

a)

$$VD: \quad V_o = V_i \frac{Z_{R2}}{Z_{R1} + Z_C + Z_{R2}} = V_i \frac{R_2}{R_1 + \frac{1}{j\omega C} + R_2}$$

$$H_v[j\omega] = \frac{V_o[j\omega]}{V_i[j\omega]} = \frac{R_2}{R_1 + R_2} \frac{1}{1 - j \frac{1}{\omega C [R_1 + R_2]}}$$

b)

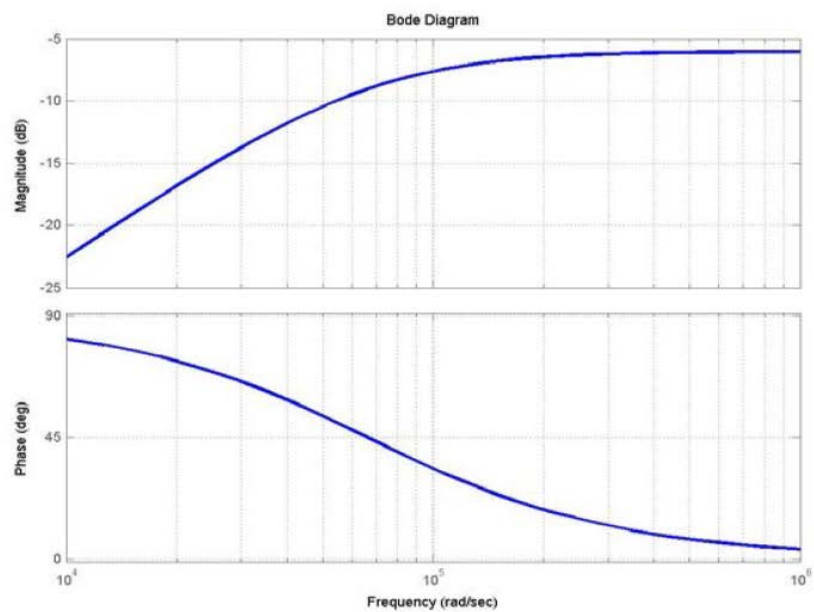


### <3>

Using voltage division:

$$Z_{eq} = \frac{Z_{R2} Z_C}{Z_{R2} + Z_C} = \frac{R_2 \frac{1}{j\omega C}}{R_2 + \frac{1}{j\omega C}} \frac{j\omega C}{j\omega C} = \frac{R_2}{1 + j\omega R_2 C}$$

$$\begin{aligned} VD: H_v[j\omega] &= \frac{V_o[j\omega]}{V_i[j\omega]} = \frac{Z_{RL}}{Z_{R1} + Z_{eq} + Z_{RL}} = \frac{R_L}{R_1 + \frac{R_2}{1 + j\omega R_2 C} + R_L} \frac{1 + j\omega R_2 C}{1 + j\omega R_2 C} = \\ &= \frac{R_L [1 + j\omega R_2 C]}{R_1 + R_2 + R_L + j[R_1 + R_L]\omega R_2 C} = \frac{R_L}{R_1 + R_2 + R_L} \frac{1 + j\omega R_2 C}{1 + j \frac{[R_1 + R_L]\omega R_2 C}{R_1 + R_2 + R_L}} \end{aligned}$$

Plotting the response in a Bode Plot:

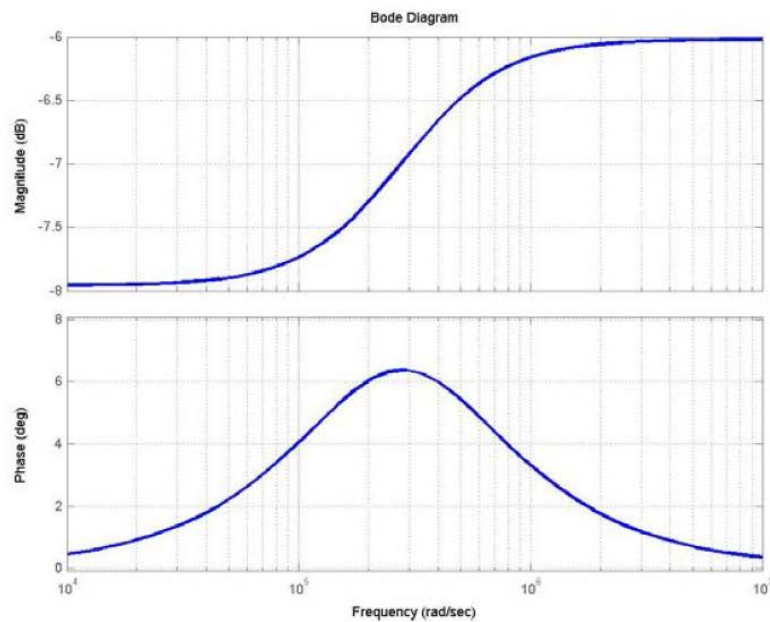

## <4>

The function in Figure P6.20 is an even function. Thus, we only need to compute the  $a_n$  coefficients.

We can compute the Fourier series coefficient using the integrals in equations (6.20) and (6.21):

$$a_0 = \frac{1}{T} \int_0^T x(t) dt = \frac{1}{T} \int_0^{T/2} \sin\left(\frac{2\pi}{T}t\right) dt = \frac{1}{2\pi} \left[ -\cos\left(\frac{2\pi}{T}t\right) \right]_0^{T/2} = \frac{1}{2\pi} [-\cos(\pi) + \cos(0)] = \frac{1}{\pi}$$

$$a_n = \frac{2}{T} \int_0^T x(t) \cos\left(n \frac{2\pi}{T}t\right) dt = \frac{2}{T} \int_0^{T/2} \sin\left(\frac{2\pi}{T}t\right) \cos\left(n \frac{2\pi}{T}t\right) dt = -\frac{\cos(n\pi)+1}{\pi(n^2-1)} = \begin{cases} -\frac{2}{\pi(n^2-1)} & (n \text{ even}) \\ 0 & (n \text{ odd}) \end{cases}$$

Thus, the Fourier series expansion of the function is:

$$x(t) = \frac{1}{\pi} - \sum_{n=1}^{\infty} \frac{\cos(n\pi)+1}{\pi(n^2-1)} \cos\left(n \frac{2\pi}{T}t\right)$$

## <5>

The periodic function shown in Figure P6.21 can be defined

as:

$$x(t) = \begin{cases} A & 0 \leq t \leq \frac{T}{4} \\ -A & T - \frac{T}{4} \leq t \leq T \end{cases}$$

The function in Figure P6.19 is an odd function. Thus, we only need to compute the  $b_n$  coefficients.

We can compute the Fourier series coefficient using the integrals in equation (6.22):


$$b_n = \frac{2}{T} \int_{-T/2}^{T/2} x(t) \sin\left(n \frac{2\pi}{T}t\right) dt = \frac{2}{T} \left( -\int_{-T/4}^0 A \sin\left(n \frac{2\pi}{T}t\right) dt + \int_0^{T/4} A \sin\left(n \frac{2\pi}{T}t\right) dt \right) = \frac{2A}{n\pi} \left( 1 - \cos\left(n \frac{\pi}{2}\right) \right) = \frac{2A}{n\pi}$$

## <6>

Taking the output as the voltage across the parallel R-C subcircuit,

$$\frac{V_o}{V_s} = \frac{1/LC}{(j\omega)^2 + j\omega \frac{1}{RC} + \frac{1}{LC}} = \frac{3/64}{(j\omega)^2 + j\omega 2 + 3/64} \left( = \frac{\omega_n^2 \mu}{(j\omega)^2 + j\omega(2\xi\omega_n) + \omega_n^2} \right)$$

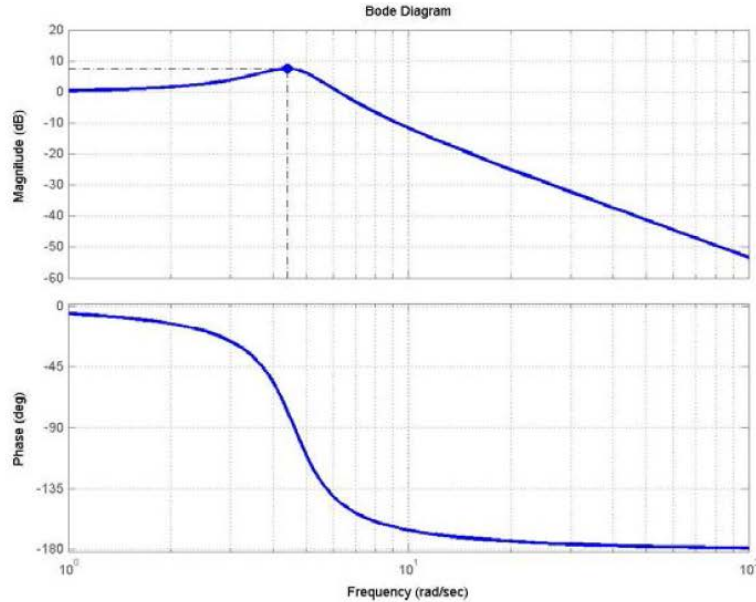The corresponding Bode diagrams are shown below:



In this circuit, as frequency increases, the impedance of the capacitor decreases and the impedance of the inductor increases. Both effects cause the magnitude of the output voltage to decrease so this is a 2<sup>nd</sup> order low pass filter.

The resonance frequency is,

$$\omega_n = \sqrt{\frac{1}{LC}} = \sqrt{\frac{64}{3}} \cong 4.6188 \text{ rad/s.}$$

The damping ratio is,

$$\zeta = \frac{1/RC}{2\omega_n} = \frac{\sqrt{3}}{8} \cong 0.2165$$

The quality factor is,

$$Q = \frac{1}{2\zeta} = \frac{4}{\sqrt{3}} \cong 2.3094$$

The bandwidth is,

$$B = \frac{\omega_n}{Q} = \frac{8}{\sqrt{3}} \frac{1}{4/\sqrt{3}} = 2 \text{ rad/s.}$$

## <7>

a)

As  $\omega \rightarrow 0 : Z_L \rightarrow 0 \Rightarrow \text{Short}$

$Z_C \rightarrow \infty \Rightarrow \text{Open}$

$\Rightarrow H_v \rightarrow 0$

As  $\omega \rightarrow \infty : Z_L \rightarrow \infty \Rightarrow \text{Open}$

$Z_C \rightarrow 0 \Rightarrow \text{Short}$

$\Rightarrow H_v = \frac{V_o}{V_i} \rightarrow \frac{R_2}{R_1 + R_2}$

The filter is a high pass filter.

b) First, we find the Thévenin equivalent circuit seen by the capacitor:

$$Z_T = (Z_{R1} + Z_C) \parallel (Z_{R2} \parallel Z_L)$$

and


$$V_{OC} = \frac{Z_{R2}}{Z_{R1} + Z_C + Z_{R2}} V_{in}$$

$$\frac{V_{out}}{V_{OC}} = \frac{Z_C}{Z_T + Z_L}$$

Therefore,

$$\frac{V_{out}}{V_{in}} = \frac{R_2}{R_1 + \frac{1}{j\omega C} + R_2} \cdot \frac{Z_L}{Z_T + Z_L}$$

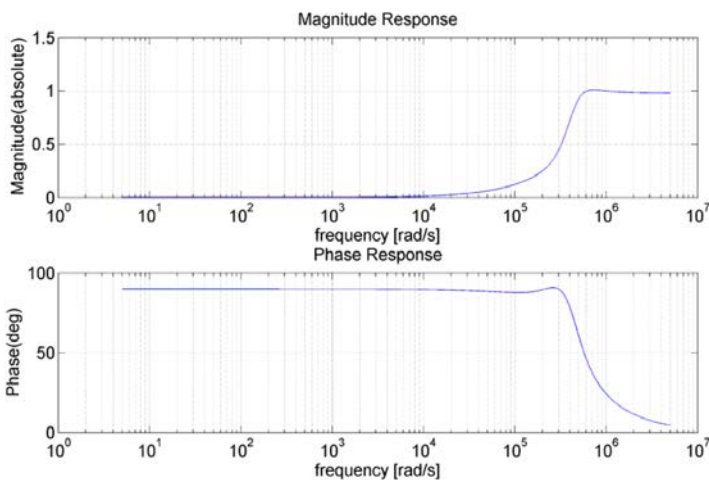Substituting the numerical values, the corresponding Bode diagrams are shown in the Figure.



<8>

(a)

$$Z_{eq} = \frac{1}{\frac{1}{Z_C} + \frac{1}{Z_L} + \frac{1}{Z_{R_L}}} = \frac{1}{j\omega C + \frac{1}{j\omega L} + \frac{1}{R_L}} = \frac{j\omega L R_L}{(j\omega)^2 L C R_L + j\omega L + R_L}$$

$$VD: H_V(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{Z_{eq}}{Z_{R_S} + Z_{eq}} = \frac{\frac{j\omega L R_L}{(j\omega)^2 L C R_L + j\omega L + R_L}}{R_S + \frac{j\omega L R_L}{(j\omega)^2 L C R_L + j\omega L + R_L}}$$

$$H_V(j\omega) = \frac{j\omega L R_L}{(j\omega)^2 L C R_S R_L + j\omega L (R_L + R_S) + R_S R_L} = \frac{1}{R_S} \frac{j\omega L}{(j\omega)^2 L C + j\omega L \left( \frac{R_L + R_S}{R_S R_L} \right) + 1}$$

b) The resonance frequency is  $\omega_n = \sqrt{\frac{1}{LC}} \cong 1.4142 \text{ Mrad/s}$ .

c) Half power frequencies (see the following d) for  $\zeta$ :

$$\omega_{1,2} = \omega_n \sqrt{1 + \zeta^2} \pm \zeta \omega_n = 1.4142 \cdot 10^6 \sqrt{1 + (0.1485)^2} \pm (0.1485) \cdot 1.4142 \cdot 10^6 = (1.4297 \pm 0.21) \cdot 10^6 \text{ rad/sec}$$

$$\text{So } \omega_2 = 1.2197 \cdot 10^6 \text{ rad/sec; } \omega_1 = 1.6397 \cdot 10^6 \text{ rad/sec;}$$

d) The damping ratio is  $\zeta = \frac{\omega_n}{2} L \left( \frac{R_L + R_S}{R_S R_L} \right) \cong 0.1485$ . The quality factor is  $Q = \frac{1}{2\zeta} \cong 3.3672$ . The bandwidth is,

$$B = \frac{\omega_n}{Q} \cong 420 \text{ Krad/s.}$$



<9>

**Analysis:**

$$\frac{V_{out}(j\omega)}{V_s(j\omega)} = \frac{R_L \parallel Z_{ab}}{R_L \parallel Z_{ab} + R_S}$$

$$Z_{ab} = \frac{(j\omega L) \left( \frac{1}{j\omega C} \right)}{j\omega L + \frac{1}{j\omega C}} = \frac{j\omega L}{1 - LC\omega^2}$$
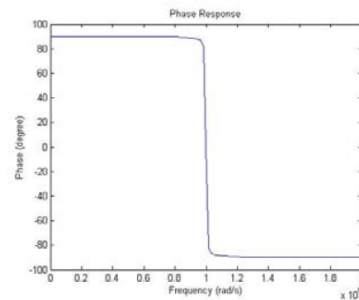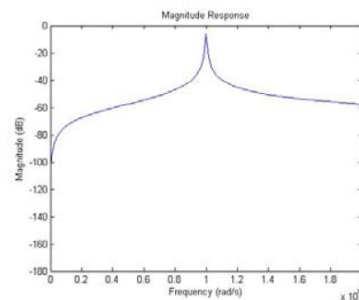
$$R_L \parallel Z_{ab} = \frac{j\omega L R_L}{R_L - \omega^2 L C R_L + j\omega L} = \frac{j\omega L}{1 - \omega^2 LC + j\omega L/R_L}$$



$$\frac{V_{out}(j\omega)}{V_s(j\omega)} = \frac{j\omega L/R_S}{j\omega(L/R_S + L/R_L) + 1 - \omega^2 LC} = \frac{j\omega L/R_S}{j\omega(L/R_S + L/R_L) + 1 - \omega^2 LC}$$



## <10>

$$(a) \quad \frac{V_O(s)}{V_S(s)} = \frac{\frac{1}{C_2 s} \parallel R_L}{\frac{1}{C_2 s} \parallel R_L + sL + R_S \parallel \frac{1}{C_1 s}} \quad v_s(t)$$

$$\text{We have} \quad \frac{1}{C_2 s} \parallel R_L = \frac{R_L}{R_L C_2 s + 1}$$

Therefore,

$$\frac{V_O(s)}{V_S(s)} = \frac{\frac{R_L}{R_L C_2 s + 1}}{\frac{R_L}{R_L C_2 s + 1} + sL + \frac{R_S}{R_S C_1 s + 1}} = \frac{R_S C_1 s + 1}{s^3 K_1 + s^2 K_2 + s K_3 + K_4}$$

where

$$K_1 = C_2 R_S C_1 L$$

$$K_2 = C_2 L + C_1 L \frac{R_S}{R_L}$$

$$K_3 = R_S C_1 + R_S C_2 + \frac{L}{R_L}$$

$$K_4 = 1 + \frac{R_S}{R_L}$$

$$\frac{V_O(\omega)}{V_S(\omega)} = \frac{\frac{j\omega}{2000\pi} + 1}{\frac{-j\omega^3}{(2000\pi)^3} - \frac{2\omega^2}{(2000\pi)^2} + \frac{3j\omega}{2000\pi} + 2}$$

(b)

