

Chapter 4

Implementing ISA (Fetch, Decode, Execute)

Part 1: Single Cycle Design

Big Picture


- ❑ Part 1: what is computer, CSE, computer architecture?
 - Fundamental concepts and principles
- ❑ Part 2: ISA ([externals](#))
 - Ch. 1: performance
 - Exe. time, benchmark, model, RISC, power, multicore
 - Ch. 2: language of computer; ISA
 - What is a good ISA? Today's RISC-style ISA (MIPS)
 - Ch. 3: computer arithmetic
 - Data representation and ALU, ISA – data perspective
- ❑ Part 3: implementation of ISA ([internals](#))
 - Ch. 4: processor
 - Ch. 5: memory system

Big Picture

- ❑ Part 3: implementation of ISA ([internals](#))
 - High-level organization, not circuits design
 - Ch. 4: processor
 - Given ISA, what is a good implementation?
 - Instruction sequencing (fetch-decode-execution)
 - † Datapath and control, pipelining
 - Ch 5: memory system design
 - Cache memory (a part of processor)

Another Engineering Paradigm

 - ❑ Requirement engineering
 - Requirements in processor design?
- ❑ External design interface
 - Go through detailed simulation of internal design
- ❑ Internal design implementation
 - Finalize internal design
- ❑ Verification & validation
- ❑ Maintenance bug fix



iterative

† Iterative and hierarchical

Implementation of ISA

- ❑ Datapath and control (internals, chip design)
 - High-level organization (and low-level circuits design)
 - Affect CPI and clock cycle time pipeline
 - † ISA affect IC (instruction count), CPI, clock
- ❑ Three implementations
 - Single cycle implementation
 - Multi-cycle implementation (optional)
 - Pipelined implementation


The Processor: Datapath & Control

- ❑ We're ready to look at an implementation of the MIPS
- ❑ Simplified to contain only:
 - Memory-reference instructions: **lw, sw**
 - Arithmetic-logical instructions: **add, sub, and, or, slt**
 - Control flow instructions: **beq, j**
- ❑ Generic Implementation: repeat the following
 - Instruction fetch (IF)
 - Get the instruction from memory, $PC \leftarrow PC + 4$
 - Instruction decode (ID)
 - Use the instruction to decide exactly what to do
 - Instruction execute (EX)
 - Do it

Instruction Execution

- ❑ PC \rightarrow instruction memory, **fetch instruction**, PC \leftarrow PC+4
- ❑ **Decode instruction (opcode)**
 - † Register numbers \rightarrow register file, read registers
- ❑ **Execute instruction**: depending on instruction class
 - Use ALU to calculate
 - Arithmetic result
(then store result in register)
 - Memory address for load/store
(load: read data memory, store data in register)
(store: write to data memory)
 - Branch target address (then PC \leftarrow target address)
- † Functional units and their order

CPU Overview: Schematic Diagram

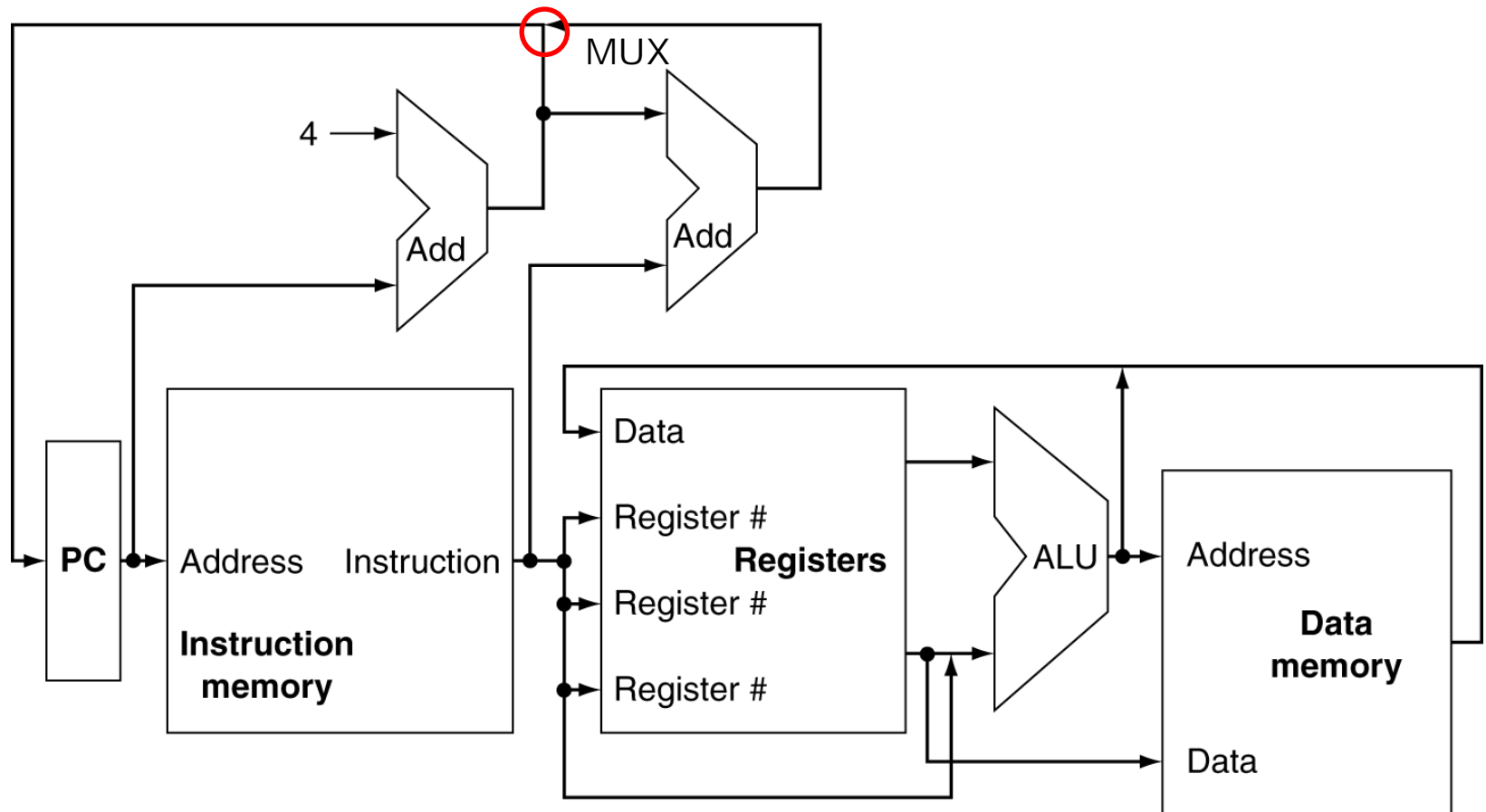

- ❑ Why does this look familiar?
- ❑ ISA determine functional units and their order

How do we execute MIPS instructions?

☐ ALU instructions

add \$t0, \$t1, \$t2 // R-type

addi \$t0, \$t1, 4 // I-type

☐ Data transfer instructions

lw \$t0, 12(\$t1) // I-type

st \$t0, 12(\$t1)

☐ Branch instructions


beq \$t0, \$t1, 8 // I-type

R	op	rs	rt	rd	shamt	funct
I	op	rs	rt	16 bit address		
J	op	26 bit address				

Instruction Decode

- ❑ Where is it in the datapath?
 - Not shown (will come back to it)



Need to Use Multiplexers

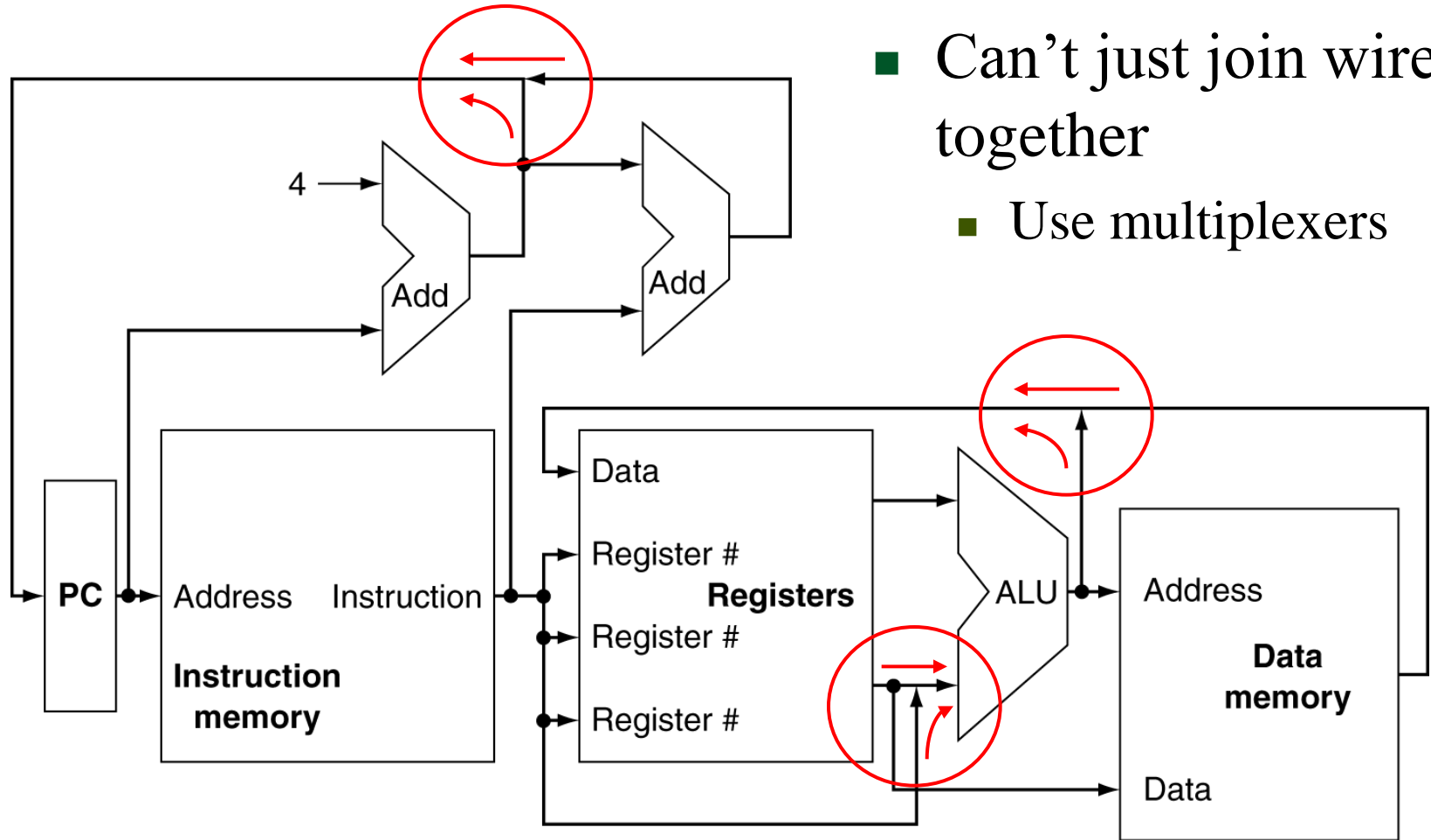

- Can't just join wires together
- Use multiplexers



Multiplexers (반복)

 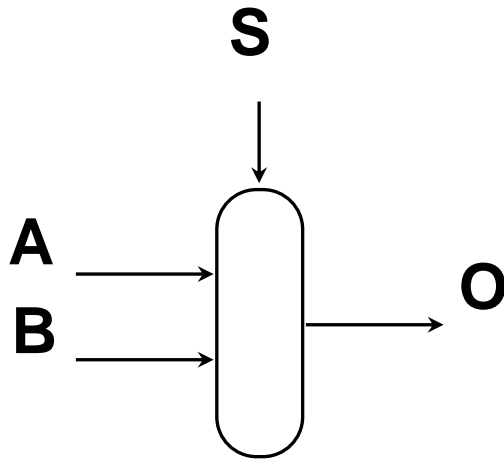- 2-to-1 MUX, 4-to-1 MUX (c.f., Demultiplexer)



Multiplexer Abstraction (반복)

 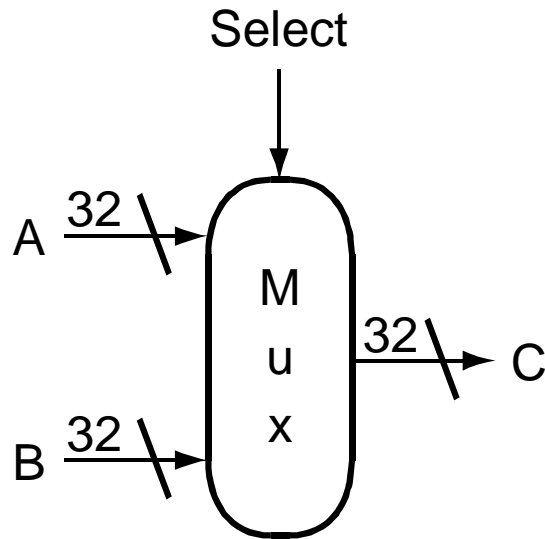
- ❑ Make sure you understand the abstractions!
- ❑ 32 of 2-to-1 mux



Digital Logic Design (반복)

- ❑ Given: AND, OR, NOT
 - ❑ Design
 - Combinational logic circuits
 - Decoder, mux, ..., ALU
 - Sequential logic circuits
 - Latch, flip-flop, register, counter, ..., CPU
 - ❑ Notion of abstraction
 - ❑ VHDL/Verilog simulation (software flavor)
- † How do you define combinational or sequential logic?



Sequential circuits (state diagram) (반복)

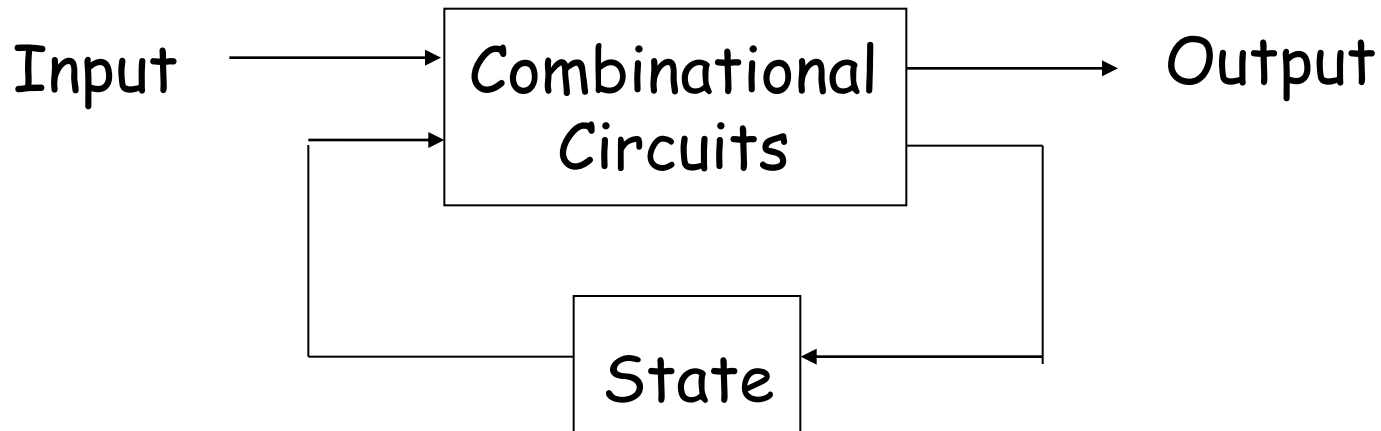

□ Two types of functional units:


- elements that operate on data values (combinational – truth table)
- elements that contain state (sequential – state diagram)

Sequential circuits (반복)

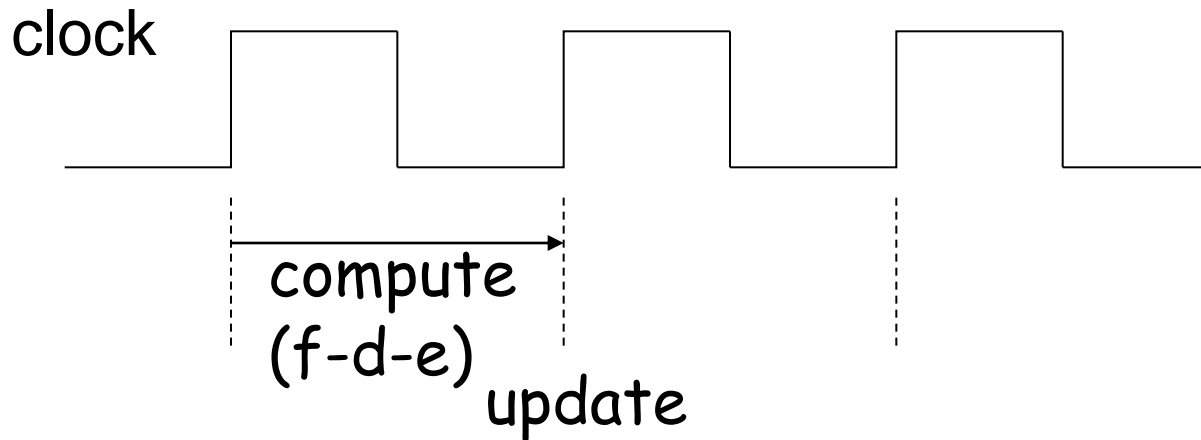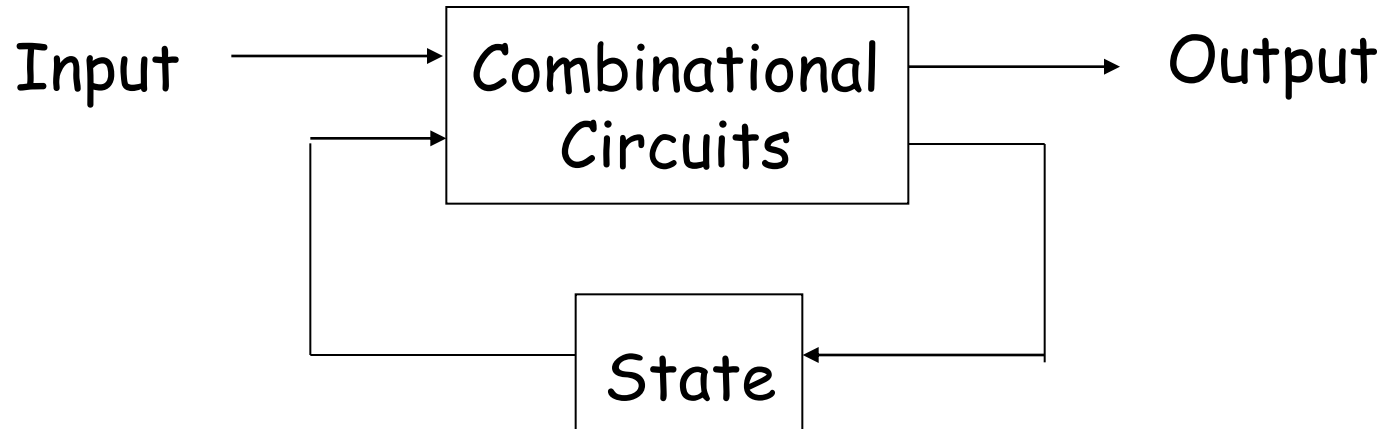

† Synchronous logic circuits

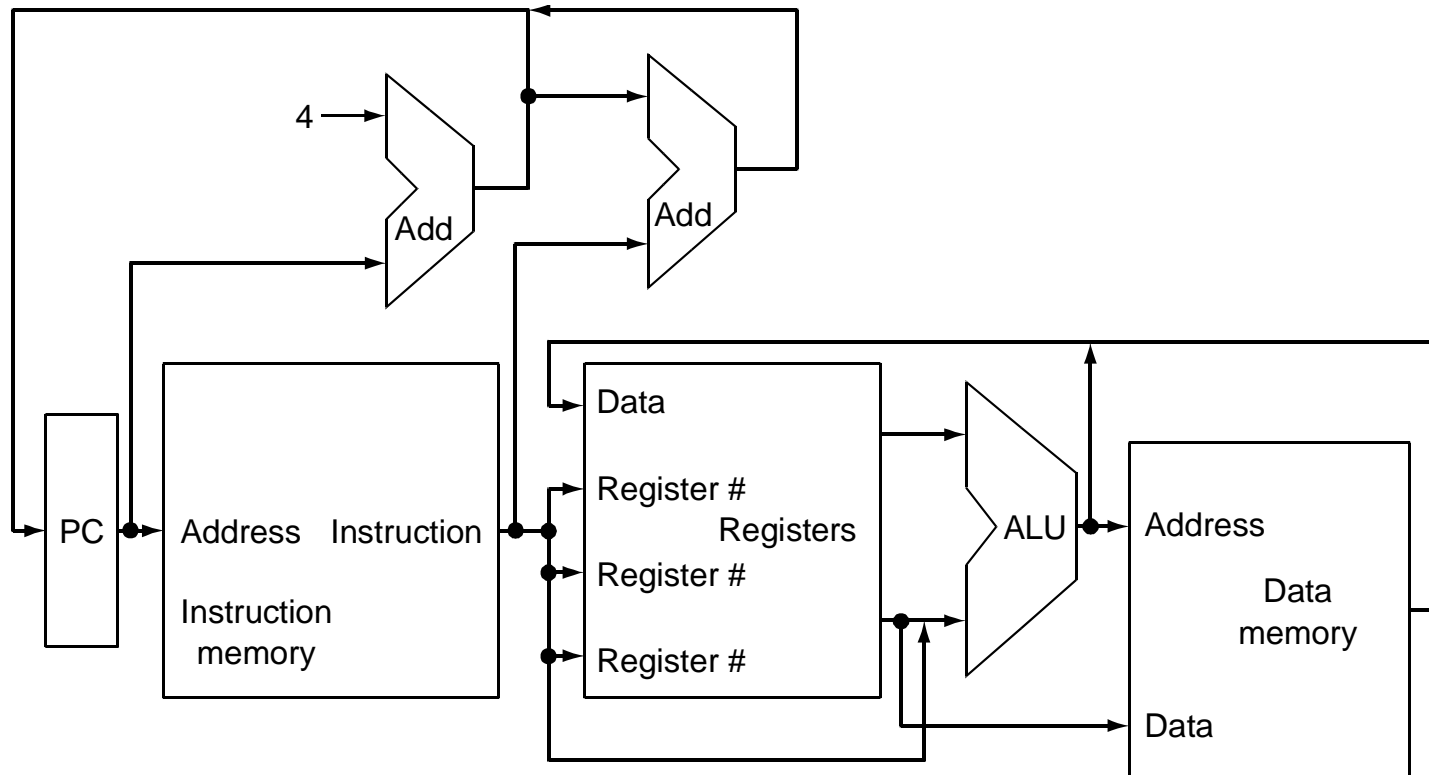CPU: synchronous sequential logic circuits





❑ What are the states?

- Result of “fetch-decode-execute” updated at the end of each clock cycle

How do we provide inputs at high speed?

❑ Pentium at 1GHz

- Light speed

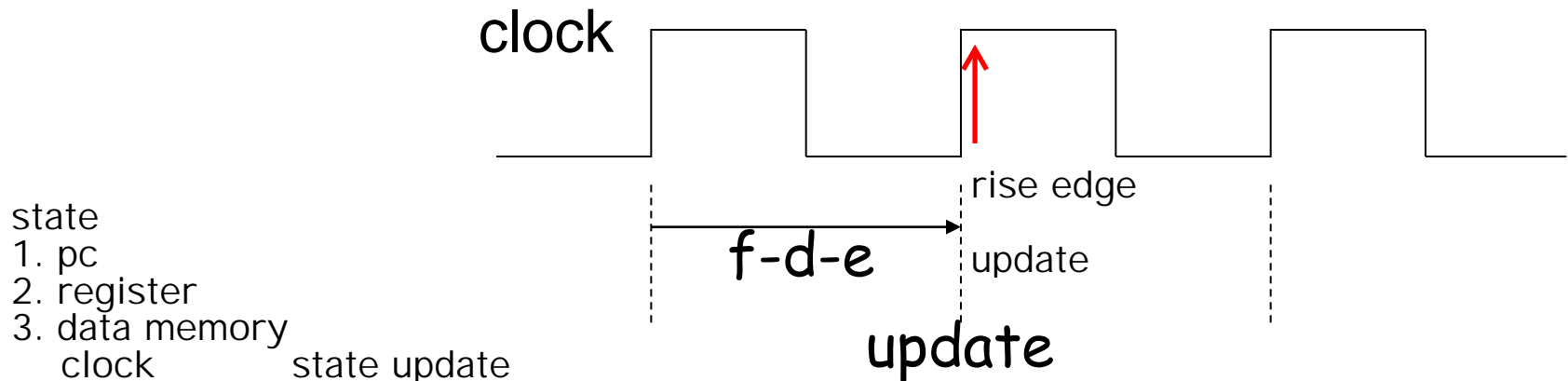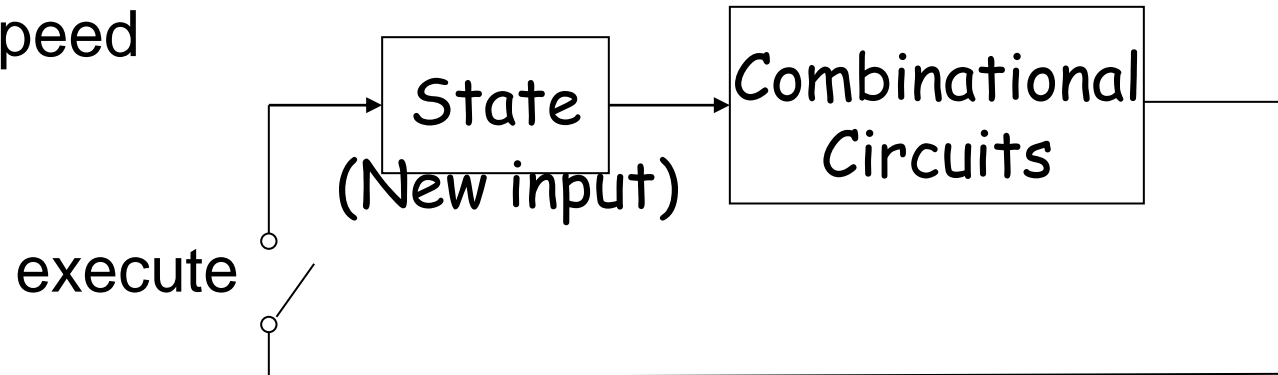


❑ Use PC to get new input by itself

Let's build a datapath

- ☐ Which can execute MIPS instructions
- ☐ Using smaller building blocks


Building Blocks (Functional Units; Abstractions)

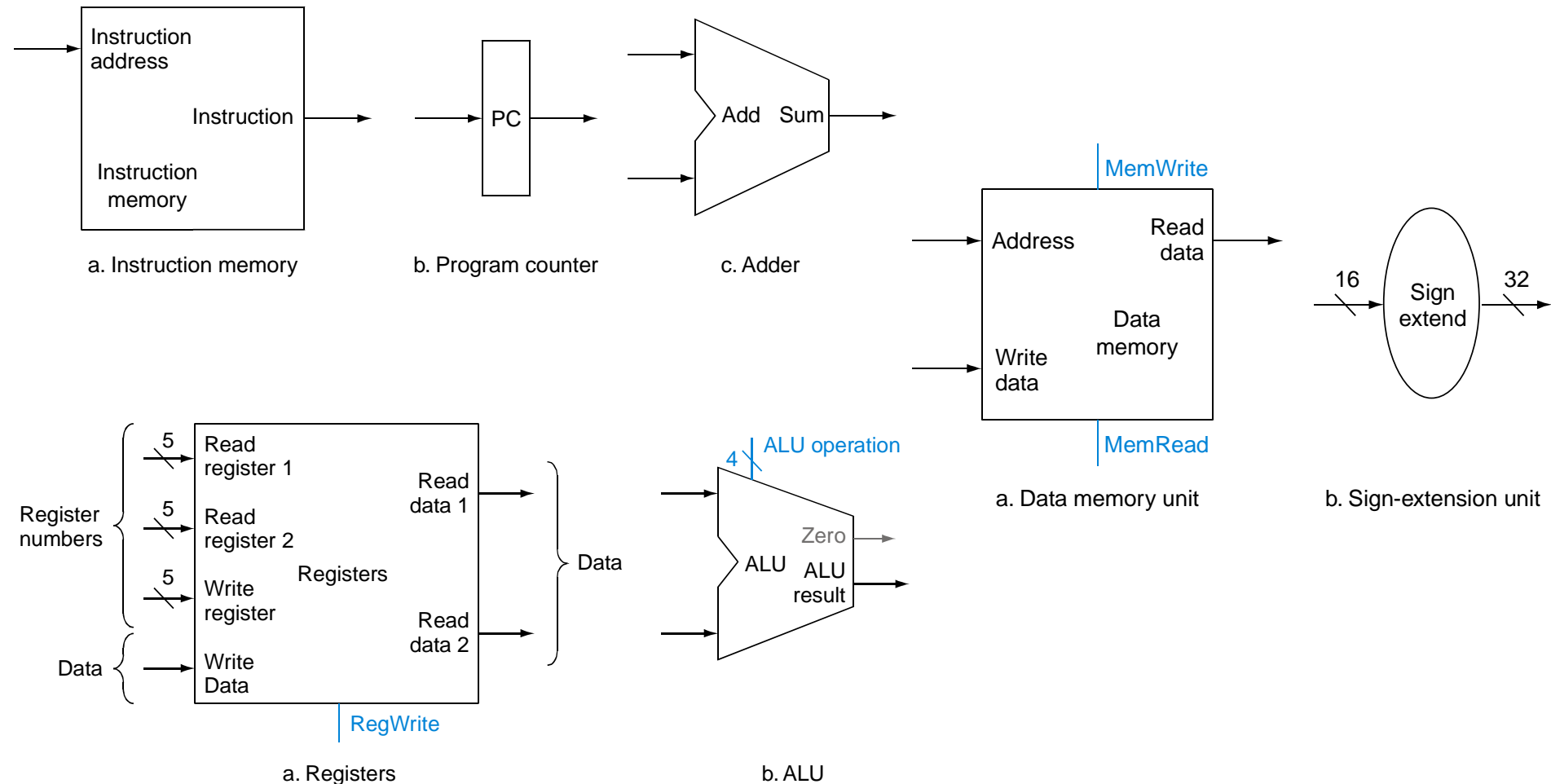□ Include the functional units we need for each instruction




Instruction Memory, Adder, ALU

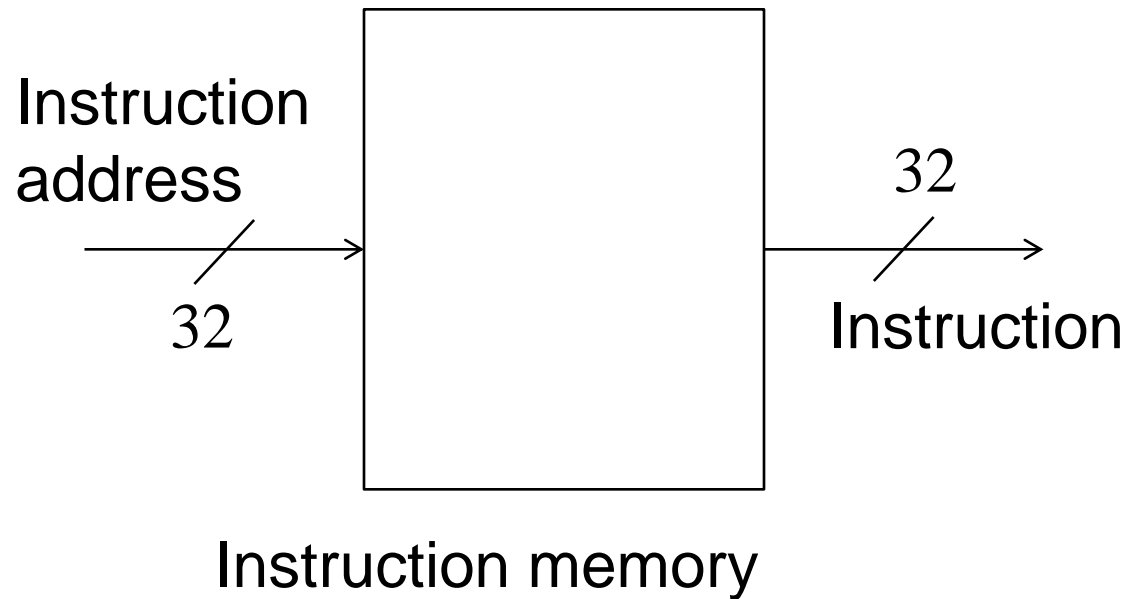- ❑ Combinational blocks: no states, nothing to do with clock




Instruction Memory, Adder, ALU

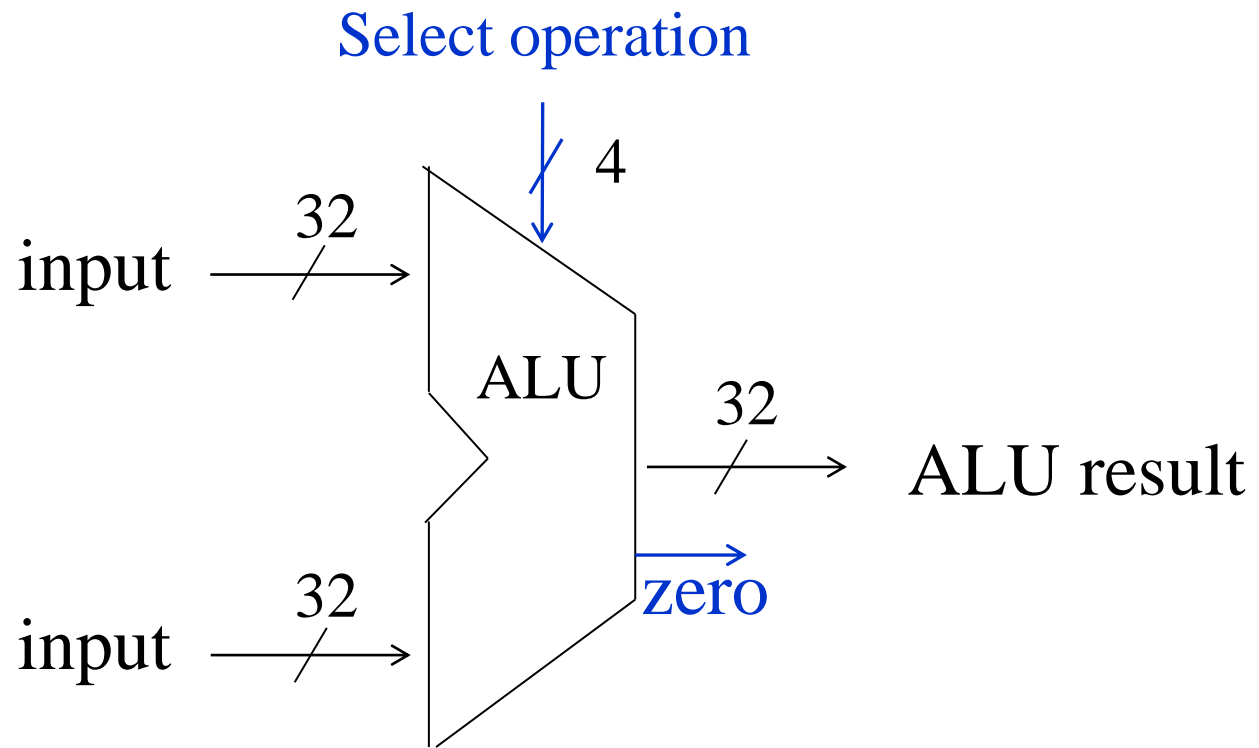- ❑ Combinational blocks: no states, nothing to do with clock




Registers (including PC)

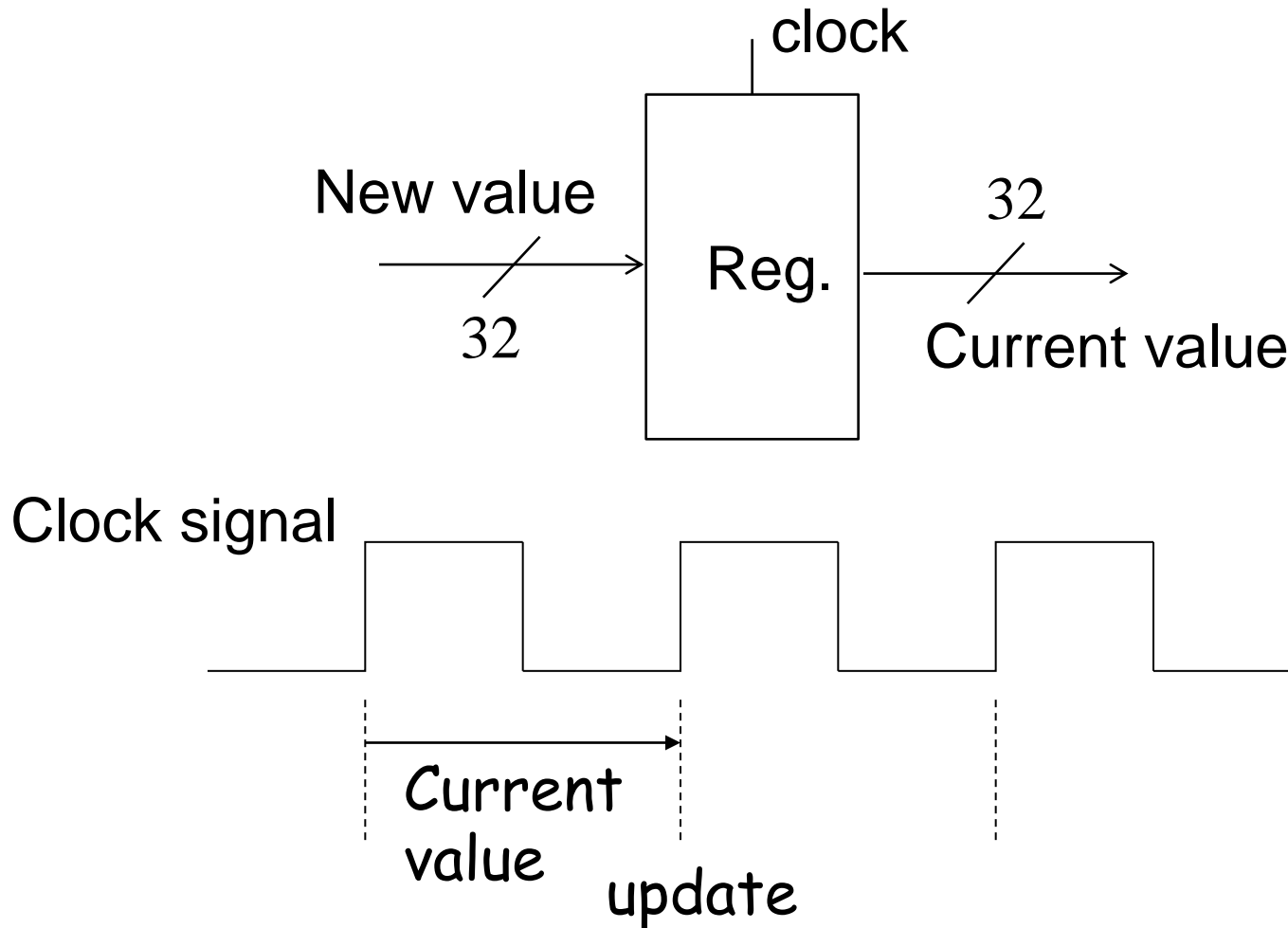- ❑ Sequential blocks: has states, in sync with clock




Sign Extension

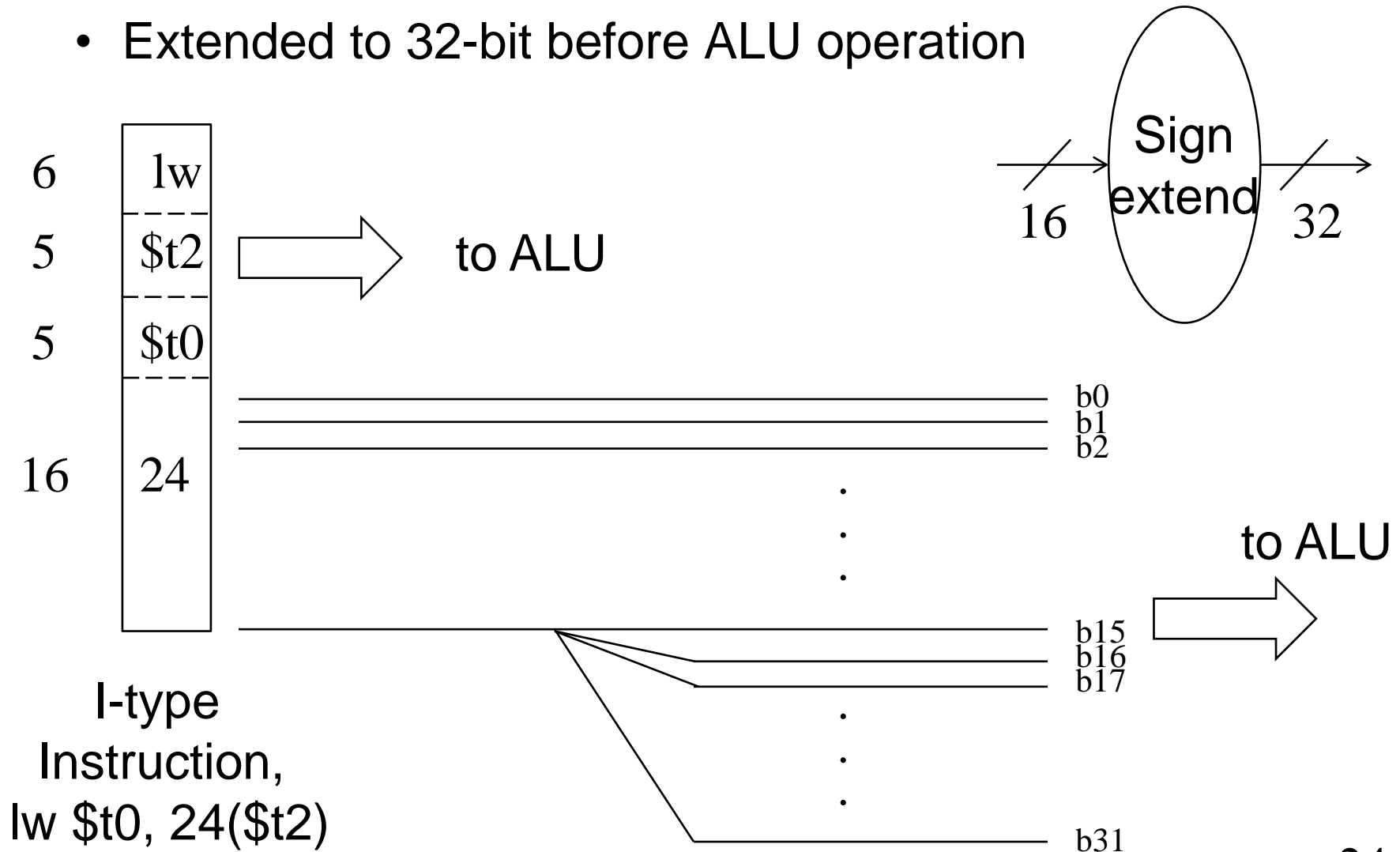- ❑ 16-bit immediate in instruction (2's complement)
 - Extended to 32-bit before ALU operation




Data Memory

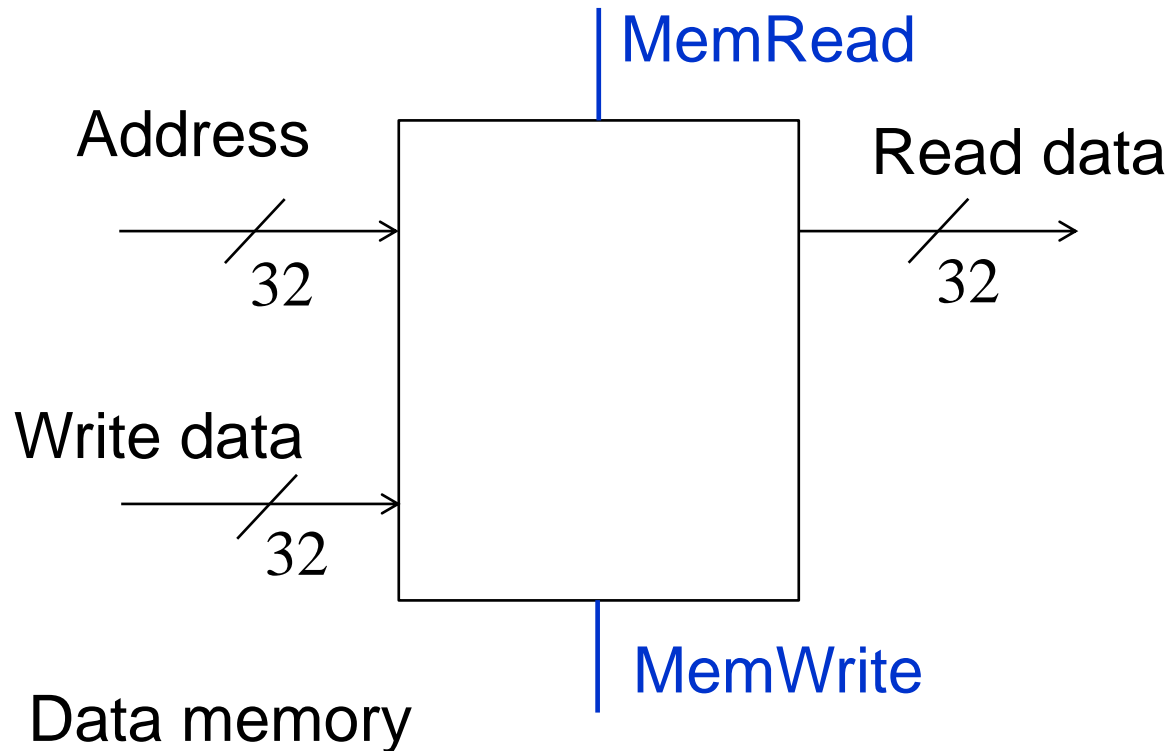- ❑ Memory read (**MemRead** = 1) // load
- ❑ Memory write (**MemWrite** = 1) // store



Register File


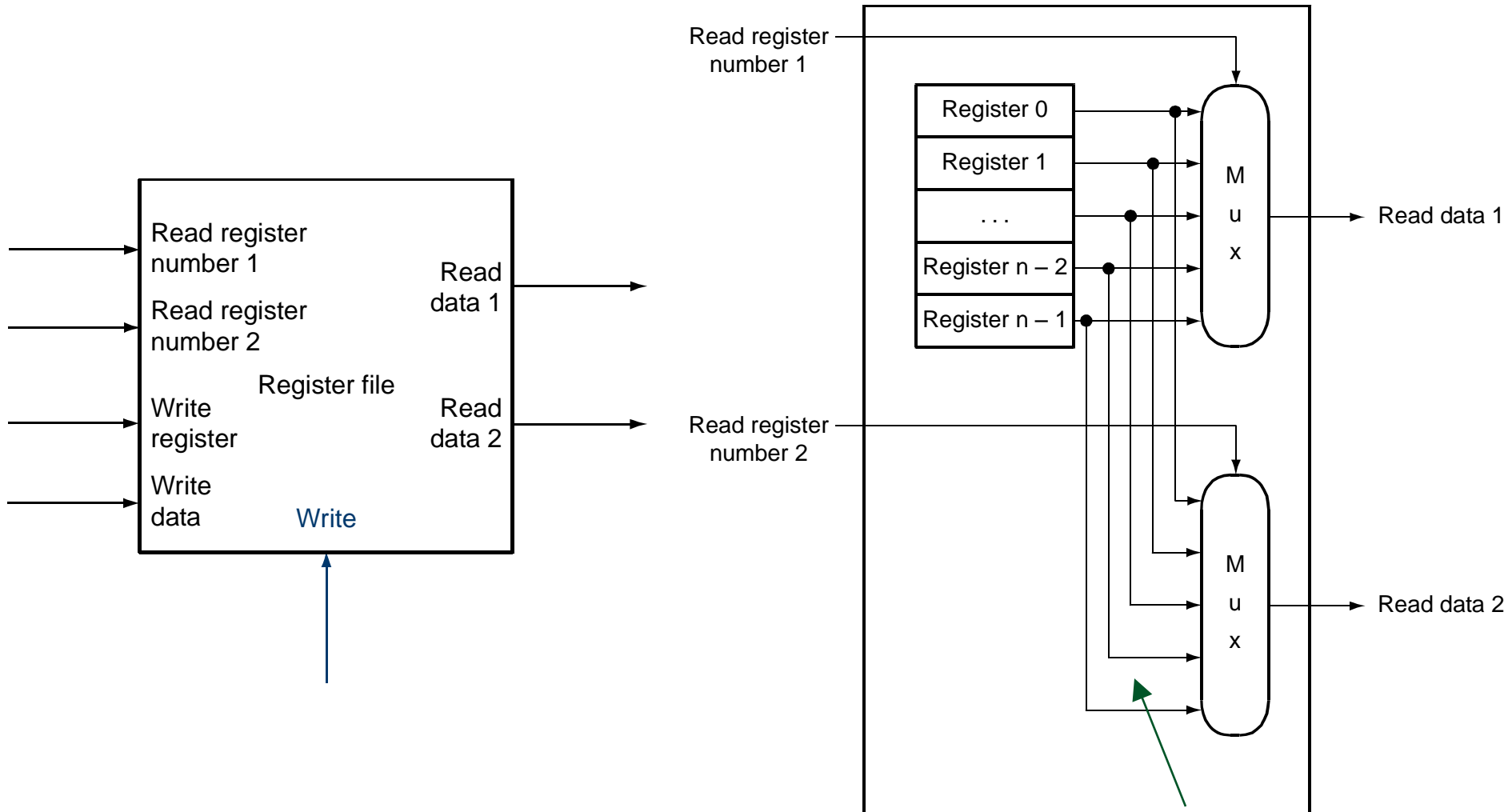


❑ Register read

- Register: built with 32 flip-flops


Multiplexer Abstraction (반복)

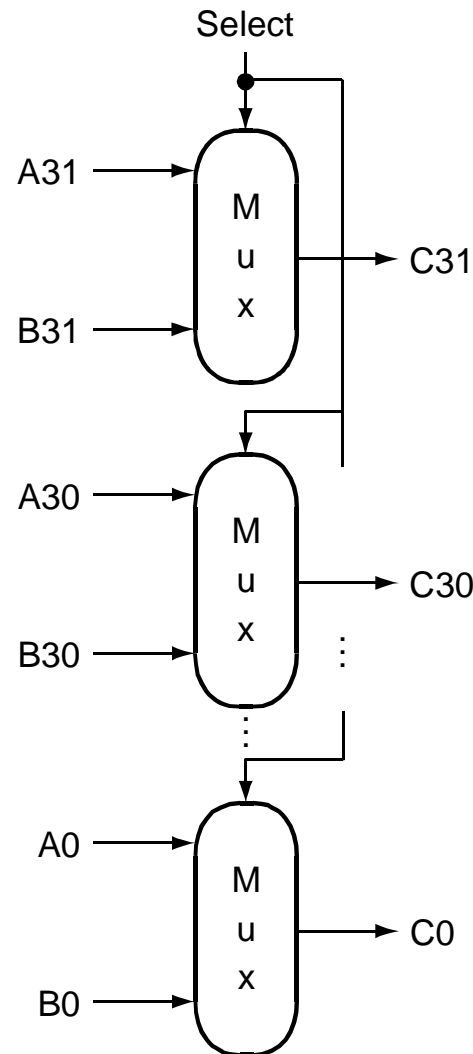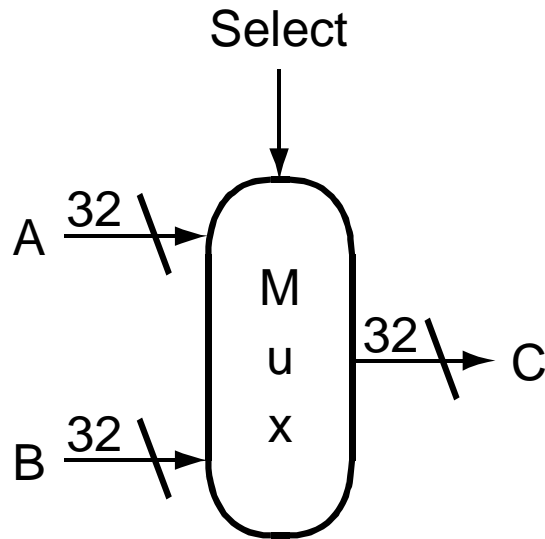- ❑ Make sure you understand the abstractions!
- ❑ 32 of 2-to-1 mux




Register File

□ Write

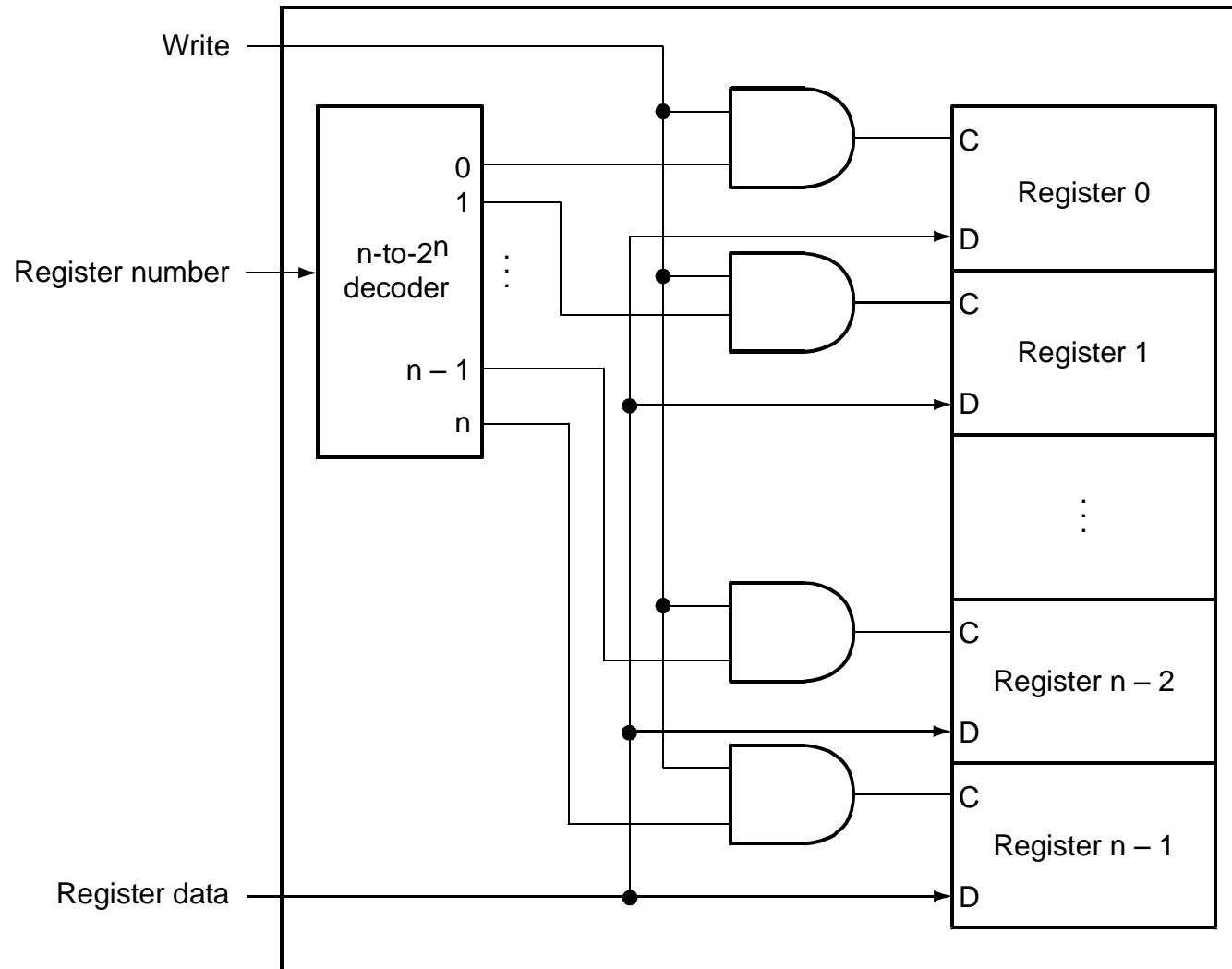


Instruction Fetch

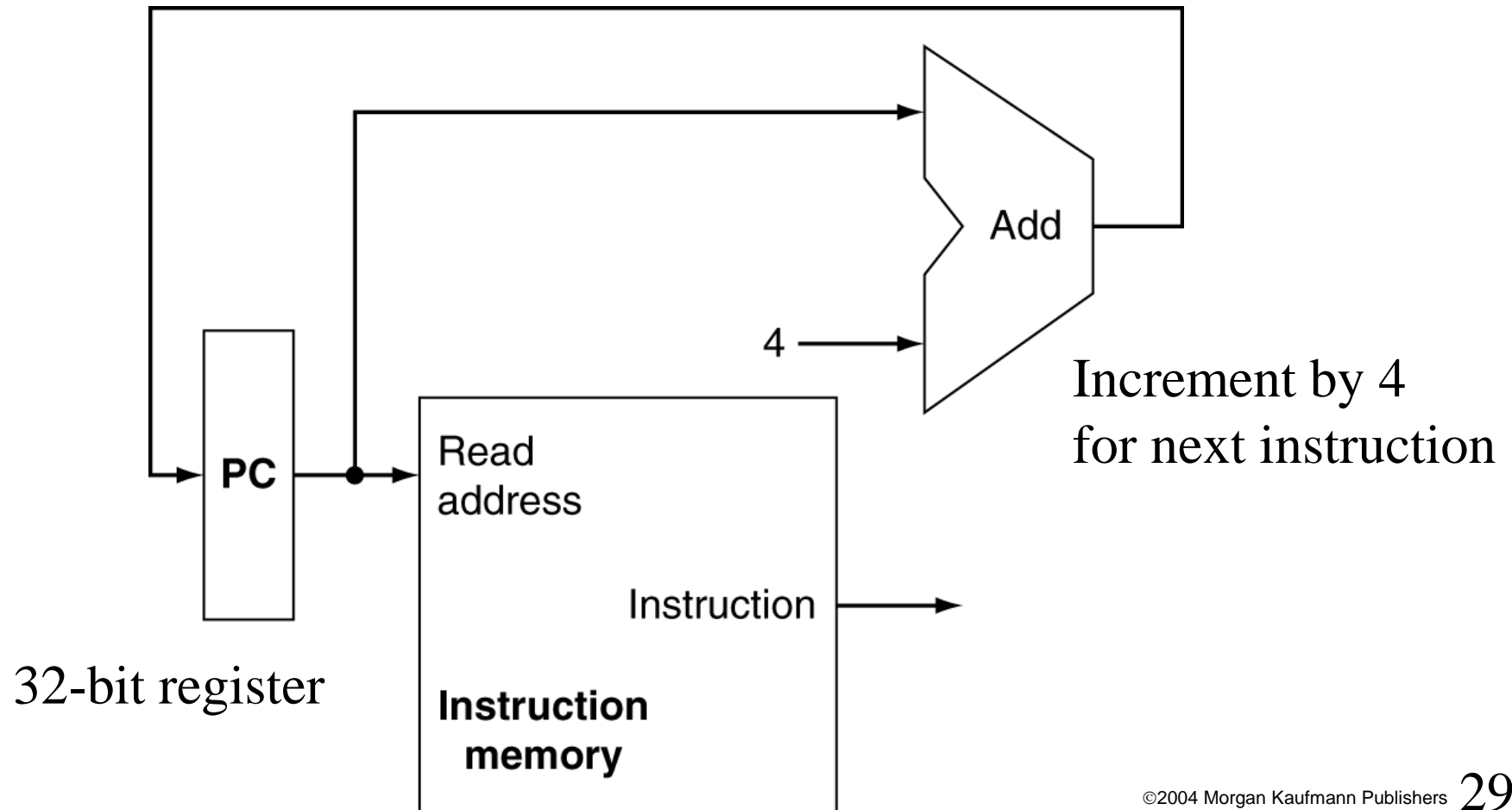- ❑ What happens?
- ❑ Combinational or sequential?




R-Format Instructions

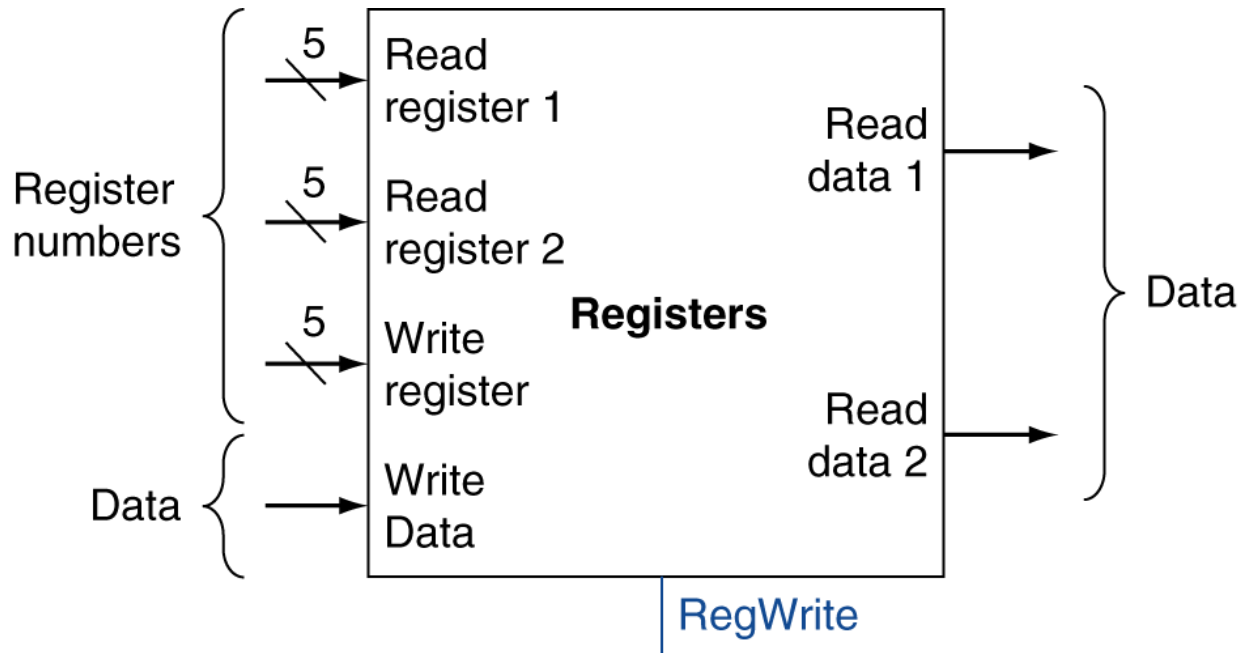- ❑ Read two register operands
- ❑ Perform arithmetic/logical operation
- ❑ Write register result



a. Registers

 

b. ALU

How do we execute MIPS instructions?

❑ ALU instructions

add \$t0, \$t1, \$t2 // R-type

addi \$t0, \$t1, 4 // I-type

❑ Data transfer instructions

lw \$t0, 12(\$t1) // I-type

st \$t0, 12(\$t1)

❑ Branch instructions


beq \$t0, \$t1, 8 // I-type

R	op	rs	rt	rd	shamt	funct
I	op	rs	rt	16 bit address		
J	op	26 bit address				

Load/Store Instructions

- ❑ Read register operands
- ❑ Calculate address using 16-bit offset
 - Use ALU, but sign-extend offset
- ❑ Load: Read memory and update register
- ❑ Store: Write register value to memory


Load/Store Instructions

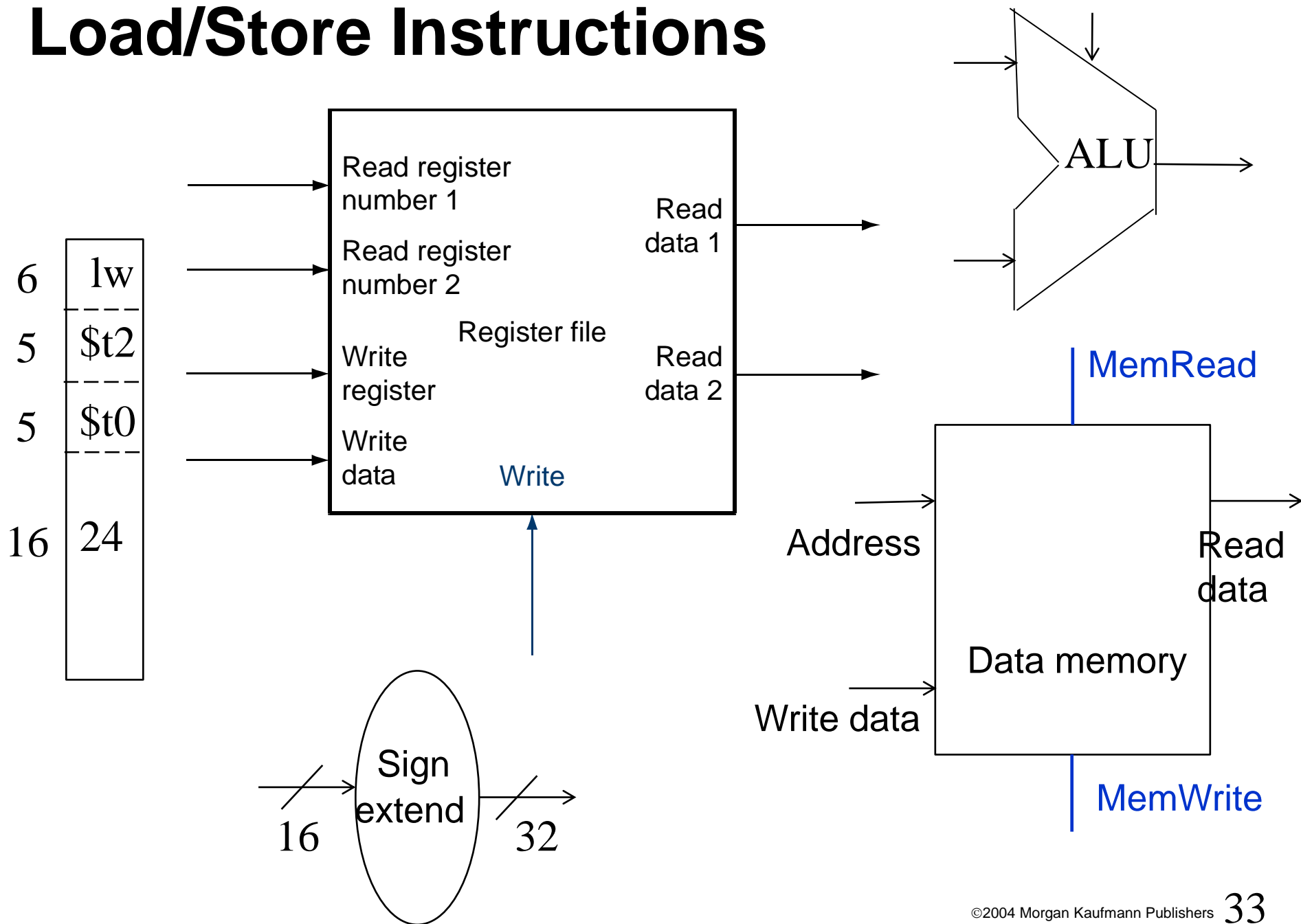

Branch Instructions


- ❑ Read register operands
- ❑ Compare operands
 - Use ALU, subtract and check Zero output
- ❑ Calculate target address
 - Sign-extend displacement
 - Shift left 2 places (word displacement)
 - Add to PC + 4
 - Already calculated by instruction fetch

Branch Instructions

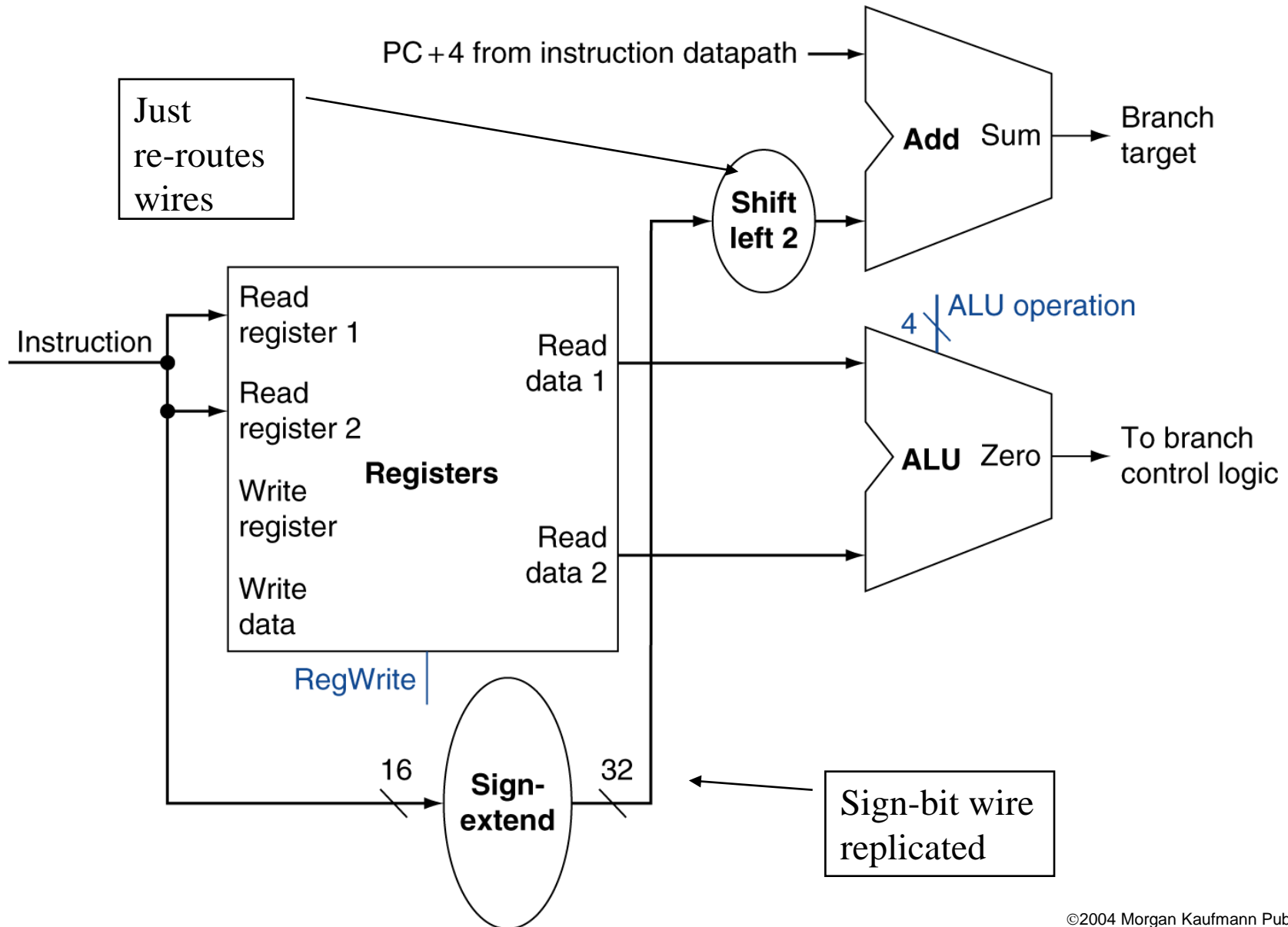

Building the Datapath

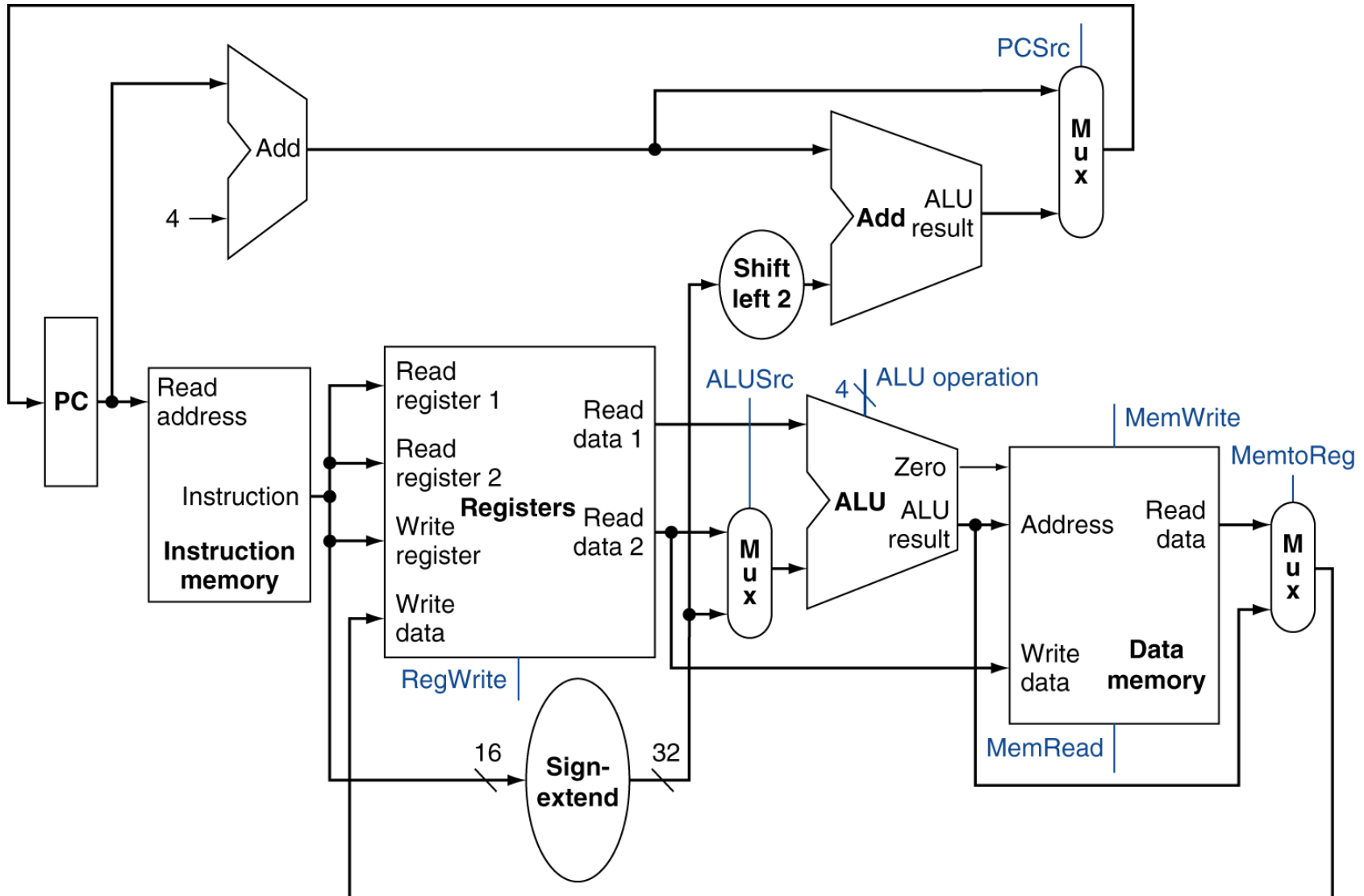- ❑ Use multiplexors to stitch them together



Building the Datapath

☐ What is datapath?

- Major functional units, flow of data between them
- † Must execute all MIPS instructions

☐ Use multiplexers where alternate data sources are used for different instructions

- Colored control signals

☐ Does it look familiar?


- Because you understand high-level behavior (ISA)


☐ Datapath design is high-level organization

- Affect CPI and clock cycle time
 - Will come back to this in pipelined design

Building the Datapath

- Datapath derived from instruction

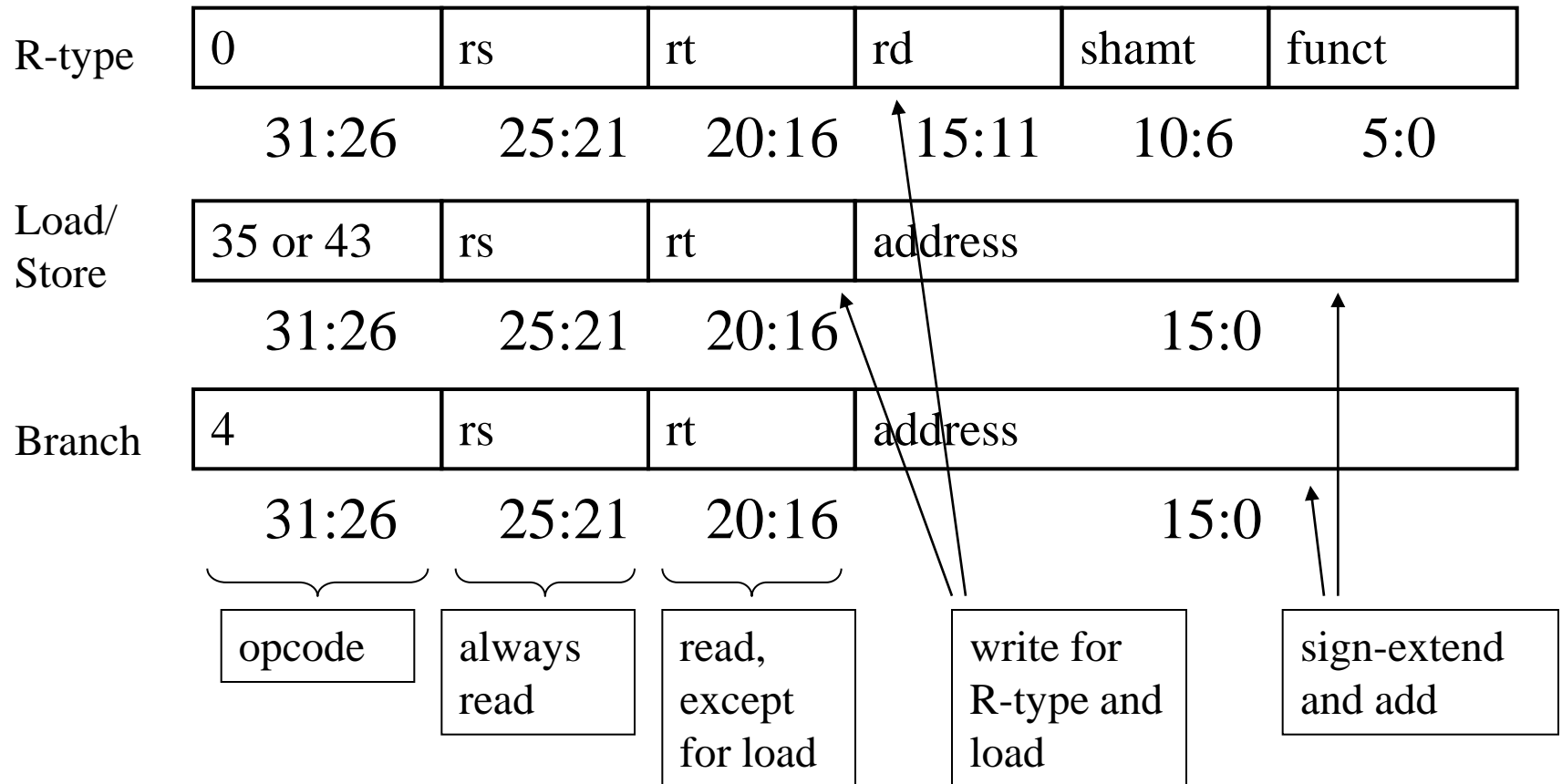

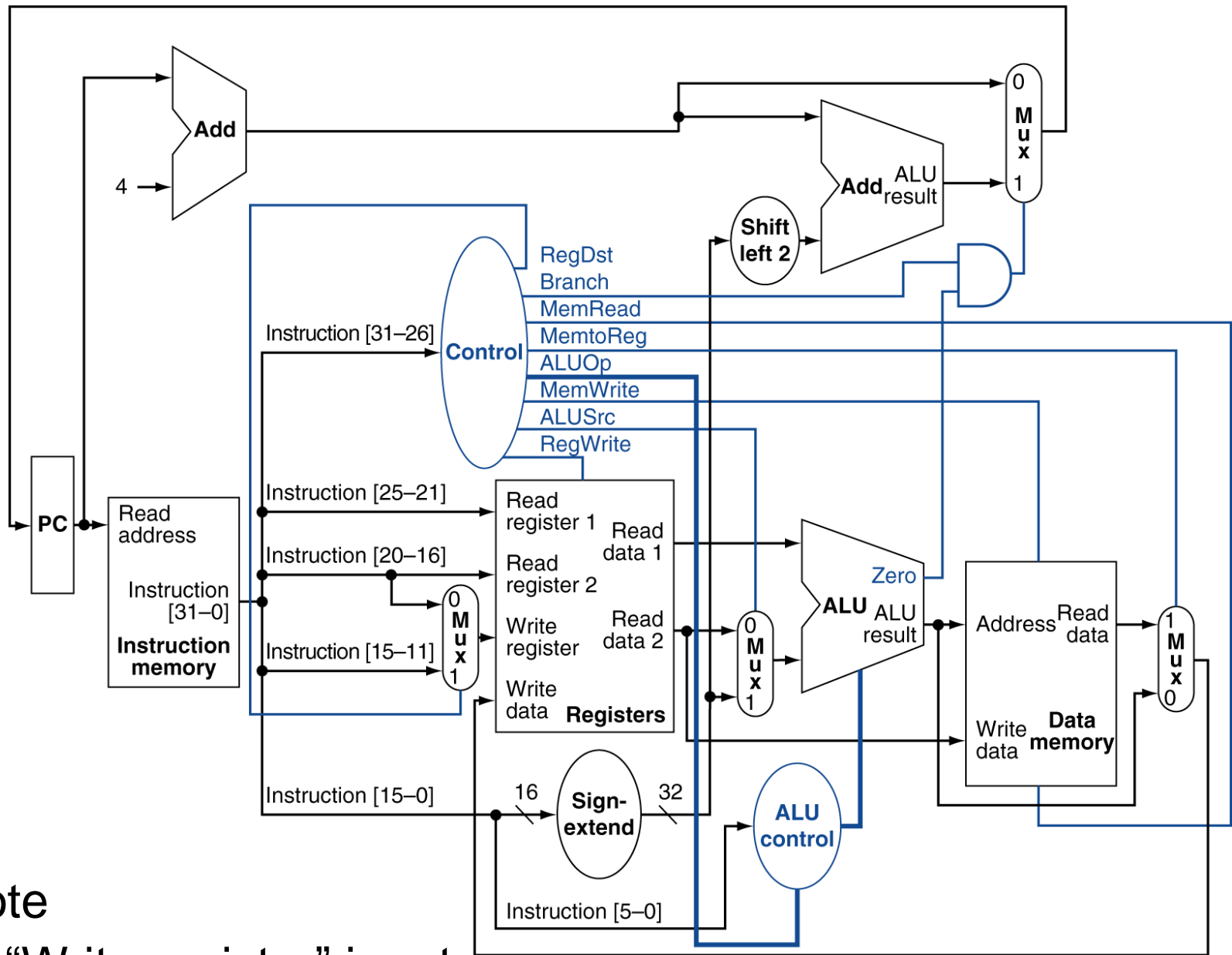


□ Note

- “Write register” input
- Colored control signals – what is “decode”?

Control Design

- ❑ Control
 - Given instruction, determine values of control signals
 - That's decoding
- ❑ Note: simultaneous decode and register read
- ❑ Do you understand the terms: datapath and control?
 - Think about any chip design (e.g., MPEG2, DES)
 - † Performance - quantitative approach
- ❑ ISA designer (architect) consider them during ISA design
 - Higher-level design require deep understanding of lower-level designs

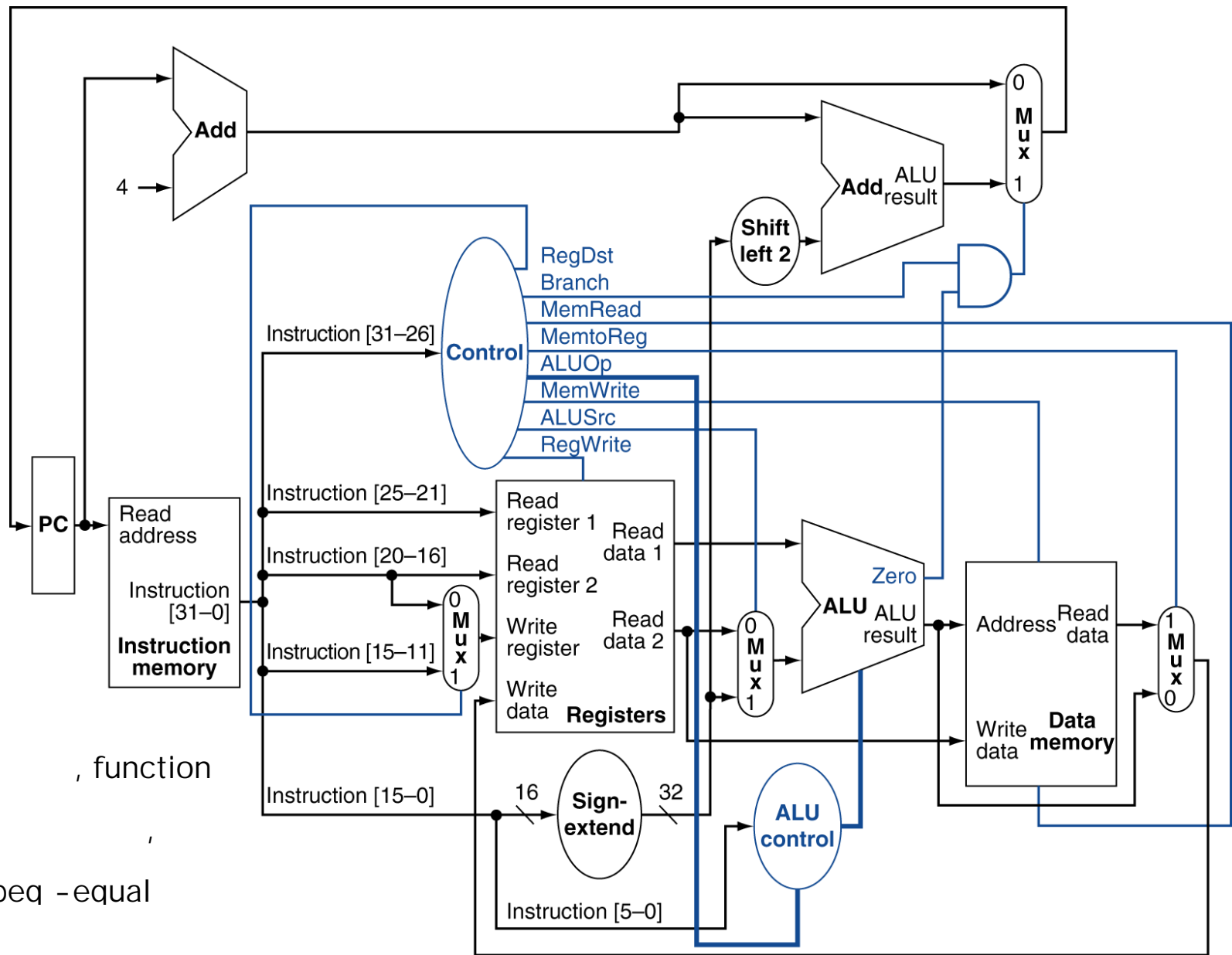

ALU control
 1. R-format
 field , function
 2. R-format
 alu operation ,
 ex) lw - add, beq - equal

Note

- Simultaneous decode and register read

Control Design

- ❑ Decoding: determine the values of colored control signals
 - Selecting operations to perform (ALU, read/write, etc.)
 - Controlling the flow of data (multiplexor inputs)
- ❑ Information comes from the 32 bits of the instruction
 - opcode and function code

add \$8, \$17, \$18

000000	10001	10010	01000	00000	100000
--------	-------	-------	-------	-------	--------

op	rs	rt	rd	shamt	funct
----	----	----	----	-------	-------

Control Design

- ❑ Two separate control units for simplicity
 - Lower ALU control unit: select ALU operation
 - Upper control unit: the rest of control
- ❑ Let's design lower ALU control unit first

Lower ALU Control Unit

☐ What should the ALU do with this instruction? add

- Example: lw \$1, 100(\$2)

35	2	1	100
----	---	---	-----

op	rs	rt	16-bit offset
----	----	----	---------------

☐ What ALU should do for “beq”? minus

☐ What ALU should do for R-type instructions? function field

Lower ALU Control Unit

- ❑ ALU used for
 - Load/Store: F = add
 - Branch: F = subtract
 - R-type: F depends on funct field
- ❑ ALU designed such that:

ALU control	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set-on-less-than
1100	NOR

Lower ALU Control Unit

- ❑ Assume 2-bit ALUOp derived from opcode
 - Combinational logic derives ALU control

opcode	ALUOp	Operation	funct	ALU function	ALU control
lw	00	load word	XXXXXX	add	0010
sw	00	store word	XXXXXX	add	0010
beq	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
		subtract	100010	subtract	0110
		AND	100100	AND	0000
		OR	100101	OR	0001
		set-on-less-than	101010	set-on-less-than	0111

Instruction opcode	ALUOp	Instruction operation	Func field	Desired ALU action	ALU control input
LW	00	load word	XXXXXX	add	0010
SW	00	store word	XXXXXX	add	0010
Branch equal	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
R-type	10	subtract	100010	subtract	0110
R-type	10	AND	100100	and	0000
R-type	10	OR	100101	or	0001
R-type	10	set on less than	101010	set on less than	0111

ALUOp		Func field						Operation
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	
0	0	X	X	X	X	X	X	0010
X	1	X	X	X	X	X	X	0110
1	X	X	X	0	0	0	0	0010
1	X	X	X	0	0	1	0	0110
1	X	X	X	0	1	0	0	0000
1	X	X	X	0	1	0	1	0001
1	X	X	X	1	0	1	0	0111

don't care
- 2bit

374


(don't care

logic


)

Lower ALU Control Unit

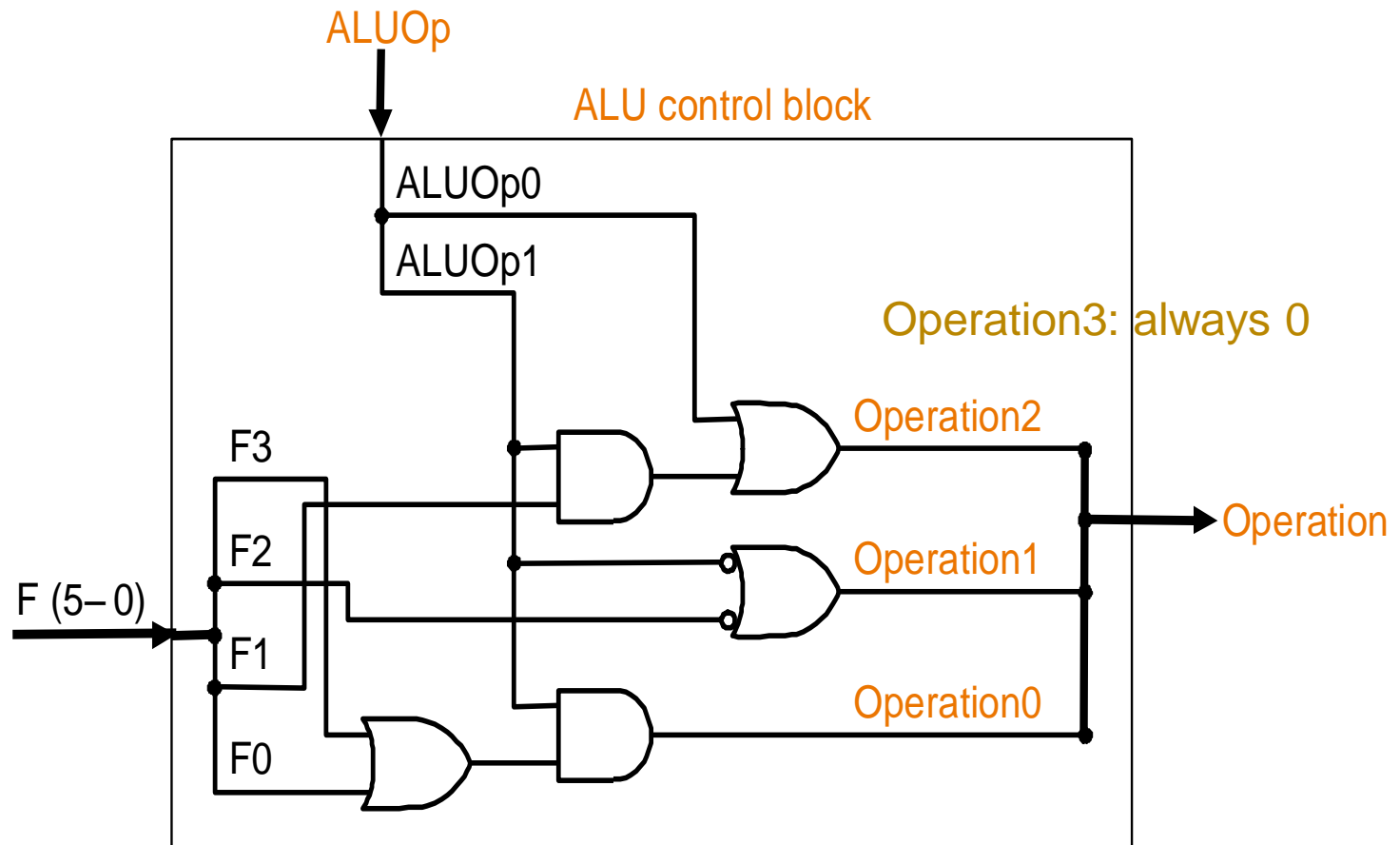
- ❑ Simple combinational logic (truth tables) – run CAD tools



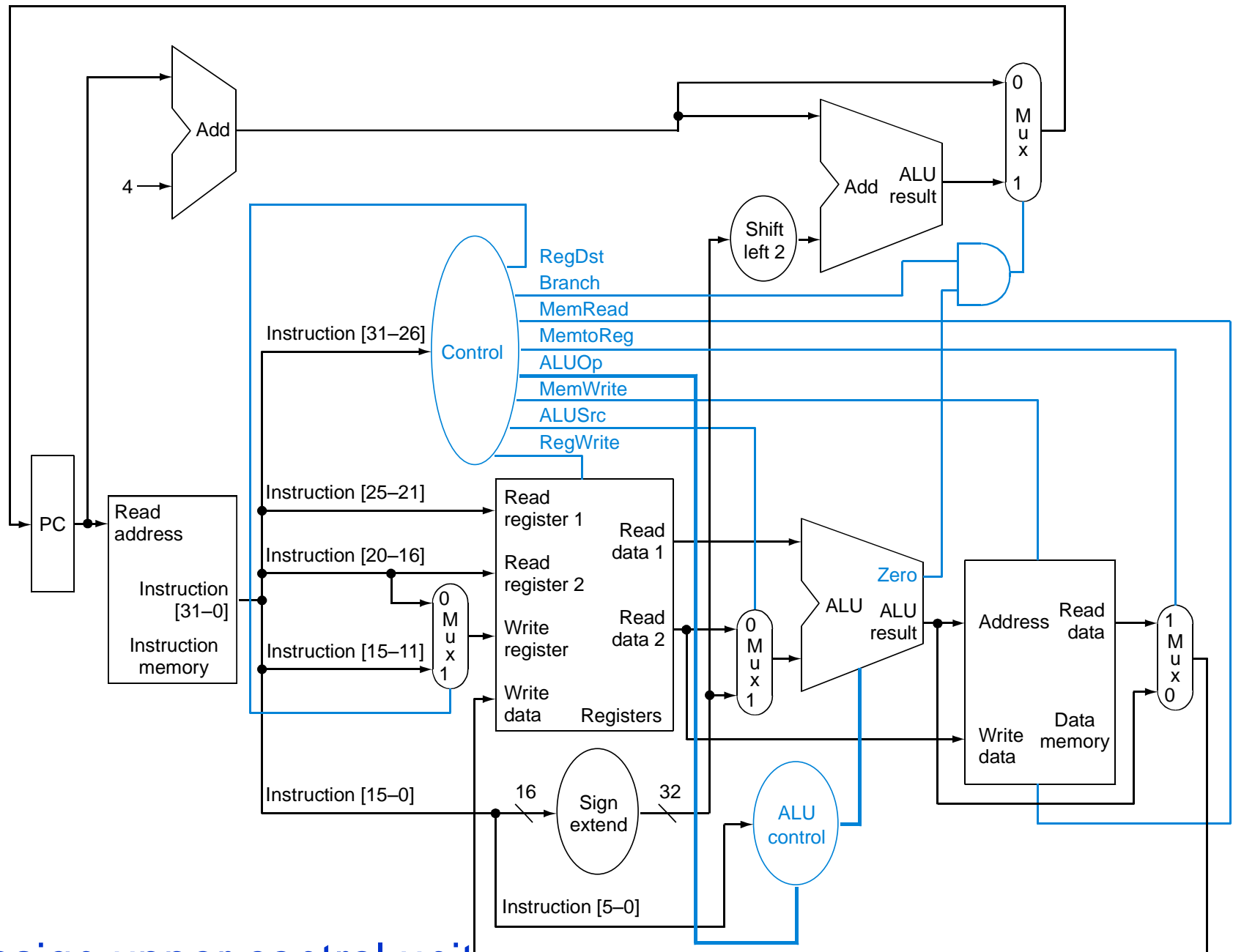- algorithm x
VLSI cad tools - truth table optimal combinational logic



Design upper control unit

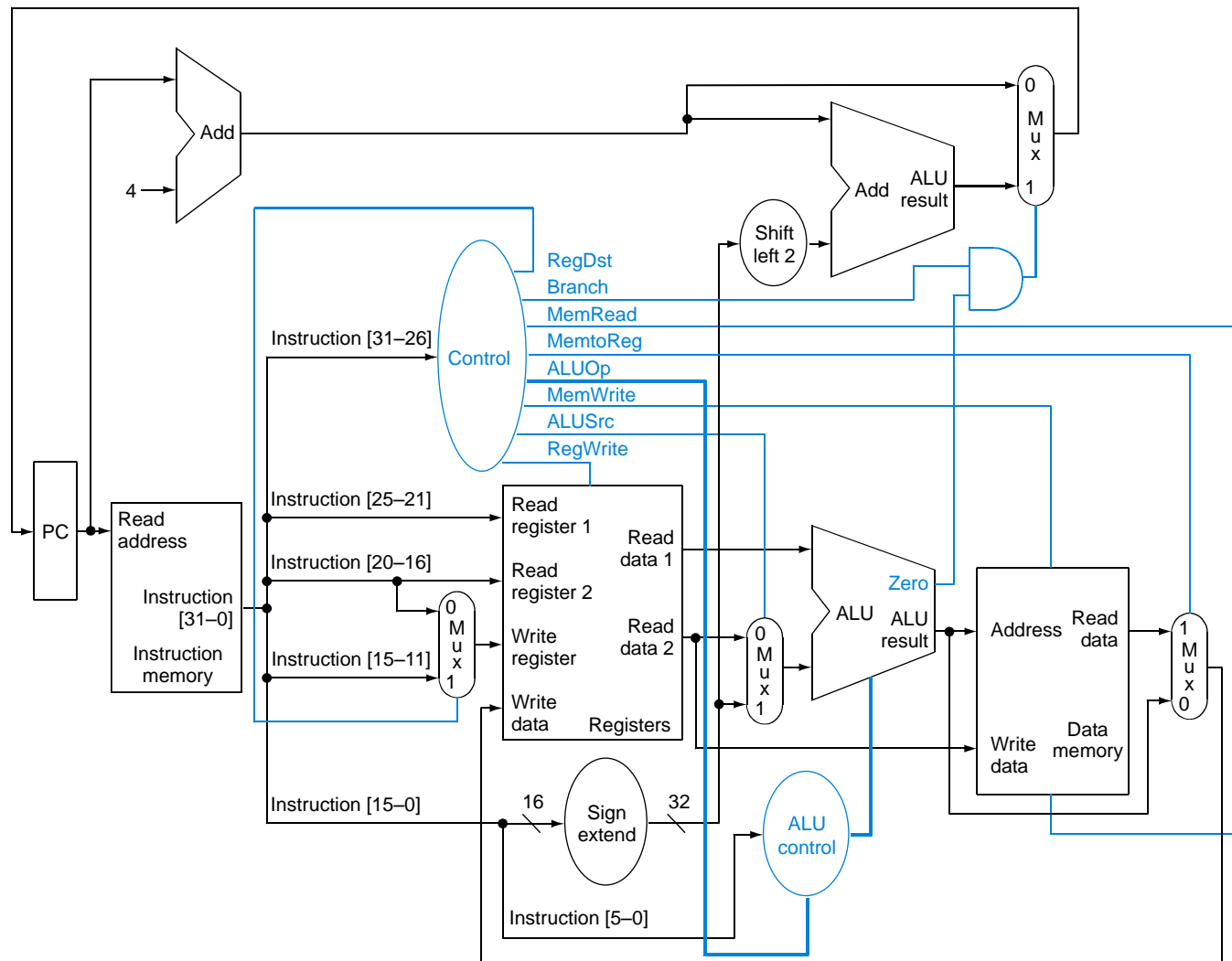


register write
don't care 가

Instruction	RegDst	ALUSrc	Memto-Reg	Reg Write	Mem Read	Mem Write	Branch	ALUOp1	ALUp0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

Upper Control Unit

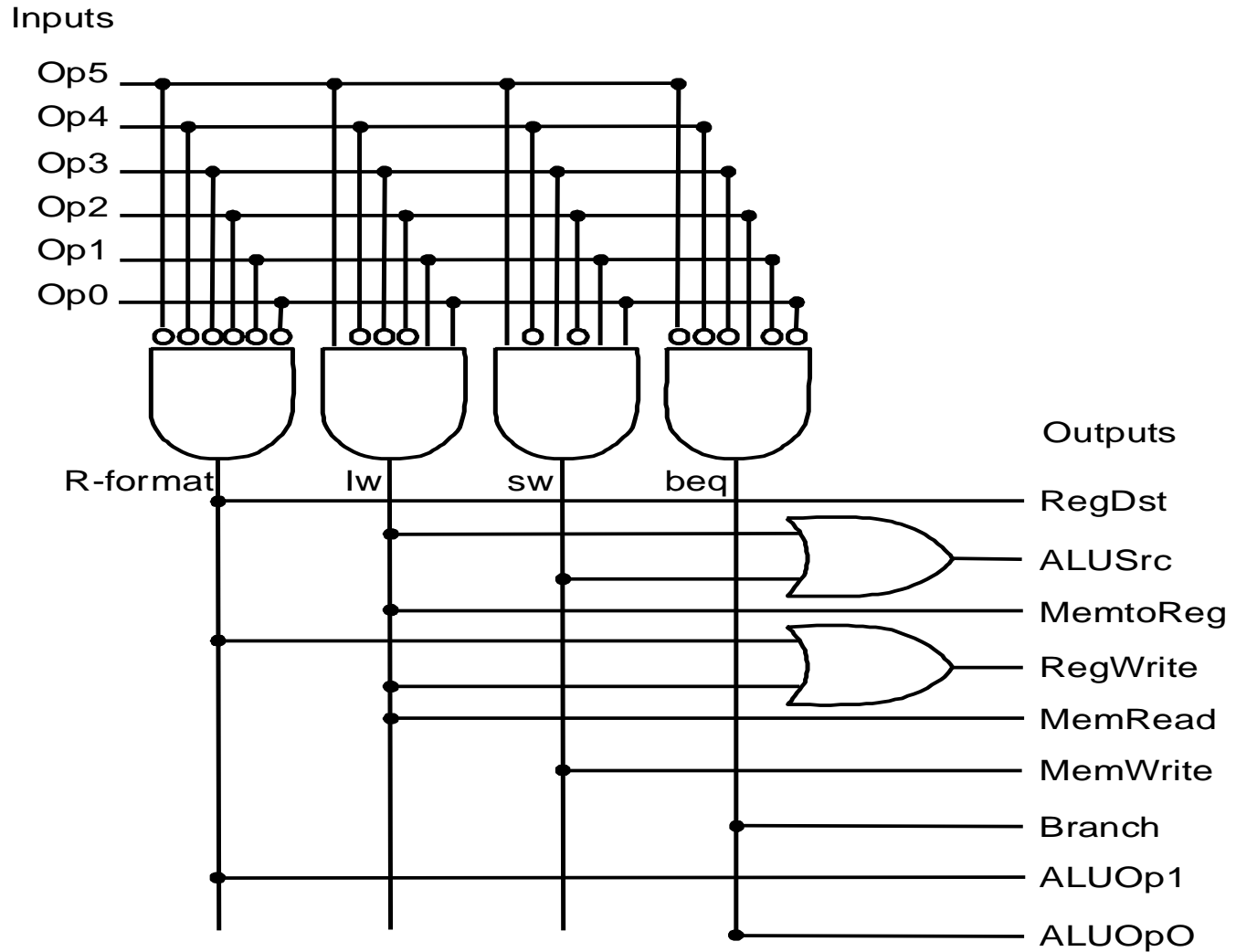- Simple combinational logic (truth tables)




Instruction Decode (반복)

- ❑ Where is it in the datapath?
 - Not shown (will come back to it)
 - Instead, what is shown is “read two operands (registers)”
 - But we do not know the instruction
 - † It does no harm
- ❑ RISC
 - Parallel instruction decoding and operand access

Control Design (반복)

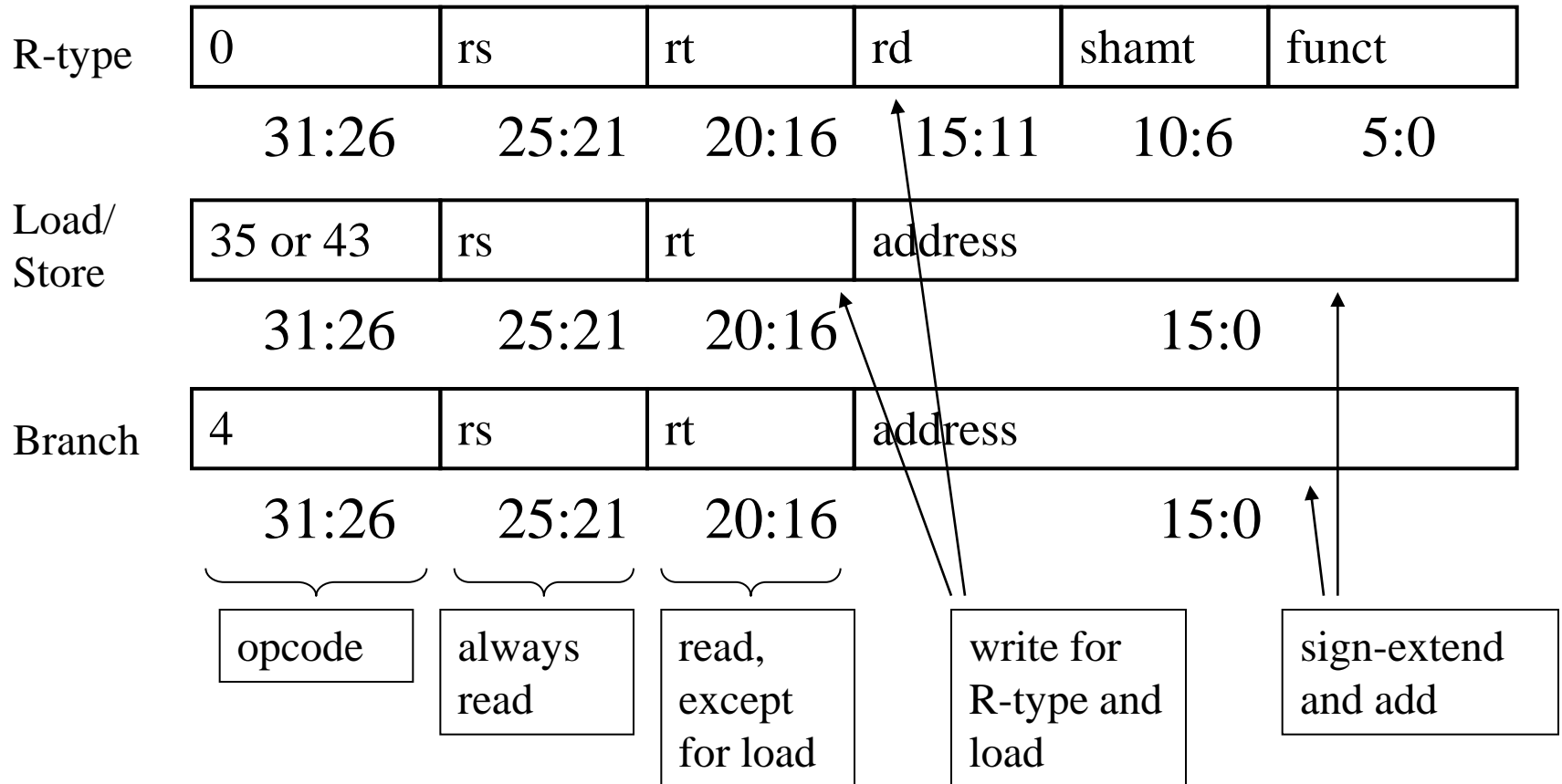❑ Control signals derived from instruction




Implemented 8 instructions


- ❑ Processors have many more instructions
- ❑ What if we want to add “jump” instruction?
 - Same principles
 - Only more datapath and control

Want to implement “jump” instruction?

- ❑ More datapath and control

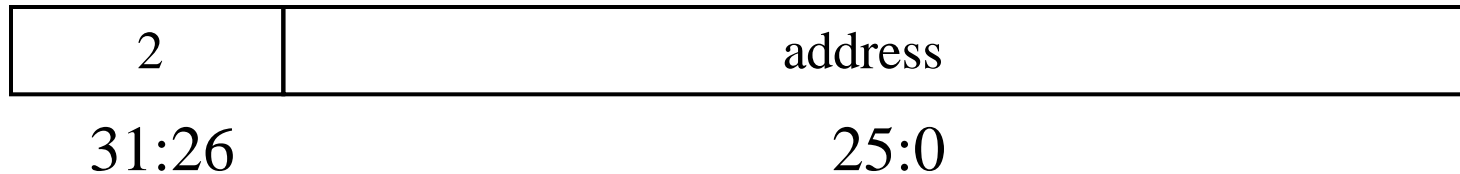

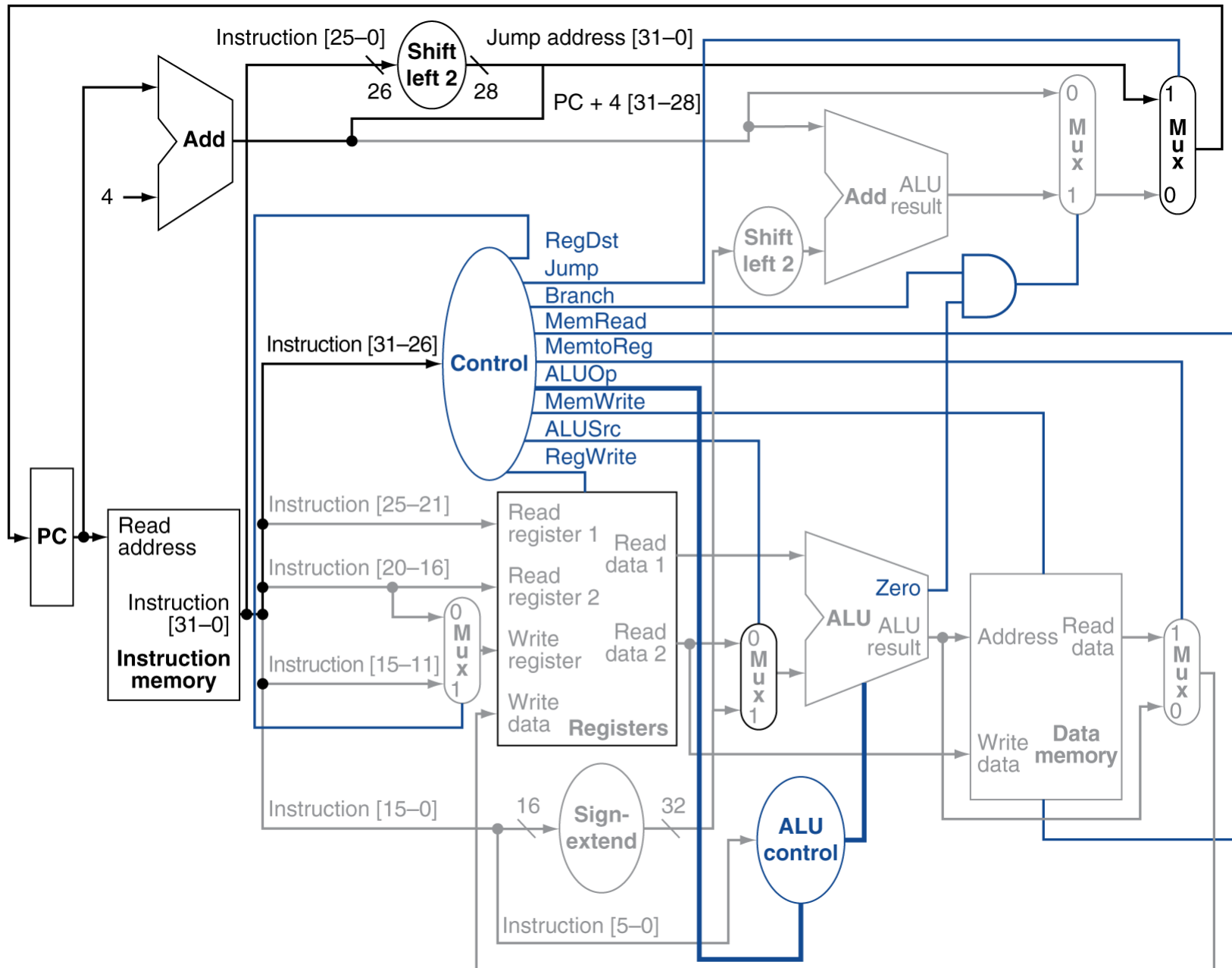- Jump uses word address
- Update PC with concatenation of
 - Most-significant 4 bits of PC
 - 26-bit jump address
 - † 28-bit byte address
- Need an extra control signal decoded from opcode



Control for “jump” instructions

- ❑ One more output signal for control unit
 - Let’s call it “jump”
 - One more column in truth table
- ❑ New jump instruction to implement
 - One more row in truth table

Instruction	RegDst	ALUSrc	Memto-Reg	Reg Write	Mem Read	Mem Write	Branch	ALUOp1	ALUOp0	Jump
R-format	1	0	0	1	0	0	0	1	0	0
lw	0	1	1	1	1	0	0	0	0	0
sw	X	1	X	0	0	1	0	0	0	0
beq	X	0	X	0	0	0	1	0	1	0
Jump	X	X	X	0	X	0	X	X	X	1

read write instruction data data

Processor Design Done


- ❑ How do we fabricate our processor?
 - What if we visit Intel or Samsung?
 - Same situation when developing industry prototypes
- ❑ Field programmable logic (FPGA) by Altera or Xilinx
 - Software tool (and FPGA chips)
 - VHDL/Verilog description of our design
 - Compile and test
 - Dump to FPGA chips
- † You will do the first two steps as class project
 - See related materials in class homepage

RISC Processor Design Project

- ☐ Descriptions in class homepage
- ☐ TA hour?

Single Cycle Implementation

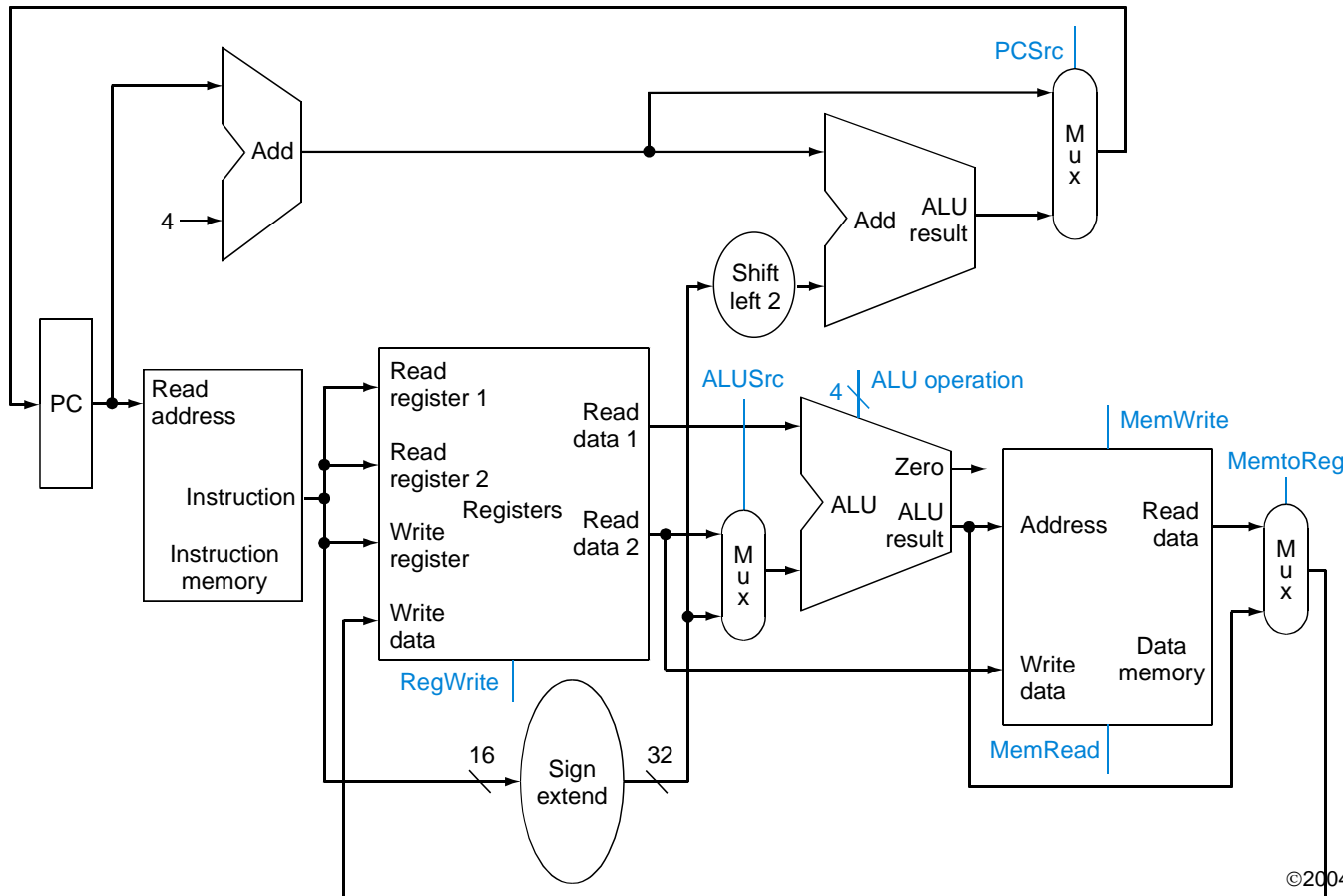- ❑ Calculate cycle time assuming negligible delays except:
 - memory (200ps), ALU and adders (200ps), register file access (100ps)




Single cycle implementation

Instr	Instr fetch	Register read	ALU op	Memory access	Register write	Total time
lw	200ps	100 ps	200ps	200ps	100 ps	800ps
sw	200ps	100 ps	200ps	200ps		700ps
R-format	200ps	100 ps	200ps		100 ps	600ps
beq	200ps	100 ps	200ps			500ps

❑ To think about

- Longest delay determines clock period
 - Critical path: load instruction (also think about “mult”)
- Violates design principle
 - Making the common case fast
- We will improve performance by pipelining


Our Single Cycle Implementation

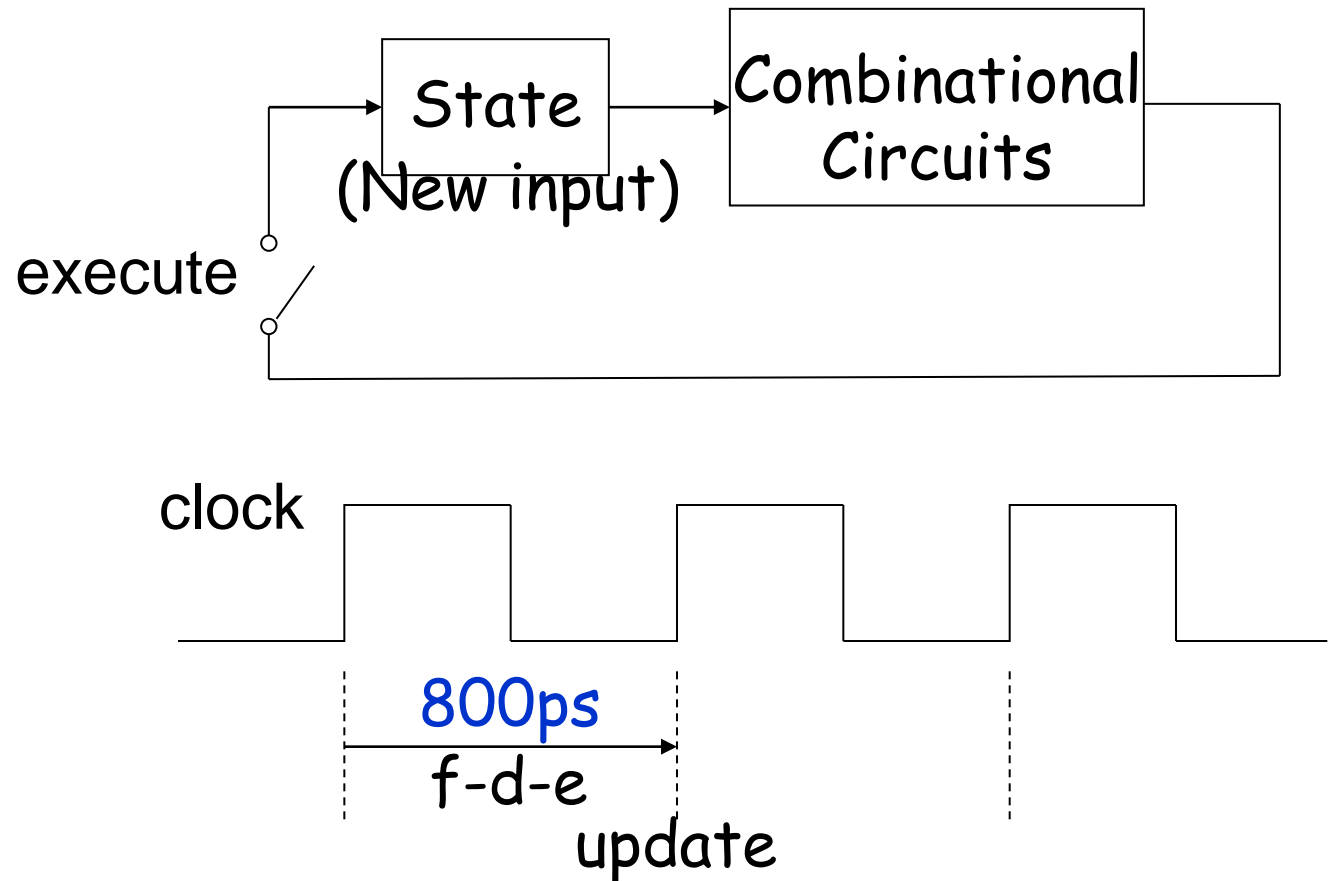


- ❑ Cycle time determined by length of the longest path

High-Level Org.: CPI and Clock Cycle

 - ❑ Single-cycle: $\text{CPI} = 1$, clock cycle



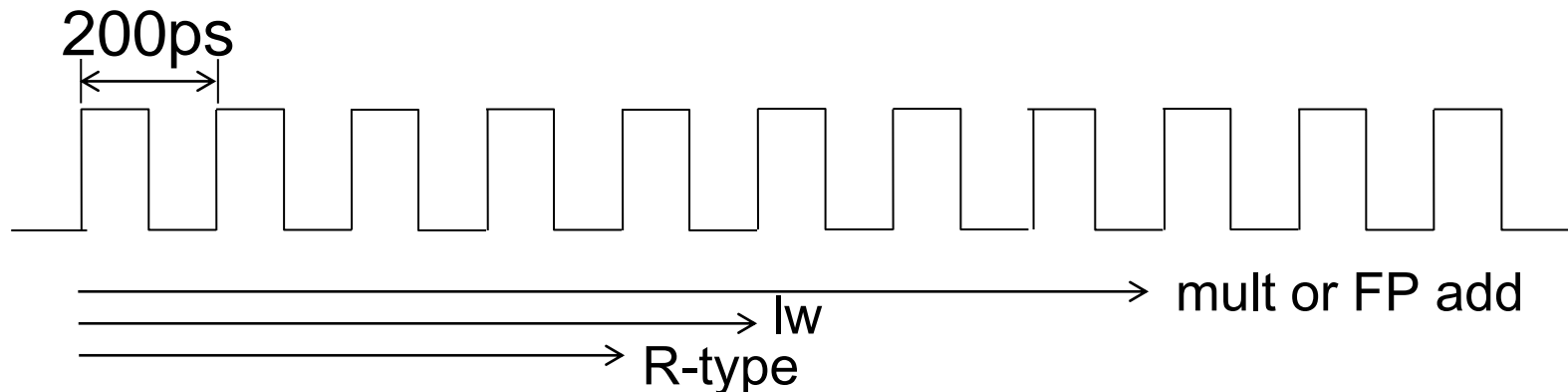- ❑ Multi-cycle: $\text{CPI} \uparrow$, clock cycle \downarrow , overall performance \uparrow



- ❑ Pipelined: $\text{CPI} = 1$, clock cycle \downarrow


MIPS Pipeline

- Five stages, one step per stage
 1. IF: Instruction fetch from memory
 2. ID: Instruction decode & register read
 3. EX: Execute operation or calculate address
 4. MEM: Access memory operand
 5. WB: Write result back to register

Instr	Instr fetch	Register read	ALU op	Memory access	Register write	Total time
lw	200ps	100 ps	200ps	200ps	100 ps	800ps
sw	200ps	100 ps	200ps	200ps		700ps
R-format	200ps	100 ps	200ps		100 ps	600ps
beq	200ps	100 ps	200ps			500ps

Multicycle vs. Pipeline

- ❑ Each stage run different instruction

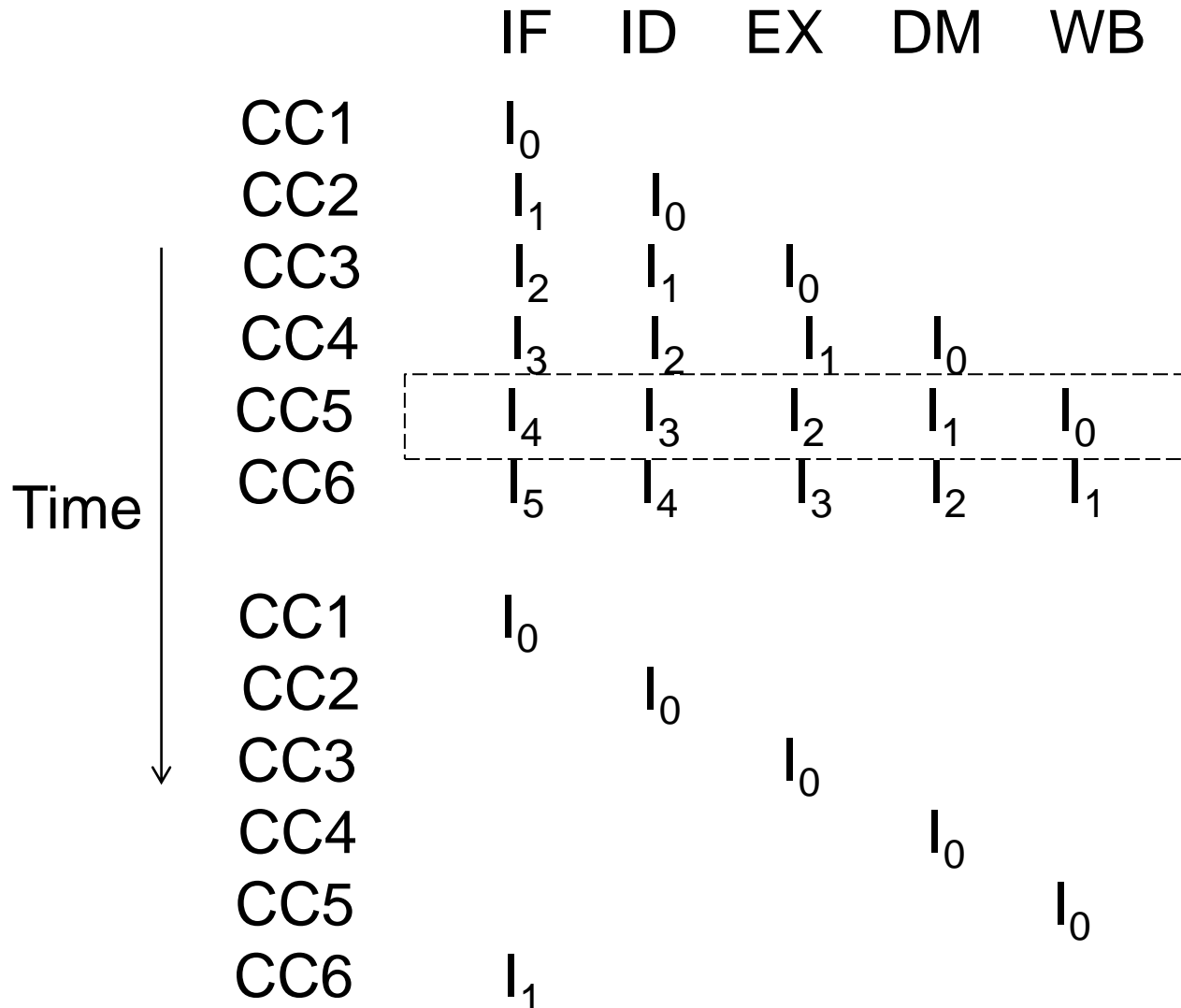

Where we are headed

- ❑ Single Cycle Problems:
 - What if we had a more complicated instruction like floating point?
- ❑ Multicycle implementation (will cover very lightly)
 - Use a “smaller” cycle time
 - Different instructions take different numbers of cycles
- ❑ Pipelining (pipelined datapath and control)
 - Overlapped instruction execution
 - Instruction-level parallelism
 - † Can improve both CPI and clock cycle time