

# Electrical Engineering

## HW 1 – Chapter 2, Solution

<1>

**Solution:**

**Known quantities:**

$$i_o = 2 \text{ A}, \quad i_2 = -7 \text{ A}$$

**Find:**

- a)  $i_1$
- b)  $i_3$

**Analysis:**

- a) Use KCL at the node between  $R_0$ ,  $R_1$ , and  $R_2$ .

$$i_o - i_1 + i_2 = 0$$

$$i_1 = i_o + i_2$$

$$i_1 = -5 \text{ A}$$

- b) Use KCL at the node between  $R_2$ ,  $R_3$ , and the current source.

$$6 \text{ A} + i_3 - i_2 = 0$$

$$i_3 = i_2 - 6 \text{ A}$$

$$i_3 = -11 \text{ A}$$

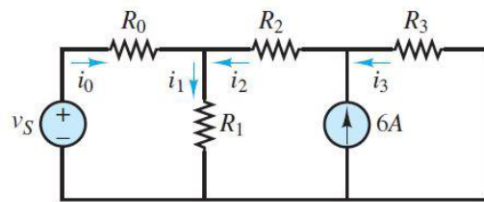


Figure P2.13

<2>

### Problem 2.17

Use KCL to determine the unknown currents in Figure P2.17.

**Solution:**

**Known quantities:**

$$i_a = -2 \text{ A}, \quad i_b = 6 \text{ A}, \quad i_c = 1 \text{ A}, \quad i_d = -4 \text{ A}$$

**Find:**

- a)  $i_1$
- b)  $i_2$
- c)  $i_3$
- d)  $i_4$

**Analysis:**

- a) Use KCL at Node A.

$$i_1 - i_a - i_c = 0$$

$$i_1 = i_a + i_c$$

$$i_1 = -1 \text{ A}$$

- b) Use KCL at Node B.

$$i_2 - i_1 - i_b = 0$$

$$i_2 = i_1 + i_b$$

$$i_2 = 5 \text{ A}$$

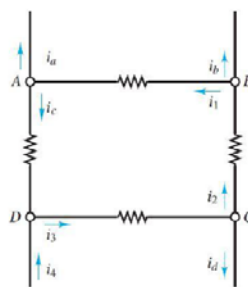


Figure P2.17

c) Use KCL at Node C.

$$i_3 - i_2 - i_d = 0$$

$$i_3 = i_2 + i_d$$

$$i_3 = 1A$$

d) Use KCL at Node D.

$$i_c + i_4 - i_3 = 0$$


$$i_4 = i_3 - i_c$$

$$i_4 = 0A$$

## <3>
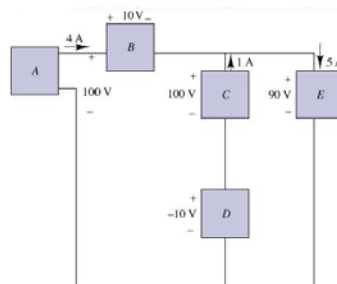
### Problem 2.24

For the circuit shown in Figure P2.24, determine which components are supplying power and which are dissipating power. Also determine the amount of power dissipated and supplied.



**Solution:**

**Known quantities:**

Circuit shown in Figure P2.24.

**Find:**

Determine power absorbed or power delivered and corresponding amount.

**Analysis:**

If current direction is out of power source, then power source is supplying, otherwise it is absorbing.

A supplies  $(100V)(4A) = 400W$

B absorbs  $(10V)(4A) = 40W$

C supplies  $(100V)(1A) = 100W$

D supplies  $(-10V)(1A) = -10W$ , i.e. absorbs  $10W$

E absorbs  $(90V)(5A) = 450W$

## <4>

**Find:**

- Equivalent resistance
- Power delivered.

**Analysis:**

(a)

$$2\Omega + 1\Omega = 3\Omega$$

$$3\Omega \parallel 3\Omega = 1.5\Omega$$

$$4\Omega + 1.5\Omega + 5\Omega = 10.5\Omega$$

$$10.5\Omega \parallel 6\Omega = 3.818\Omega$$

$$R_{eq} = 3.818\Omega + 7\Omega = 10.818\Omega$$

(b)

$$P = \frac{14^2}{10.818} = 18.12W$$

<5>

**Solution:**

**Known quantities:**

Circuit of Figure P2.59.  $R_1=10\Omega$ ,  $R_2=5\Omega$ ,  $R_3=8\Omega$ ,  
 $R_4=2\Omega$ ,  $R_5=4\Omega$ ,  $R_6=2\Omega$ ,  $R_7=1\Omega$ ,  $R_8=10\Omega$   $v_s=20V$ .

**Find:**

The equivalent resistance seen by the voltage source.  
 The current through  $R_7$ .

**Analysis:**

Count the nodes:

$$\text{Nodes} = 4$$

Nodes A, B, C, & D as shown above.

Combine  $R_1$  and  $R_2$ :

$$R_1 || R_2 = 3.33\Omega$$

$R_4, R_5, R_6$  are in parallel with each other and in series with  $R_1 || R_2$ :

$$R_4 || R_5 || R_6 + R_1 || R_2 = 4.13\Omega$$

The previous resistance is in parallel with  $R_3$ :

$$R_3 || 4.13\Omega = 2.72\Omega$$

$R_7$  is in parallel with  $R_8$ :

$$R_8 || R_7 = 0.91\Omega$$

These last two resistances are in series and are equal to the equivalent resistance:

$$R_{eq} = 3.63\Omega$$

The current through  $R_7 || R_8$  will be the same as the total current through the circuit. Find the total current then use current division to find the current through  $R_7$ :

$$I = \frac{v_s}{R_{eq}} = 5.51A$$

$$I_{R_7} = I * \frac{R_8}{R_7 + R_8} = 5.01A$$

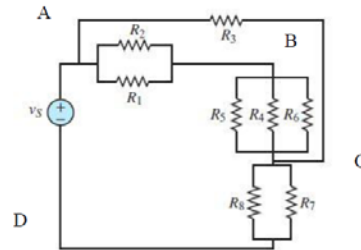


Figure P2.59