

## Electrical Engineering

### HW 3 – Chapter 4, Solution

#### <1>

a)

$$i_C(t) = C \frac{dv_C(t)}{dt} = 200 \times 10^{-6} \frac{dv_C(t)}{dt} = 2 \cdot 10^{-4} \frac{dv_C(t)}{dt} = 0.088 \cos(20t + \frac{\pi}{6}) A$$

b)

$$i_C(t) = -40 \cdot 200 \cdot 10^{-6} \cdot 90 \cdot \cos(90t + \pi/2) A = -0.72 \cos(90t + \pi/2 - \pi) A = 0.72 \cos(90t - \pi/2) A$$


c)

$$i_C(t) = 200 \cdot 10^{-6} \cdot 28 \cdot 15 \left[ -\sin\left(15t + \frac{\pi}{8}\right) \right] = -8.4 \cdot 10^{-2} \sin\left(15t + \frac{\pi}{8}\right) A$$

d)

$$i_C(t) = 200 \cdot 10^{-6} \cdot 45 \cdot 120 \left[ \cos\left(120t + \frac{\pi}{4}\right) \right] = 1.08 \cdot \cos\left(120t + \frac{\pi}{4}\right) A$$

#### <2>

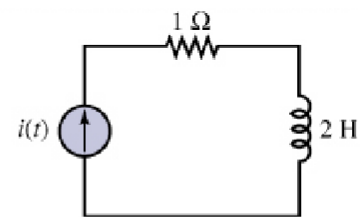

The magnetic energy stored in an inductor may be found from, (Eq. 4.16):

$$w_L(t) = \frac{1}{2} L i(t)^2 = \frac{1}{2} (2) i^2(t) = i^2(t)$$

For  $-\infty < t < 0$ ,


$$w_L(t) = 0$$

For  $0 \leq t < 10 \text{ s}$

$$w_L(t) = t^2 \text{ J}$$

For  $10 \text{ s} \leq t < +\infty$

$$w_L(t) = 100 \text{ J}$$

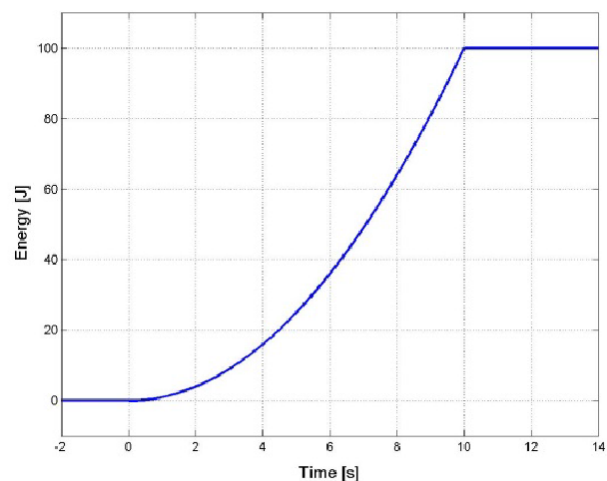

### <3>

Since the voltage waveform is piecewise continuous, the integration can be performed over each continuous segment. Where not indicated  $t$  is supposed to be expressed in seconds.

$$\begin{aligned}
 i_L(t = 30 \mu s) &= \frac{1}{L} \int_{-\infty}^{30 \mu s} v_L(\tau) d\tau = i_L(0) + \frac{1}{L} \int_0^{20 \mu s} v_L(\tau) d\tau + \frac{1}{L} \int_{20 \mu s}^{30 \mu s} v_L(\tau) d\tau = \\
 &= i_L(0) + \frac{1}{L} \left[ \frac{3}{3} \tau^3 \frac{V}{s^2} \right]_0^{20 \mu s} + \frac{1}{L} [1.2 \tau \text{ nV}]_{20 \mu s}^{30 \mu s} = 0 + \frac{1}{16 \mu H} \cdot 1 \frac{V}{s^2} \cdot ((20 \mu s)^3 - 0) + \\
 &+ \frac{1}{16 \mu H} \cdot (1.2 \text{ nV}) \cdot (30 \mu s - 20 \mu s) = 1.250 \text{ nA}
 \end{aligned}$$

### <4>

#### Analysis:

The first step is to redraw the circuit and place a break where there is a capacitor and a wire where there is an inductor.

The circuit can be simplified to find the Req and total current:

$$R_{eq} = 4.66 \text{ Ohms}$$

$$I_t = \frac{6}{4.66} = 1.29 A$$

There is no current through R3, therefore, the 2F and the 3F capacitor have the same voltage across them. This can be found by calculating the voltage drop across R1:

$$\begin{aligned}
 \frac{6 - V_1}{2} &= 1.29 A \\
 V_1 &= 3.43 V
 \end{aligned}$$

Plug this voltage into the equation for energy storage in a capacitor to get the energy stored in the 2F and the 3F capacitor:

$$\begin{aligned}
 W_{C2F} &= \frac{1}{2} * 2F * (3.43V)^2 = 11.76J \\
 W_{C3F} &= \frac{1}{2} * 3F * (3.43V)^2 = 17.63J
 \end{aligned}$$

The 1F capacitor is connected to the same node with both of its leads. This means there is no voltage across it and that its energy stored is:



$$W_{C1F} = 0$$

The inductor requires the use of current division to find the current through the 8 Ohm resistor:

$$I_8 = \frac{R_2}{R_2 + R_4} * I_t = 0.43 A$$

This current is also the current through the inductor. Plug it into the energy storage of an inductor equation:
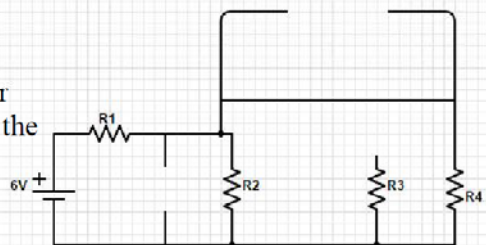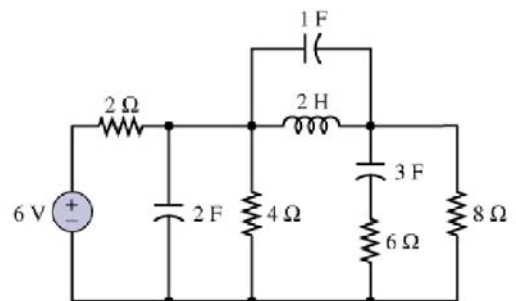
$$W_{L2H} = \frac{1}{2} * 2H * (0.43A)^2 = 0.18$$



<5>

a)  $V(j\omega) = 155\angle -25^\circ \text{ V}$

b)  $V(j\omega) = 5\angle -130^\circ \text{ V}$

c)  $I(j\omega) = 10\angle 63^\circ + 15\angle -42^\circ = (4.54 + j8.91) + (11.15 - j10.04) = 15.69 - j1.13 = 15.73\angle -4.12^\circ \text{ A}$

d)  $I(j\omega) = 460\angle -25^\circ - 220\angle 75^\circ = (416.90 - j194.40) - (56.94 - j212.50) = 359.96 + j18.10 = 360.4\angle 2.88^\circ \text{ A}$

<6>

$$X_L = \omega L = 800\Omega \Rightarrow Z_L = +j \cdot X_L = +j \cdot 800\Omega$$

$$X_C = \frac{1}{\omega C} = 3571\Omega \Rightarrow Z_C = -j \cdot X_C = -j \cdot 3571\Omega$$

$$Z_{eq1} = Z_{R2} + Z_L = R_2 + jX_L = 500 + j \cdot 800\Omega = 943.4\angle 60^\circ\Omega$$

$$Z_{eq2} = \frac{Z_{eq1} \cdot R_1}{Z_{eq1} + R_1} = 440 + j219.8$$

$$Z_{eq} = \frac{Z_{eq2} \cdot Z_C}{Z_{eq2} + Z_C} = 540.9\angle 198.8^\circ$$

<7>

$$X_L = 8\Omega, X_C = 16\Omega$$

$$R_2 \parallel C \Rightarrow Z_{eq1} = \frac{Z_{R2} \cdot Z_C}{Z_{R2} + Z_C} = 8 - j8$$

$$Z_{eq2} = Z_{eq1} + Z_L = 8$$

Using divider current law:

$$\overline{I_L} = \overline{I} \cdot \frac{Z_{R1}}{Z_{R1} + Z_{eq2}} = 20 \frac{8}{8+8} = 10$$

$$\overline{V_{R2}} = \overline{I_L} Z_{eq1} = 80 - j80 \Rightarrow V_{R2}(t) = 113.13 \cdot \cos(533.33t - 0.79)$$

<8>

$$a) \quad Z_L = j\omega L = j1000 \frac{\text{rad}}{\text{s}} \cdot 10 \text{ mH} = j10 \Omega,$$

The equivalent impedance is:

$$Z_T = \frac{Z_L \cdot R}{(Z_L + R)} + R_S = \frac{(j10)1000}{j10 + 1000} + 500 = 500 + \frac{j10^3}{100 + j} = 500.1 + j9.999 \Omega$$

The equivalent Thévenin voltage is:  $V_T = V_S = 10 \angle 0^\circ \text{ V}$

$$b) \quad Z_L = j\omega L = j10^6 \frac{\text{rad}}{\text{s}} \cdot 10 \text{ mH} = j10^4 \Omega,$$

The equivalent impedance is:

$$Z_T = \frac{Z_L \cdot R}{(Z_L + R)} + R_S = \frac{(j10^4)1000}{j10^4 + 1000} + 500 = 500 + \frac{j10^4}{1 + j10} = 1490.1 + j99.01 \Omega$$

The equivalent Thévenin voltage is:  $V_T = V_S = 10 \angle 0^\circ \text{ V}$

<9>

$$Z_C = \frac{1}{j\omega C} = \frac{-j}{300 \cdot 900 \cdot 10^{-6}} = -j3.7 \Omega,$$

$$Z_L = j\omega L = j300 \cdot 0.3 = j90 \Omega$$

Applying KCL at node 1, we have:

$$-I + \frac{V_2}{R_1} + \frac{V_2 - V_1}{R_2} + \frac{V_2 - V_1}{Z_C} = 0$$

Applying KCL at node 2, we have

$$\frac{V_1 - V_2}{R_2} + \frac{V_1}{Z_L} + \frac{V_1 - V_2}{Z_C} + \frac{V_1 - V}{R_3} = 0$$

Therefore, solving the linear system :

$$\begin{cases} V_1 = 4.25e^{j42.91} \Rightarrow v_1(t) = 4.25 \cos(300t + 42.91^\circ) \text{ V} \\ V_2 = 2.94e^{j57.27} \Rightarrow v_2(t) = 2.94 \cos(300t + 57.37^\circ) \text{ V} \end{cases}$$

