

# Electrical Engineering

## HW 3 – Chapter 4

### <1>

**4.2** For each case shown below, derive the expression for the current through a  $200\text{-}\mu\text{F}$  capacitor.  $v_C(t)$  is the voltage across the capacitor.


- $v_C(t) = 22 \cos(20t - \frac{\pi}{3}) \text{ V}$
- $v_C(t) = -40 \cos(90t + \frac{\pi}{2}) \text{ V}$
- $v_C(t) = 28 \cos(15t + \frac{\pi}{8}) \text{ V}$
- $v_C(t) = 45 \cos(120t + \frac{\pi}{4}) \text{ V}$

### <2>

**4.4** In the circuit shown in Figure P4.4, assume  $R = 1 \Omega$  and  $L = 2 \text{ H}$ . Also, let:

$$i(t) = \begin{cases} 0 & -\infty < t < 0 \\ t & 0 \leq t < 10 \text{ s} \\ 10 & 10 \text{ s} \leq t < \infty \end{cases}$$

Find the energy stored in the inductor for all time.

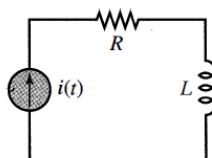


**Figure P4.4**

### <3>

**4.14** The current through a  $16\text{-}\mu\text{H}$  inductor is zero at  $t = 0$ , and the voltage across the inductor (shown in Figure P4.14) is:

$$v(t) = \begin{cases} 0 & t \leq 0 \\ 3t^2 & 0 \leq t \leq 20 \mu\text{s} \\ 1.2 \text{ nV} & t \geq 20 \mu\text{s} \end{cases}$$


Determine the current through the inductor at  $t = 30 \mu\text{s}$ .

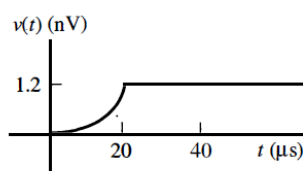

**Figure P4.14**

### <4>

**4.35** Assume steady-state conditions and find the energy stored in each capacitor and inductor shown in Figure P4.35.

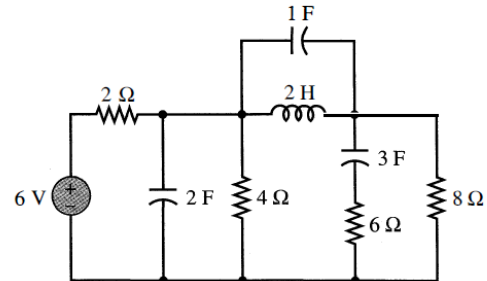

**Figure P4.35**

### <5>


**4.37** Find the phasor form of the following functions:

- $v(t) = 155 \cos(377t - 25^\circ) \text{ V}$
- $v(t) = 5 \sin(1,000t - 40^\circ) \text{ V}$
- $i(t) = 10 \cos(10t + 63^\circ) + 15 \cos(10t - 42^\circ) \text{ A}$
- $i(t) = 460 \cos(500\pi t - 25^\circ) - 220 \sin(500\pi t + 15^\circ) \text{ A}$

### <6>

**4.47** Determine the equivalent impedance seen by the source  $v_S$  in Figure P4.47 when:

$$\begin{aligned} v_S(t) &= 10 \cos(4,000t + 60^\circ) \text{ V} \\ R_1 &= 800 \text{ m}\Omega, \quad R_2 = 500 \text{ n}\Omega \\ L &= 200 \text{ mH} \quad C = 70 \text{ nF} \end{aligned}$$

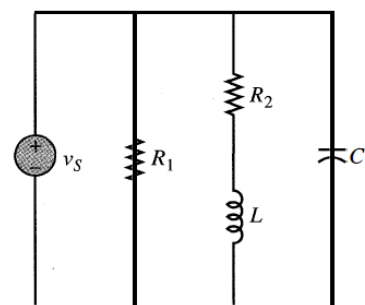

**Figure P4.47**


&lt;7&gt;

**4.51** Determine the voltage  $v_2(t)$  across  $R_2$  in the circuit of Figure P4.51.

$$i(t) = 20 \cos(533.33t) \text{ A}$$

$$R_1 = 8 \, \Omega \quad R_2 = 16 \, \Omega$$

$$L = 15 \text{ mH} \quad C = 117 \, \mu\text{F}$$

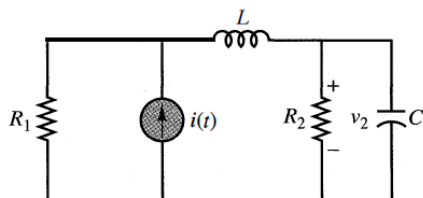

**Figure P4.51**


&lt;8&gt;

**4.70** Determine the Thévenin equivalent network seen by the load  $R_o$  in Figure P4.70. Assume:

$$R_S = R_o = 500 \, \Omega \quad L = 10 \text{ mH} \quad R = 1 \text{ k}\Omega$$

and:

- $v_S(t) = 10 \cos(1,000t)$
- $v_S(t) = 10 \cos(1,000,000t)$

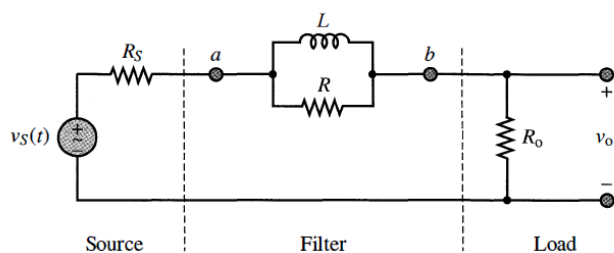

**Figure P4.70**

&lt;9&gt;


**4.74** Use nodal analysis to determine the node voltages  $v_a(t)$  and  $v_b(t)$  shown in Figure P4.74. Assume:

$$i(t) = 2 \cos(300t) \text{ A}$$

$$v(t) = 7 \cos(300t + \pi/4) \text{ V}$$

$$R_1 = 4 \, \Omega \quad R_2 = 3 \, \Omega \quad R_3 = 5 \, \Omega$$

$$L = 300 \text{ mH} \quad C = 300 \, \mu\text{F}$$

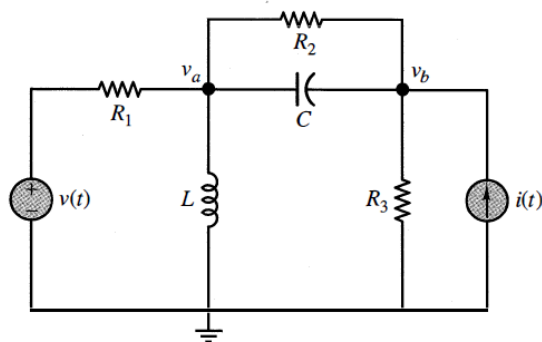

**Figure P4.74**