




## Finite State Machines

- Design methodology for sequential logic
  - identify distinct states
  - create state transition diagram
  - choose state encoding
  - write combinational Verilog for next-state logic
  - write combinational Verilog for output signals
- Lots of examples

Reminder: Lab #2 due tonight!
 
## Finite State Machines


- Finite State Machines (FSMs) are a useful abstraction for **sequential circuits** with centralized "**states**" of operation
- At each clock edge, combinational logic computes **outputs** and **next state** as a function of **inputs** and **present state**




## Two Types of FSMs

Moore and Mealy FSMs : different output generation

### Moore FSM:

 


### Mealy FSM:

 

 
## Design Example: Level-to-Pulse

- A **level-to-pulse converter** produces a single-cycle pulse each time its input goes high.
- It's a synchronous rising-edge detector.
- Sample uses:
  - Buttons and switches pressed by humans for arbitrary periods of time
  - Single-cycle enable signals for counters




## Step 1: State Transition Diagram


- Block diagram of desired system:

 

 - State transition diagram** is a useful FSM representation and design aid:



## Valid State Transition Diagrams

 

- Arcs leaving a state are **mutually exclusive**, i.e., for any combination input values there's at most one applicable arc
- Arcs leaving a state are **collectively exhaustive**, i.e., for any combination of input values there's at least one applicable arc
- So for each state: for any combination of input values there's exactly one applicable arc
- Often a starting state is specified
- Each state specifies values for all outputs (Moore)

## Choosing State Representation

### Choice #1: **binary encoding**


For  $N$  states, use  $\text{ceil}(\log_2 N)$  bits to encode the state with each state represented by a unique combination of the bits. Tradeoffs: most efficient use of state registers, but requires more complicated combinational logic to detect when in a particular state.

### Choice #2: **"one-hot" encoding**

For  $N$  states, use  $N$  bits to encode the state where the bit corresponding to the current state is 1, all the others 0. Tradeoffs: more state registers, but often much less combinational logic since state decoding is trivial.

 
## Step 2: Logic Derivation

Transition diagram is readily converted to a state transition table (just a truth table)




Current State		In	Next State		Out
$S_1$	$S_0$	$L$	$S_1^+$	$S_0^+$	$P$
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	1
1	1	0	0	0	0
1	1	1	1	1	0

 
- Combinational logic may be derived using Karnaugh maps




## Moore Level-to-Pulse Converter

 

 
Moore FSM circuit implementation of level-to-pulse converter:




## Design of a Mealy Level-to-Pulse

 

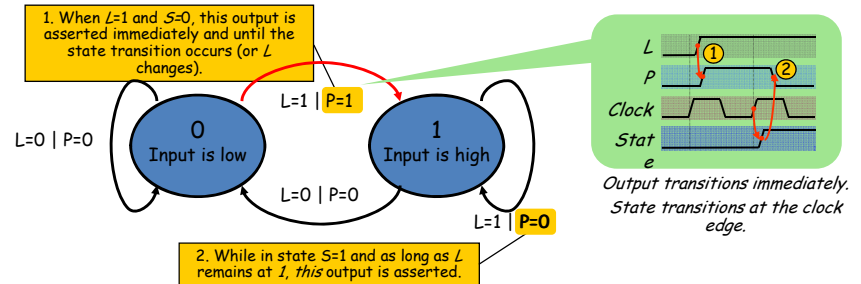- Since outputs are determined by state *and* inputs, Mealy FSMs may need fewer states than Moore FSM implementations




## Mealy Level-to-Pulse Converter

 

Pres. State	In	Next State	Out
S	L	S*	P
0	0	0	0
0	1	1	1
1	0	0	0
1	1	1	0

 Mealy FSM circuit implementation of level-to-pulse converter:




- FSM's state simply remembers the previous value of L
- Circuit benefits from the Mealy FSM's implicit single-cycle assertion of outputs during state transitions


## Moore/Mealy Trade-Offs

- How are they different?
  - Moore: **outputs = f( state )** only
  - Mealy **outputs = f( state and input )**
  - Mealy outputs generally occur one cycle earlier than a Moore:

Moore: delayed assertion of P

 

Mealy: immediate assertion of P

 

- Compared to a Moore FSM, a Mealy FSM might...
  - Be more difficult to conceptualize and design
  - Have fewer states

## Example: Intersection Traffic Lights

- Design a controller for the traffic lights at the intersection of two streets - two sets of traffic lights, one for each of the streets.
- Step 1: Draw starting state transition diagram. Just handle the usual green-yellow-red cycle for both streets. How many states? Well, how many different combinations of the two sets of lights are needed?
- Step 2: add support for a walk button and walk lights to your state transition diagram.
- Step 3: add support for a traffic sensor for each of the streets - when the sensor detects traffic the green cycle for that street is extended.

Example to be worked collaboratively on the board...

## FSM Example

### GOAL:


Build an electronic combination lock with a reset button, two number buttons (0 and 1), and an unlock output. The combination should be **01011**.




### STEPS:

1. Design lock FSM (block diagram, state transitions)
2. Write Verilog module(s) for FSM

## Step 1A: Block Diagram

 

## Step 1B: State transition diagram

 

## Step 2: Write Verilog

```
module lock(input clk,reset_in,b0_in,b1_in,
            output out);
```

```
// synchronize push buttons, convert to pulses
```

```
// implement state transition diagram
reg [2:0] state,next_state;
always @(*) begin
    // combinational logic!
    next_state = ???;
end
always @(posedge clk) state <= next_state;
```


```
// generate output
assign out = ???;
```

```
// debugging?
endmodule
```
 
## Step 2A: Synchronize buttons

```
// button
// push button synchronizer and level-to-pulse converter
// OUT goes high for one cycle of CLK whenever IN makes a
// low-to-high transition.
```

```
module button(
    input clk,in,
    output out
);
    reg r1,r2,r3;
    always @(posedge clk)
    begin
        r1 <= in; // first reg in synchronizer
        r2 <= r1; // second reg in synchronizer, output is in sync!
        r3 <= r2; // remembers previous state of button
    end
```




```
// rising edge = old value is 0, new value is 1
assign out = ~r3 & r2;
endmodule
```
 
## Step 2B: state transition diagram

```
parameter S_RESET = 0; // state assignments
parameter S_0 = 1;
parameter S_01 = 2;
parameter S_010 = 3;
parameter S_0101 = 4;
parameter S_01011 = 5;
```

```
reg [2:0] state, next_state;
always @(*) begin
    // implement state transition diagram
    if (reset) next_state = S_RESET;
    else case (state)
        S_RESET: next_state = b0 ? S_0 : b1 ? S_RESET : state;
        S_0: next_state = b0 ? S_0 : b1 ? S_01 : state;
        S_01: next_state = b0 ? S_010 : b1 ? S_RESET : state;
        S_010: next_state = b0 ? S_0 : b1 ? S_0101 : state;
        S_0101: next_state = b0 ? S_010 : b1 ? S_01011 : state;
        S_01011: next_state = b0 ? S_0 : b1 ? S_RESET : state;
        default: next_state = S_RESET; // handle unused states
    endcase
end
```



```
always @(posedge clk) state <= next_state;
```

## Step 2C: generate output

```
// it's a Moore machine! Output only depends on current state
```

```
assign out = (state == S_01011);
```

## Step 2D: debugging?

```
// hmmm. What would be useful to know? Current state?
```

```
assign hex_display = {1'b0,state[2:0]};
```

## Step 2: final Verilog implementation

```

module lock(input clk,reset_in,b0_in,b1_in,
            output out, output [3:0] hex_display);

    wire reset, b0, b1; // synchronize push buttons, convert to pulses
    button b_reset(clk,reset_in,reset);
    button b_0(clk,b0_in,b0);
    button b_1(clk,b1_in,b1);

    parameter S_RESET = 0; parameter S_0 = 1; // state assignments
    parameter S_01 = 2; parameter S_010 = 3;
    parameter S_0101 = 4; parameter S_01011 = 5;

    reg [2:0] state,next_state;
    always @(*) begin // implement state transition diagram
        if (reset) next_state = S_RESET;
        else case (state)
            S_RESET: next_state = b0 ? S_0 : b1 ? S_RESET : state;
            S_0: next_state = b0 ? S_0 : b1 ? S_01 : state;
            S_01: next_state = b0 ? S_010 : b1 ? S_RESET : state;
            S_010: next_state = b0 ? S_0 : b1 ? S_0101 : state;
            S_0101: next_state = b0 ? S_010 : b1 ? S_01011 : state;
            S_01011: next_state = b0 ? S_0 : b1 ? S_RESET : state;
            default: next_state = S_RESET; // handle unused states
        endcase
    end
    always @ (posedge clk) state <= next_state;

    assign out = (state == S_01011); // assign output: Moore machine
    assign hex_display = {1'b0,state}; // debugging
endmodule

```

## Where should CLK come from?

- Option 1: external crystal
  - Stable, known frequency, typically 50% duty cycle
- Option 2: internal signals
  - Option 2A: output of combinational logic



- No! If inputs to logic change, output may make several transitions before settling to final value → several rising edges, not just one! Hard to design away output glitches...
- Option 2B: output of a register
  - Okay, but timing of CLK2 won't line up with CLK1

