

Electrical Engineering

HW 4 – Chapter 5

<1>

- 5.23** Determine the current i_C through the capacitor just before and just after the switch is closed in Figure P5.23. Assume steady-state conditions for $t < 0$. $V_1 = 15 \text{ V}$, $R_1 = 0.5 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$, and $C = 0.4 \mu\text{F}$.

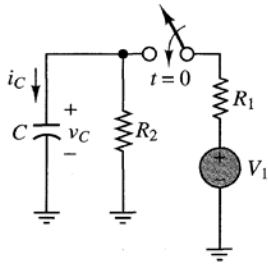


Figure P5.23

<2>

- 5.32** Determine the voltage v_C across the capacitor shown in Figure P5.32 for $t > 0$. The voltage across the capacitor just before the switch is thrown is $v_C(0^-) = -7 \text{ V}$. Assume:

$$I_o = 17 \text{ mA} \quad C = 0.55 \mu\text{F}$$

$$R_1 = 7 \text{ k}\Omega \quad R_2 = 3.3 \text{ k}\Omega$$

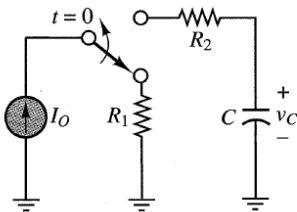


Figure P5.32

(Hint: the source is current source not voltage source)

<3>

- 5.33** For $t < 0$, the circuit shown in Figure P5.29 is at steady state. The switch is thrown at $t = 0$. Determine the current i_L through the inductor for $t > 0$. Assume:

$$V_{S1} = 9 \text{ V} \quad V_{S2} = 12 \text{ V}$$

$$L = 120 \text{ mH} \quad R_1 = 2.2 \Omega$$

$$R_2 = 4.7 \Omega \quad R_3 = 18 \text{ k}\Omega$$

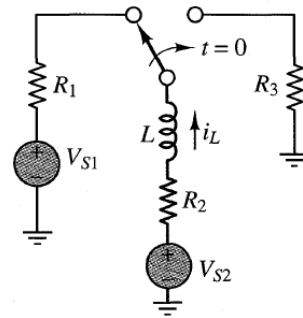


Figure P5.29

<4>

- 5.37** Determine the current i_C through the capacitor in Figure P5.37 for all time. Assume DC steady-state conditions for $t < 0$. Also assume: $V_1 = 10 \text{ V}$, $C = 200 \mu\text{F}$, $R_1 = 300 \text{ m}\Omega$, and $R_2 = R_3 = 1.2 \text{ k}\Omega$.

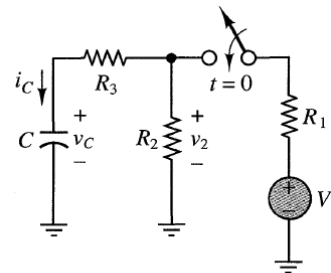


Figure P5.37

<5>

- 5.61** In the circuit shown in Figure P5.61:

$$V_{S1} = 15 \text{ V} \quad V_{S2} = 9 \text{ V}$$

$$R_{S1} = 130 \Omega \quad R_{S2} = 290 \Omega$$

$$R_1 = 1.1 \text{ k}\Omega \quad R_2 = 700 \Omega$$

$$L = 17 \text{ mH} \quad C = 0.35 \mu\text{F}$$

Assume that DC steady-state conditions exist for $t < 0$. Determine the voltage v_C across the capacitor and the current i_L through the inductor as $t \rightarrow \infty$.

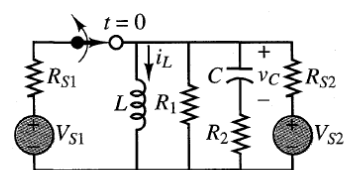


Figure P5.61

Problem <6>~<8> are regarding the second order system. Some circuits change their connections when $t > 0$ (so you may be confused when you derive a differential equation). When you derive a second-order differential equation, consider the circuit only for $t > 0$. The circuit condition for $t < 0$ is only used to calculate the initial condition of the circuit.

<6>

- 5.75** Determine i_L for $t > 0$ in Figure P5.75, assuming $i(0) = 2.5$ A and $v_C(0) = 10$ V.

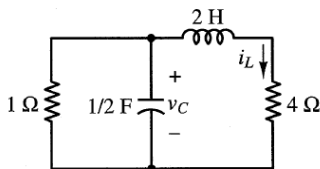


Figure P5.75

<7>

- 5.76** Find the maximum value of v_C for $t > 0$ in Figure P5.76, assuming DC steady state at $t = 0^-$.

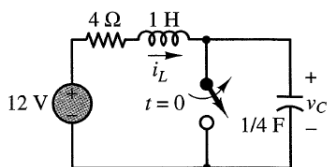


Figure P5.76

<8>

- 5.82** For $t > 0$, determine v in Figure P5.82, assuming DC steady state at $t = 0^-$.

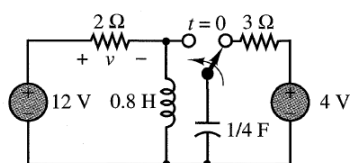


Figure P5.82