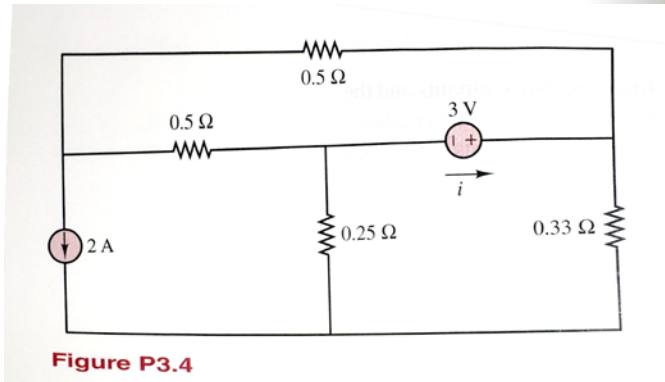


HW 2 – Chapter 3


<1>

3.4 Using node voltage analysis in the circuit of Figure P3.4, find the current i through the voltage source.




<2>

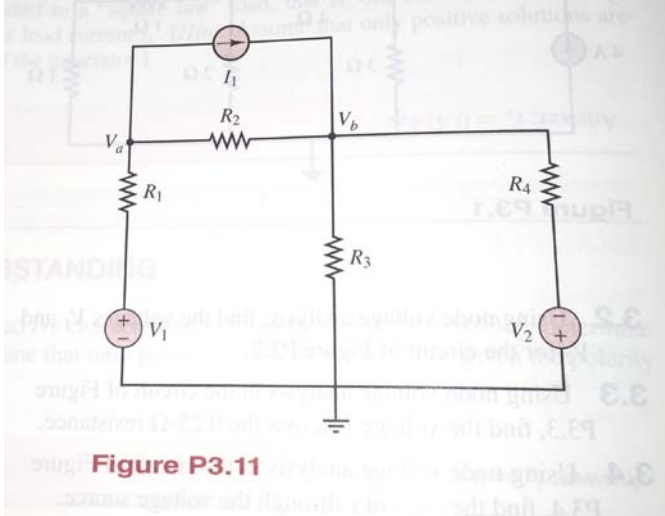3.11 Use nodal analysis in the circuit of Figure P3.11 to find V_a and V_b . Let $R_1 = 10\Omega$, $R_2 = 4\Omega$, $R_3 = 6\Omega$, $R_4 = 6\Omega$, $V_1 = 2\text{V}$, $V_2 = 4\text{V}$, $I_1 = 2\text{A}$.




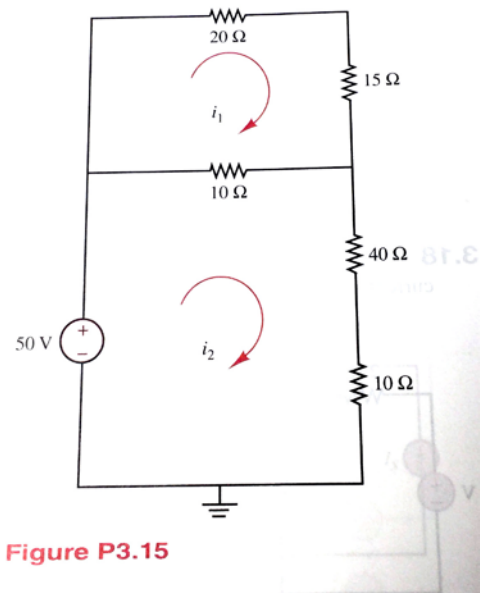3.15 Using mesh analysis, find the currents i_1 and i_2 and the voltage across the upper 10Ω resistor in the circuit of Figure P3.15.



<4>

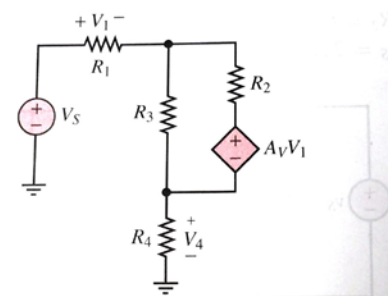3.24 Use nodal analysis on the circuit in Figure P3.24 to determine the voltage V_4 . Note that one source is a dependent (controlled) voltage source! Let $V_S = 5\text{V}$; $A_V = 70$; $R_1 = 2.2\text{k}\Omega$; $R_2 = 1.8\text{k}\Omega$; $R_3 = 6.8\text{k}\Omega$; $R_4 = 220\Omega$.



<5>

3.29 Use mesh analysis to find mesh currents in Figure P3.29. Let $R_1 = 8\ \Omega$, $R_2 = 3\ \Omega$, $R_3 = 5\ \Omega$, $R_4 = 2\ \Omega$, $R_5 = 4\ \Omega$, $R_6 = 3\ \Omega$, $V_1 = 4\text{ V}$, $V_2 = 2\text{ V}$, $V_3 = 1\text{ V}$, $V_4 = 2\text{ V}$, $V_5 = 3\text{ V}$, $V_6 = 2\text{ V}$.

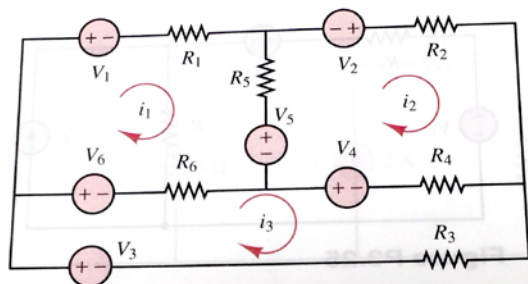


Figure P3.29

<8>

3.53 Find the Norton equivalent of the network seen by R_2 in Figure P3.53. Use it and current division to compute the current i through R_2 . Assume $I_1 = 10\text{ A}$, $I_2 = 2\text{ A}$, $V_1 = 6\text{ V}$, $R_1 = 3\ \Omega$, and $R_2 = 4\ \Omega$.

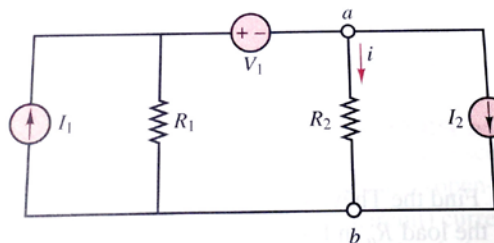


Figure P3.53

<6>

3.50 Use the principle of superposition to determine the current i_o through R_1 in Figure P3.50. Let $R_1 = 8\ \Omega$, $R_2 = 2\ \Omega$, $R_3 = 3\ \Omega$, $R_4 = 4\ \Omega$, $R_5 = 2\ \Omega$, $V_1 = 15\text{ V}$, $I_1 = 2\text{ A}$, $I_2 = 3\text{ A}$.

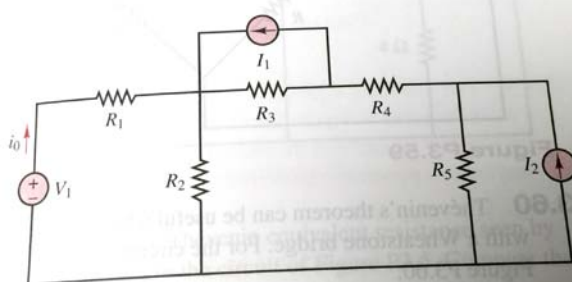


Figure P3.50

<9>

3.73 The Thévenin equivalent network seen by a load R_o is depicted in Figure P3.73. Assume $V_T = 10\text{ V}$, $R_T = 2\ \Omega$, and that the value of R_o is such that maximum power is transferred to it. Determine:

- The value of R_o .
- The power P_o dissipated by R_o .
- The efficiency (P_o/P_{V_T}) of the circuit.

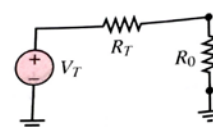


Figure P3.73

<7>

3.51 Find the Thévenin equivalent of the network seen by the $3\text{-}\Omega$ resistor in Figure P3.51.

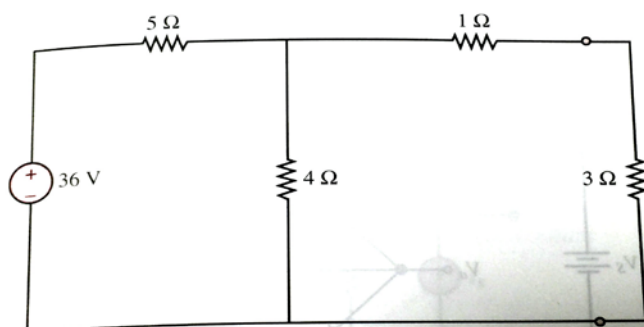


Figure P3.51