

# Electrical Engineering

## HW 1 – Chapter 2

<1>

- 2.13** Use KCL to determine the unknown currents in the circuit of Figure P2.13. Assume  $i_0 = 2$  A and  $i_2 = -7$  A.

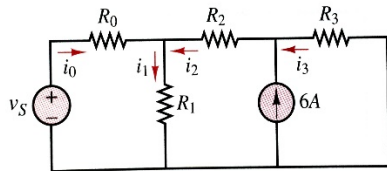


Figure P2.13

<2>

- 2.17** Use KCL to determine the current  $i_1$ ,  $i_2$ ,  $i_3$ , and  $i_4$  in the circuit of Figure P2.17. Assume that  $i_a = -2$  A,  $i_b = 6$  A,  $i_c = 1$  A and  $i_d = -4$  A.

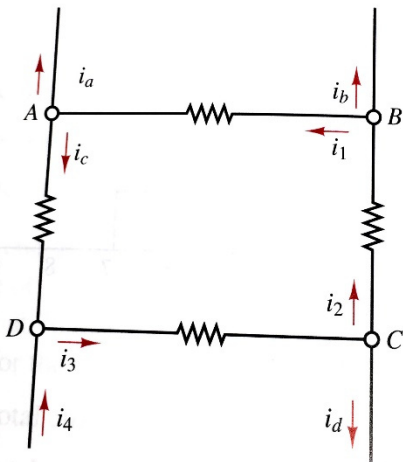


Figure P2.17

<3>

- 2.24** For the circuit shown in Figure P2.24, determine which components are supplying power and which are dissipating power. Also determine the amount of power dissipated and supplied.

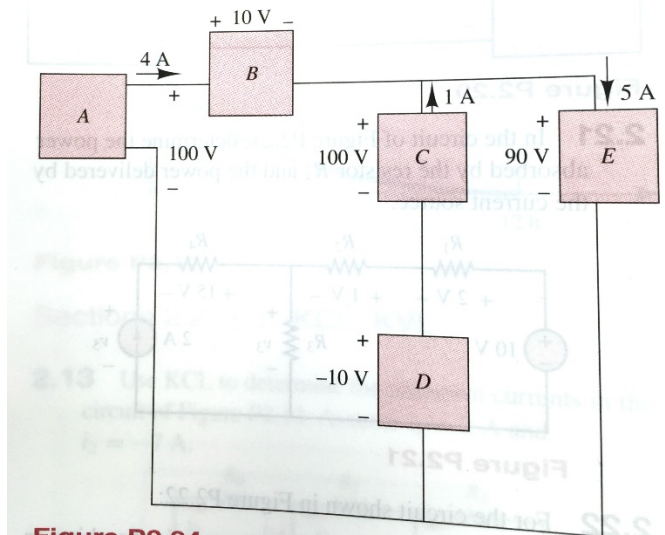


Figure P2.24

<4>

- 2.57** For the circuit shown in Figure P2.57, find the equivalent resistance seen by the source. How much power is delivered by the source?


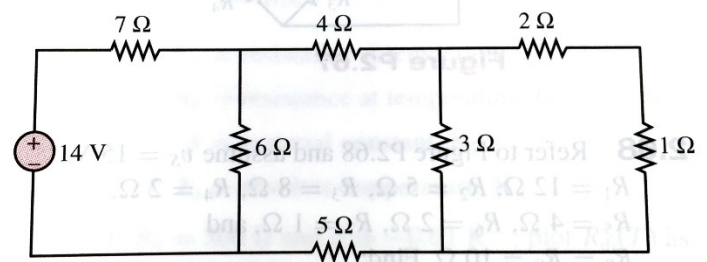


Figure P2.57

**2.59** Refer to Figure P2.59. Assume  $v_S = 20\text{ V}$ ,  $R_1 = 10\ \Omega$ ,  $R_2 = 5\ \Omega$ ,  $R_3 = 8\ \Omega$ ,  $R_4 = 2\ \Omega$ ,  $R_5 = 4\ \Omega$ ,  $R_6 = 2\ \Omega$ ,  $R_7 = 1\ \Omega$ , and  $R_8 = 10\ \Omega$ . How many nodes are in the circuit? Use KCL and Ohm's law to determine:

- The current in the resistor  $R_7$ .
- The equivalent resistance seen by the voltage source  $v_S$ .

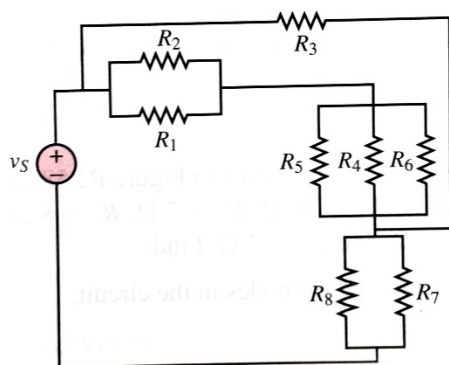

**Figure P2.59**