

# Machine Called Computer

## Part 2

- Invention of computer
- Digital Logic Design
- Notion of "Abstraction"

### References:

1. Computer Organization and Design & Computer Architecture, Hennessy and Patterson (slides are adapted from those by the authors)

# Big Picture

## ❑ 컴퓨터의 탄생

- 과학적 성취 (수학적 개념의 창조)
  - Boole in 19C
- 실용적 도구 개발 - 산업혁명의 맥
  - Automata (자동장치) 개발
  - 자동 계산기 (calculator) 개발
- 구현 기술 발전
  - Transistor 발명 (wheel/shaft/cam, relays, 진공관)

## ❑ Abstraction: fundamental engineering concept

# George Boole

❑ 19C English mathematician, philosopher, logician


❑ "The Laws of Thought" in 1854

- Proposition (명제)

  - Binary (True, False; "1", "0")

- AND, OR, NOT, IF

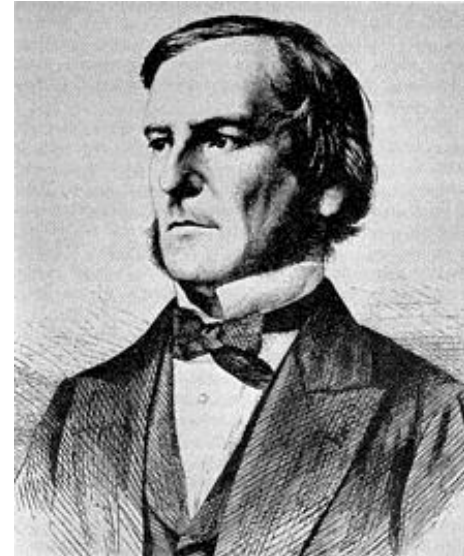- † To throw light on nature of human mind?



Public domain image

❑ Impact on computer science and mathematics

- Foundation of mathematical logic

  - vs. traditional logic (syllogism by Aristotle, B.C. 4C)

- Boolean Algebra

# Propositional Logic (명제논리학)

- Proposition: basic building block
  - Declarative sentence that is either true or false
    - 2014/10/25 is Monday,  $2 + 3 = 6$
    - $x + 3 = 5$ , what time is it?
- Compound propositions - apply recursively
  - p: 2014/10/25 is Monday, q:  $2 + 3 = 6$
  - $p \cdot q$  (AND operation)
  - $p + q$  (OR)
  - $\underline{p}$  (NOT; usually overline or bar)
  - $p \rightarrow q$  (IF)

# Truth Table

□ 1 = True; 0 = False

AND	p	q	$p \cdot q$
	1	1	1
	1	0	0
	0	1	0
	0	0	0

OR	p	q	$p + q$
	1	1	1
	1	0	1
	0	1	1
	0	0	0

NOT	p	$\bar{p}$
	1	0
	0	1


IF	p	q	$p \rightarrow q$
	1	1	1
	1	0	0
	0	1	1
	0	0	1

# In Your Mind - Digital Logic Gates

- Can implement AND, OR, NOT with electronic circuits

AND

p	q	$p \cdot q$
1	1	1
1	0	0
0	1	0
0	0	0


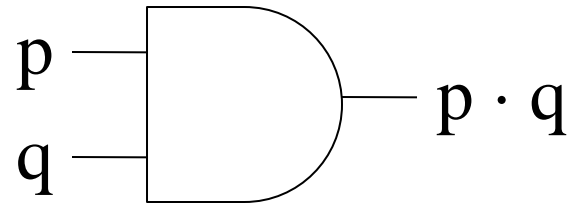


NOT

p	$\bar{p}$
1	0
0	1

OR

p	q	$p + q$
1	1	1
1	0	1
0	1	1
0	0	0

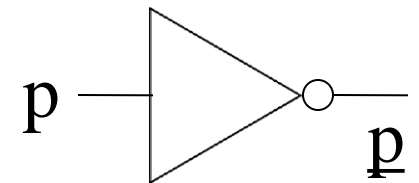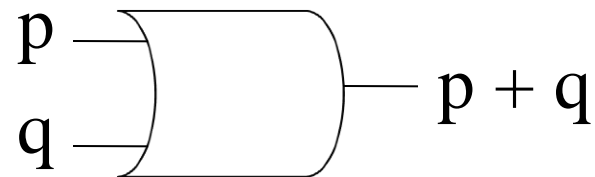

# Boolean Algebra (불 대수)

Set of values  $\{0, 1\}$

Set of operations: AND, OR, NOT

(복잡한 자동장치 설계 위한 수학적 기반 제공)

# Algebra

## □ Elementary algebra

- Use of letters and symbols to represent values and their relations, especially for solving equations

$$2 + 3 = 5$$

$$x^2 + 2x + 1 = 0$$

## □ Modern algebra (e.g., Boolean Algebra)

- Operations and relations that are defined on set of mathematical objects



# Boolean Algebra

## □ Operations and rules for working with the set $\{0, 1\}$

- Operation
  - AND, OR, NOT
- Boolean expression
  - $0, 1, x_1, x_2, \dots, x_n$  are Boolean expressions
  - If  $E_1$  and  $E_2$  are Boolean expressions, then  
 $\underline{E_1}, E_1 \cdot E_2, E_1 + E_2$  are Boolean expressions


† Compare with arithmetic expressions

† Why the name ALU (Arithmetic and Logic Unit)?

# Boolean Algebra

- Axioms  $\rightarrow$  Theorems (or knowledge)
- Given truth table, find Boolean expression for function?
  - $F = f(x,y,z)$

† Practical view

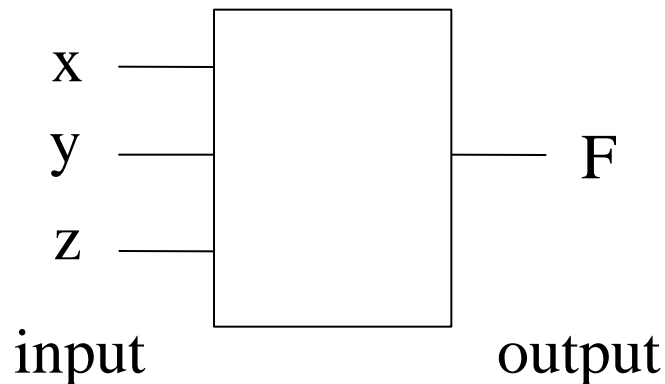


x	y	z	F
1	1	1	1
1	1	0	1
1	0	1	0
1	0	0	1
0	1	1	0
0	1	0	1
0	0	1	0
0	0	0	1

# Exercises - Boolean Expression

x	y	F
0	0	0
0	1	0
1	0	0
1	1	1

$$F = x \cdot y$$

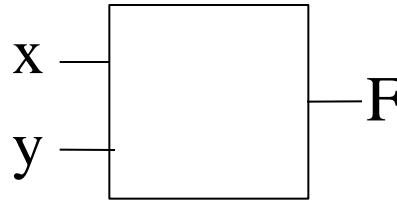

x	y	F
0	0	0
0	1	1
1	0	0
1	1	1

$$F = (x \cdot y) + (\underline{x} \cdot y)$$

Multiple outputs:

x	y	F1	F2
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

$$F1 = x + y$$

$$F2 = \underline{x} + y$$


# Boolean Algebra

## □ Theorems

## □ Given truth table, systematically find Boolean expression for F?

- $F = x \cdot y + \underline{z}$
- Simplest form?

## † Practical view

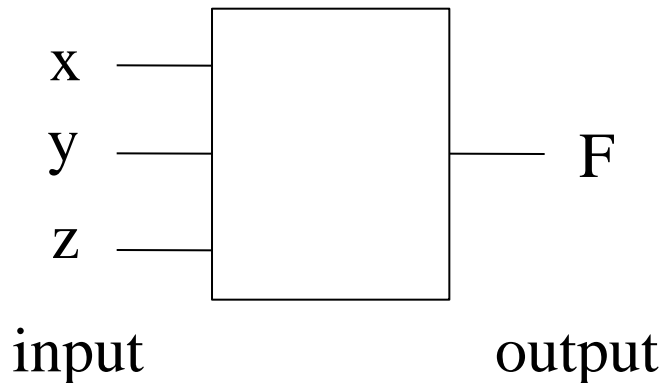


x	y	z	F
1	1	1	1
1	1	0	1
1	0	1	0
1	0	0	1
0	1	1	0
0	1	0	1
0	0	1	0
0	0	0	1

# Automata (자동장치) Design and Boolean Algebra

(복잡한 자동장치의 체계적 설계)
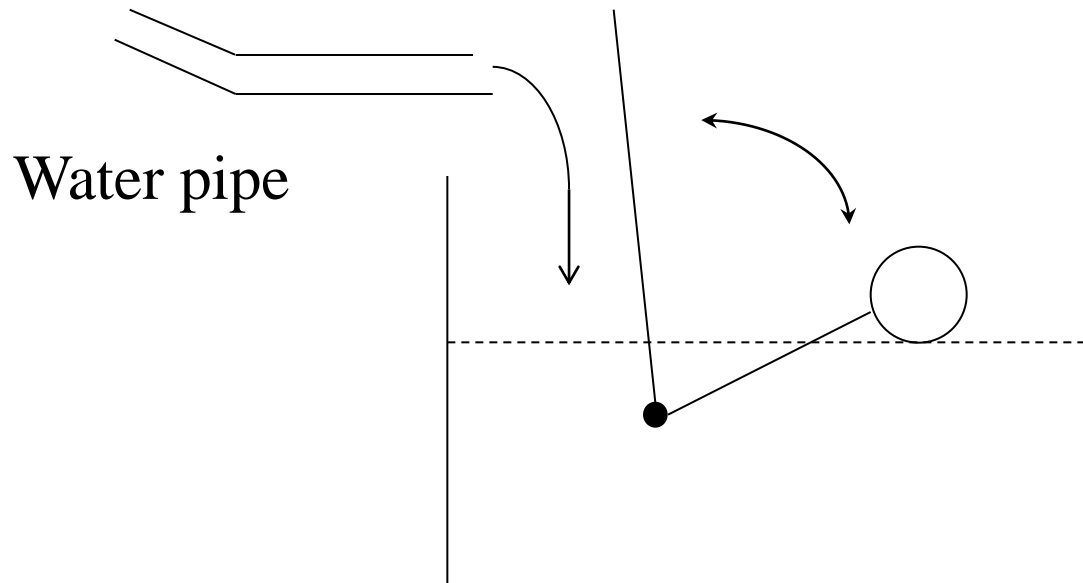
# Simple Automaton


- ❑ Self-operating machine (water-level controller)



- ❑ More useful/complex automata: "sensors" and "switches"
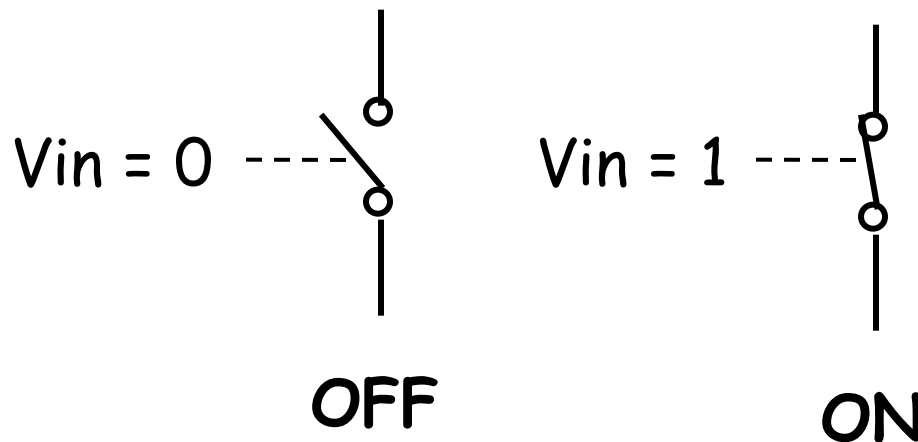
# Electronics and Digital Switch

- Need for three-terminal switching device
  - Control signal, flow between the remaining two
    - Digital switch (ON, OFF)
  - Mechanical, electromechanical, electronic



- High =  $2^V$  = "1" = True, Low =  $0^V$  = "0" = False

# Electro-Mechanical Relay

- ❑ Invented in 1835, switching speed: order of milliseconds

Image of electromagnetic relays:

<http://en.wikipedia.org/wiki/File:Relay.jpg>

Image of electromagnetic relays:

[http://en.wikipedia.org/wiki/File:Relay\\_symbols.svg](http://en.wikipedia.org/wiki/File:Relay_symbols.svg)



# Electron or Vacuum Tube

- ❑ Invented in 1906 (speed: order of microseconds)
- ❑ First commercial electron tube by RCA in 1920
  - Radio, TV, Audio, telephone networks, ENIAC

Image of electronic vacuum tubes:


<http://en.wikipedia.org/wiki/File:SE-300B-70W.jpg>

Image of electronic vacuum tubes:

[http://en.wikipedia.org/wiki/File:Triode\\_tube\\_schematic.svg](http://en.wikipedia.org/wiki/File:Triode_tube_schematic.svg)
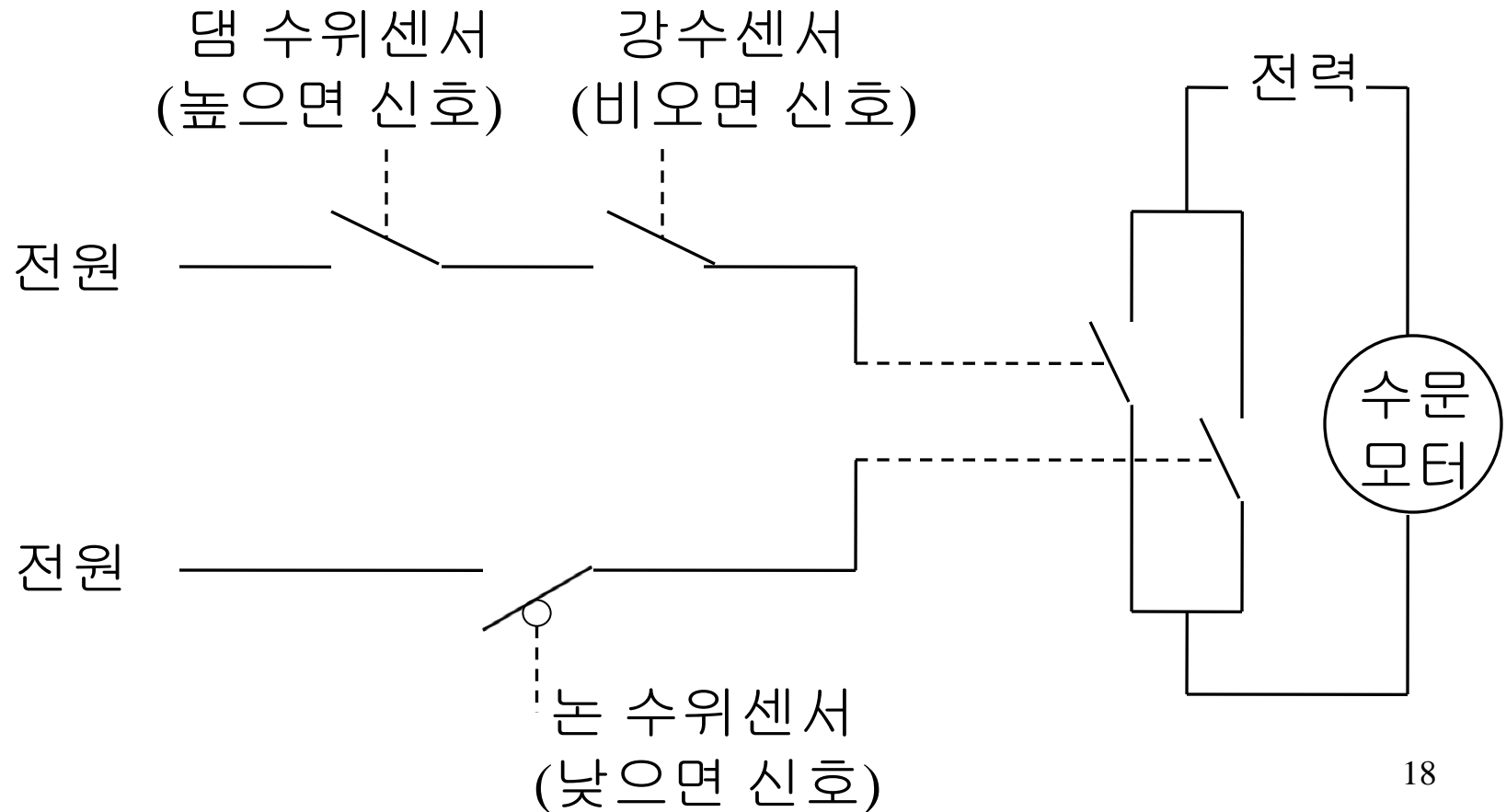
# More Meaningful Automaton

- ❑ Self-operating machine ("sensors" and digital "switches")



# Automata Design

## □ Real world example

- 댐 수위 높는데 비가 오면 수문 연다
- 또는 논에 물이 적으면 수문 연다

**x**: 댐의 수위가 높다

**y**: 비가 온다

**z**: 논에 물이 충분하다

**F**: 댐의 수문을 연다 (output)

## □ $F = x \cdot y + z$

- Simplest form?

Truth Table

x	y	z	F
1	1	1	1
1	1	0	1
1	0	1	0
1	0	0	1
0	1	1	0
0	1	0	1
0	0	1	0
0	0	0	1

# Digital Logic Design (Shannon, 1938)

## □ Real world example


- $x$ : 댐의 수위가 높다,  $y$ : 비가 온다,  $z$ : 논에 물이 충분하다
- $F$ : 댐의 수문을 연다

$x$	$y$	$z$	$F$
1	1	1	1
1	1	0	1
1	0	1	0
1	0	0	1
0	1	1	0
0	1	0	1
0	0	1	0
0	0	0	1

Truth Table

## □ $F = x \cdot y + \bar{z}$

- Simplest form?

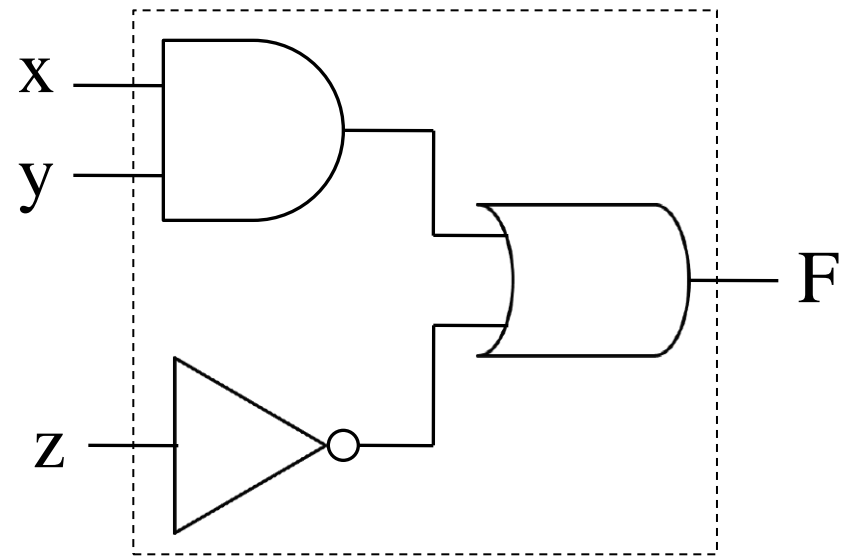

Logic Diagram

# Automata Design

- ❑ Empirical automata design
  - Ad hoc approach using 3-terminal digital switches
  - Underlying notion of AND, OR, NOT
- ❑ Relating automata design and Boolean Algebra
  - Shannon's M.S. Thesis in 1938
- ❑ Systematic design of automata
  - Think about inputs, outputs
  - Build truth table
  - Reduce to Boolean logic function
    - Readily be implemented with hardware
- ❑ Facilitate design automation (VLSI CAD tools)
  - Ultimate form of automata: ALU, processor, computer

# Digital Logic Design

## (Combinational Logic Design)

ALU: Complex Automaton

# Combinational Logic Design

## ❑ Combinational Logic

- Outputs completely determined by inputs

## ❑ Combinational logic design

- Given: AND, OR, NOT gates
- Paradigm
  - Determine input and output variables
  - Build truth table
  - Outputs: Boolean functions of input variables
    - † VLSI CAD tools


# Imagine ALU design

## □ 4-bit adder

- Input:  $a_3, a_2, a_1, a_0$ , and  $b_3, b_2, b_1, b_0$
- Output:  $F_3, F_2, F_1, F_0$

$$\begin{array}{r}
 9_{10} = 1\ 0\ 0\ 1 \\
 4_{10} = 0\ 1\ 0\ 0 \\
 \hline
 1\ 1\ 0\ 1 = 13_{10}
 \end{array}$$

$a_3$	$a_2$	$a_1$	$a_0$	
$b_3$	$b_2$	$b_1$	$b_0$	
$F_3$	$F_2$	$F_1$	$F_0$	

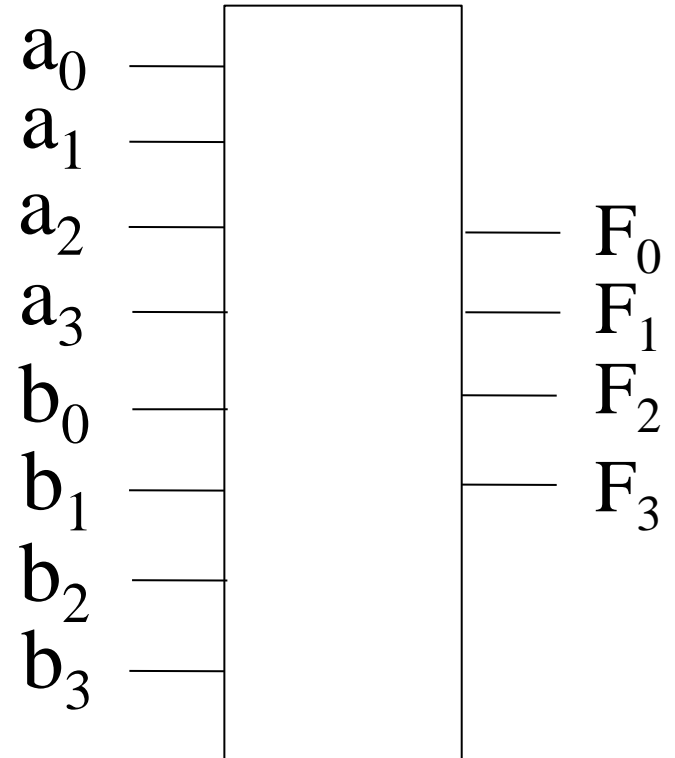




# 4-bit Adder

- ❑ Generate (large) truth table (with  $2^8$  rows)
- ❑ Find minimum Boolean expression
  - $F_3 = f(a_3, a_2, a_1, a_0, b_3, b_2, b_1, b_0)$ ,  $F_2 = \dots$ ,  $F_1 = \dots$ ,
- ❑ Implement  $F_3, F_2, F_1, F_0$

$a_3$	$a_2$	$a_1$	$a_0$	$b_3$	$b_2$	$b_1$	$b_0$	$F_3$	$F_2$	$F_1$	$F_0$
0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	1	0	0	0	1
1	0	0	1	0	1	0	0	1	1	0	1
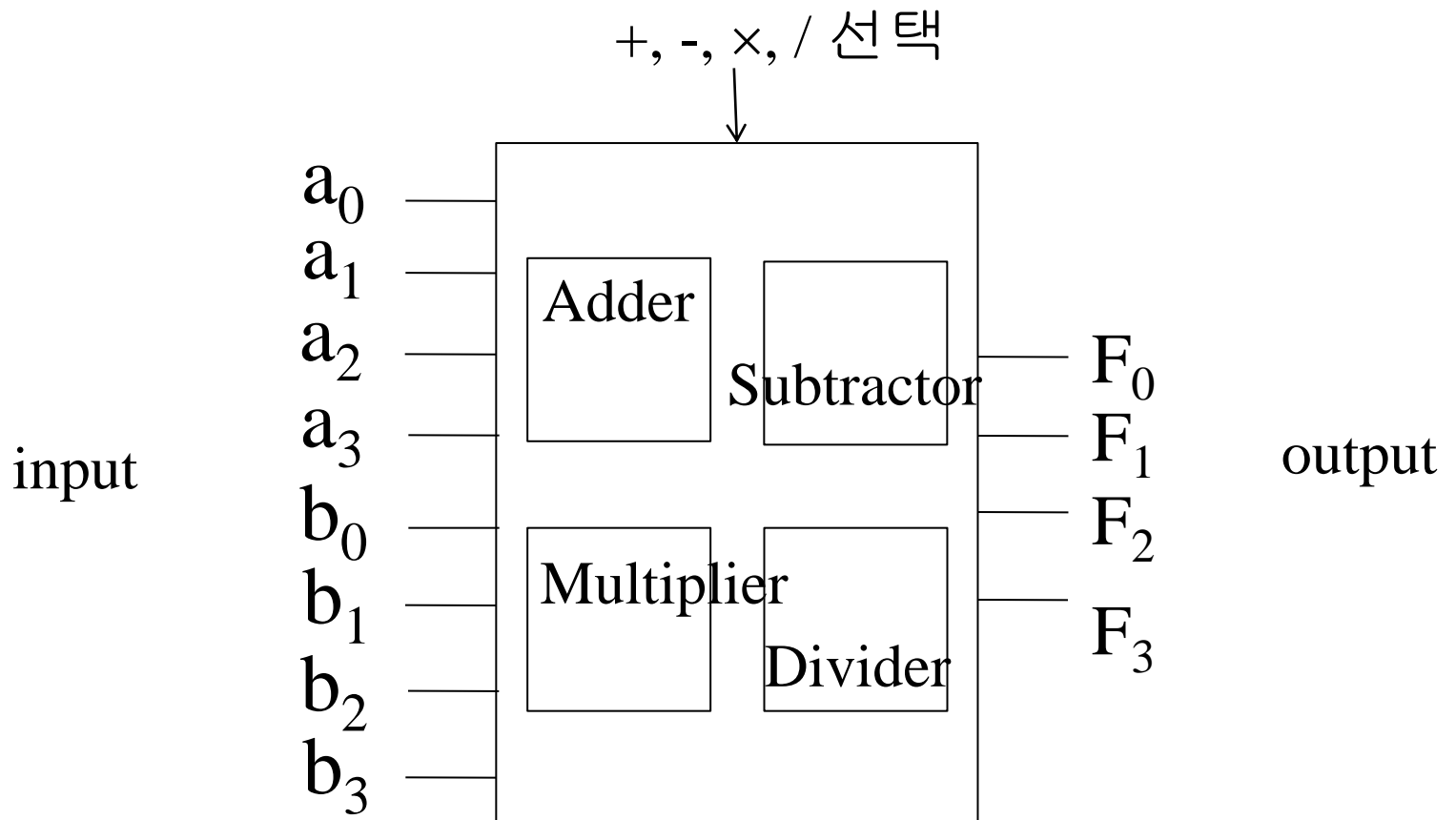
# Imagine ALU design without Abstraction

- ❑ What about 4-bit ALU?
- ❑ What about 32-bit ALU?



# Abstraction

## (Fundamental Engineering Concept)

How to deal with complexity

# Engineering: Building Abstractions

## ❑ Programmer

- Use machine instructions for programming
  - "Interface" (사용법)
- Not know computer design/organization/operation
  - "Implementation" (설계/구조/동작)

## ❑ Computer (CPU, SW) 를 포함한 모든 공학 도구/물건

- Implementation 몰라도 interface 알면 사용 가능
  - † Fundamental concept of abstraction

## ❑ Complex engineering product (예: SW, 자동차, 건물)

- 작은 부품들 사서 복잡한 모듈 만듬, 모듈들로 더 복잡한 ...
  - † Recursive abstraction building

# Add Binary Numbers


## ❑ Multiple 1-bit full adders

- Inputs: two bits to add, carry from right
- Output: carry to left

$$\begin{array}{r}
 \phantom{9_{10} = } 0001000 \\
 9_{10} = 00001001 \\
 12_{10} = 00001100 \\
 \hline
 00010101
 \end{array}
 \begin{array}{l}
 \leftarrow \leftarrow \\
 \text{carry} \\
 \\
 \\
 \\
 \\
 = 21_{10}
 \end{array}$$
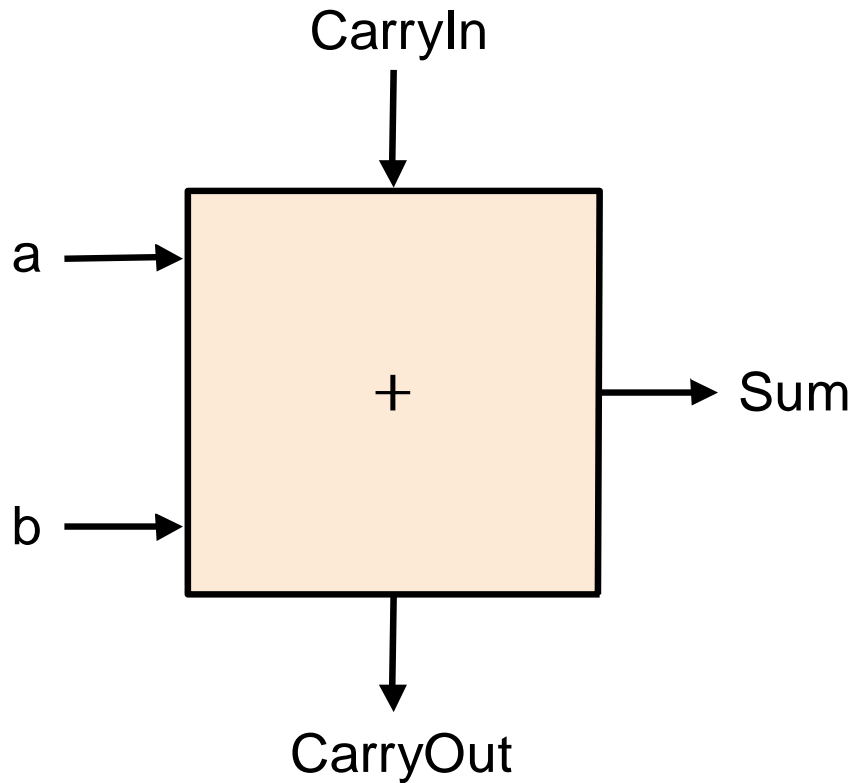
# 1-bit Full Adder Design

(Source: Computer Organization and Design, Hennessy and Patterson)





A	B	C <sub>in</sub>	S	C <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$C_{out} = a \cdot b + a \cdot C_{in} + b \cdot C_{in}$$
$$sum = a \text{ xor } b \text{ xor } C_{in}$$
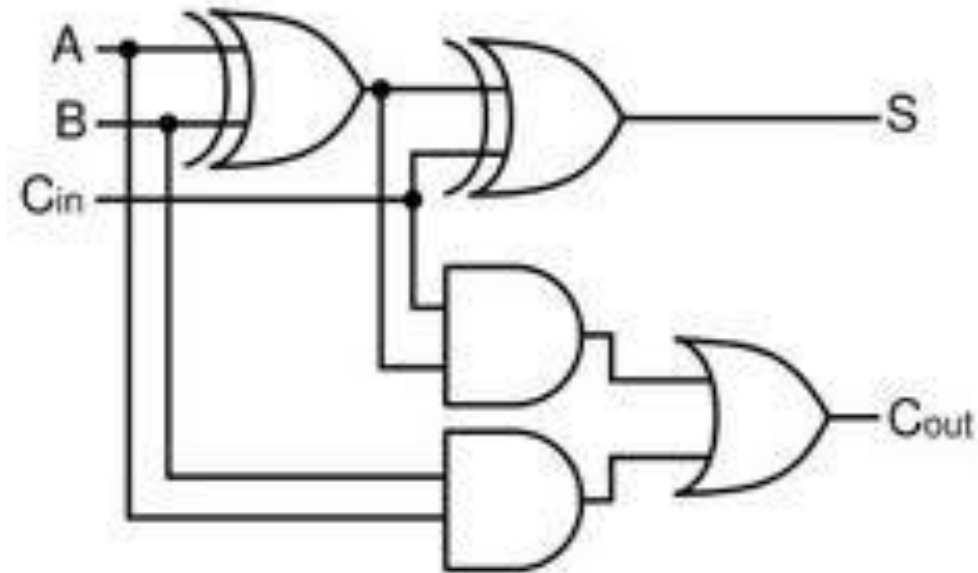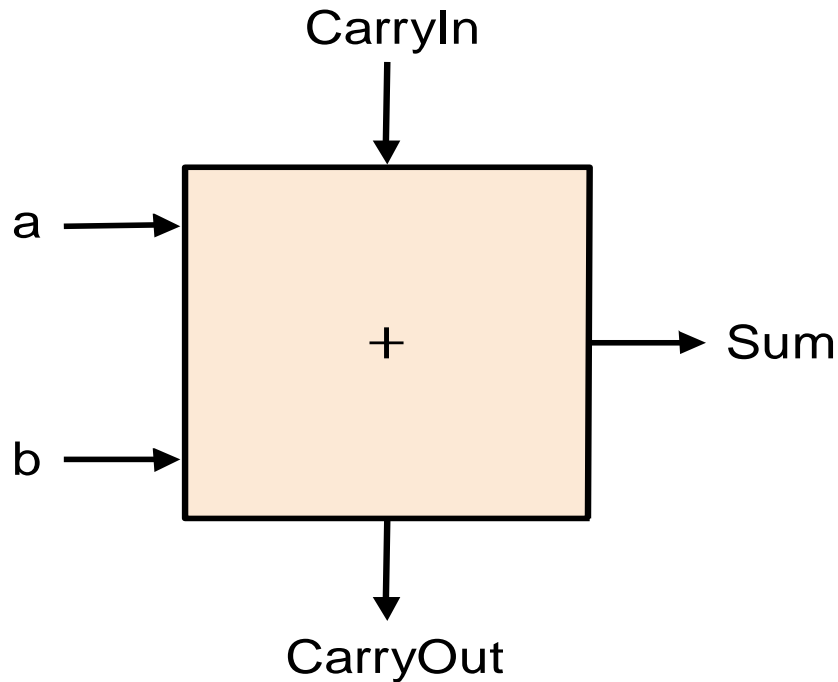
# 1-bit Full Adder Design

(Source: Computer Organization and Design, Hennessy and Patterson)




$$c_{out} = a \cdot b + a \cdot c_{in} + b \cdot c_{in}$$
$$sum = a \text{ xor } b \text{ xor } c_{in}$$

# XOR (Exclusive-OR) Gate

$$\square C = A \text{ XOR } B = A \oplus B$$

p	q	$p \oplus q$
1	1	0
1	0	1
0	1	1
0	0	0
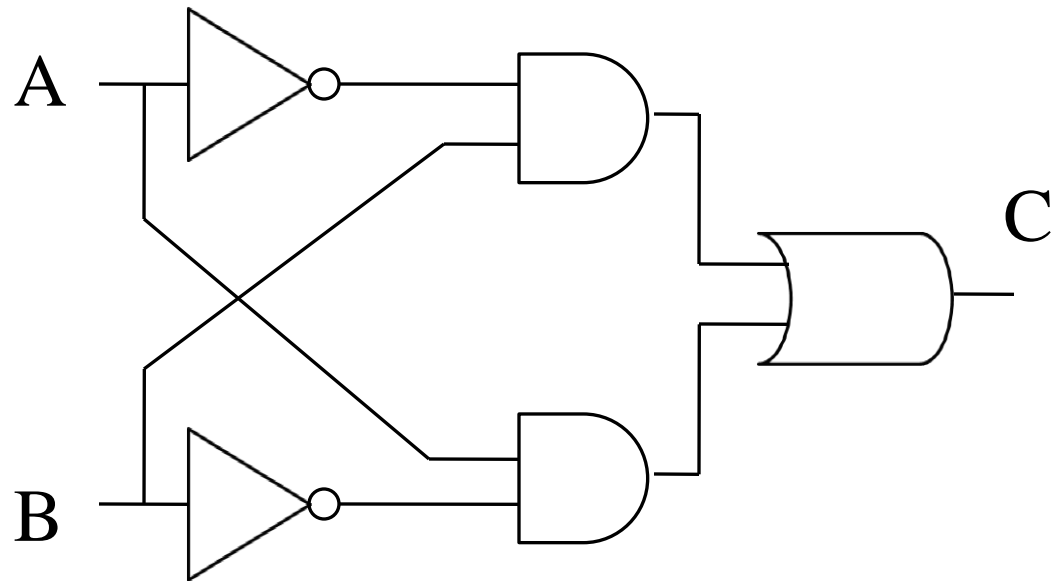
$$C = A \cdot \underline{B} + \underline{A} \cdot B$$







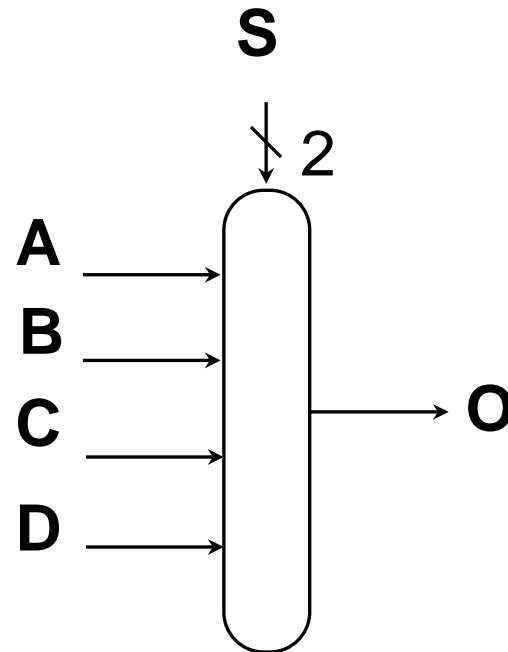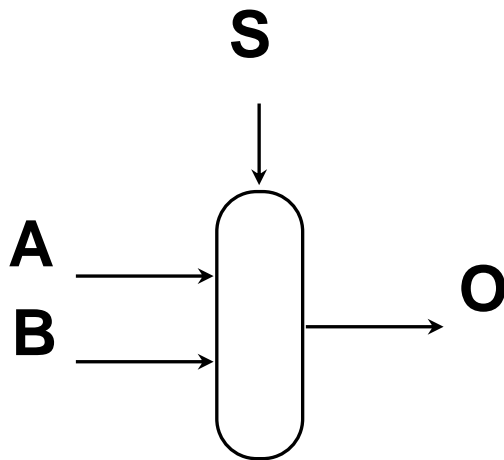
# Multiplexor (Data Selector)

(Source: Computer Organization and Design, Hennessy and Patterson)

- ❑ 2-to-1 MUX, 4-to-1 MUX (c.f., Demultiplexer)



# 4-to-1 Multiplexor (복합)

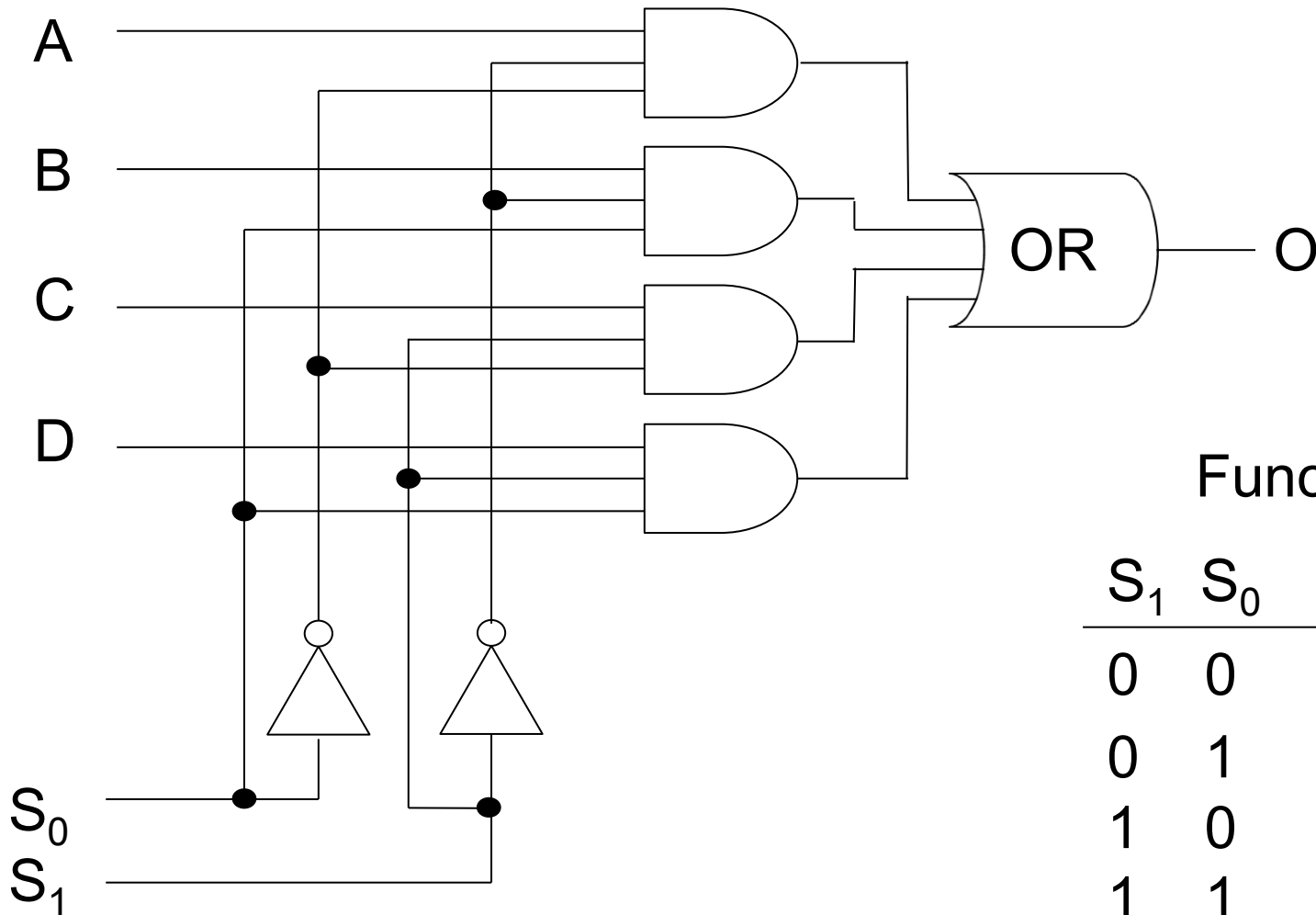


Function Table

$S_1$	$S_0$	O
0	0	A
0	1	B
1	0	C
1	1	D




# 1-bit ALU Design

(Source: Computer Organization and Design, Hennessy and Patterson)

□ 1-bit ADD, AND, OR

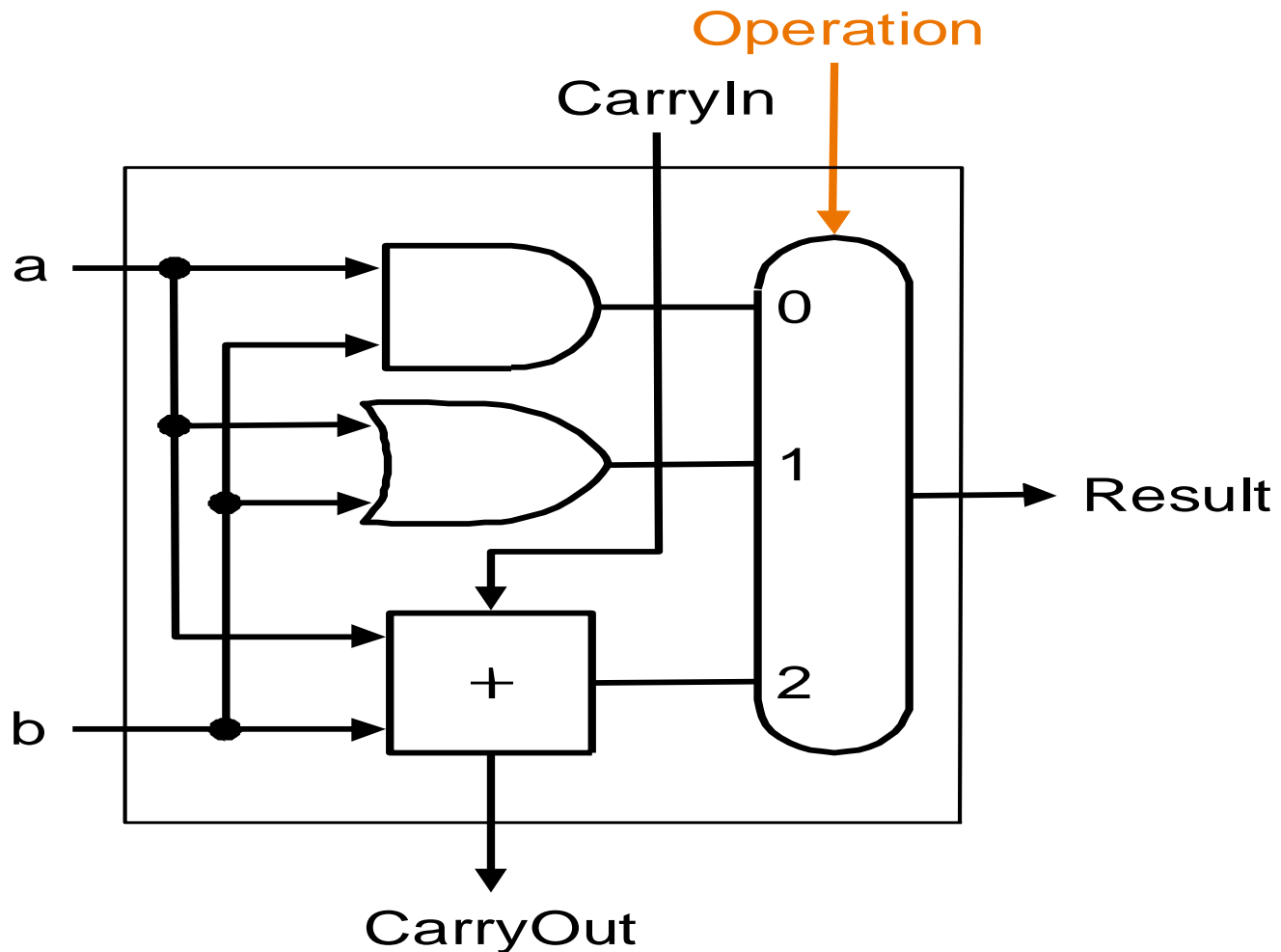
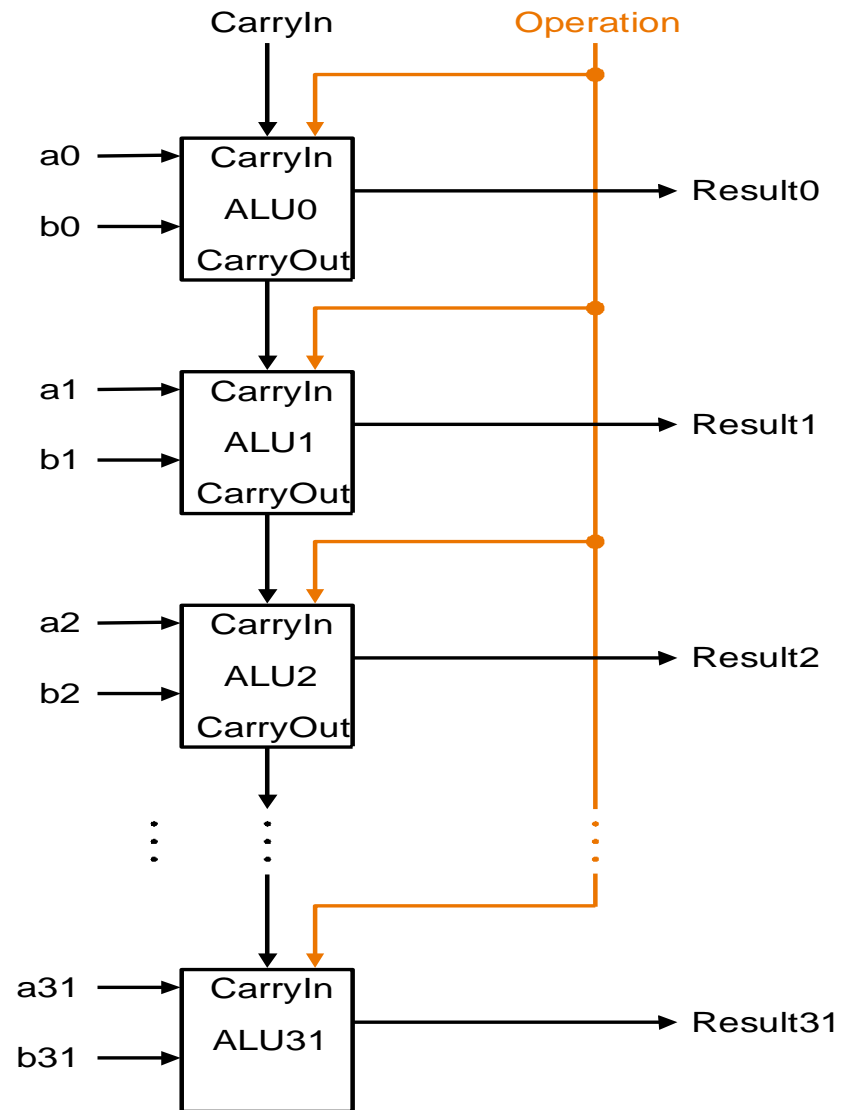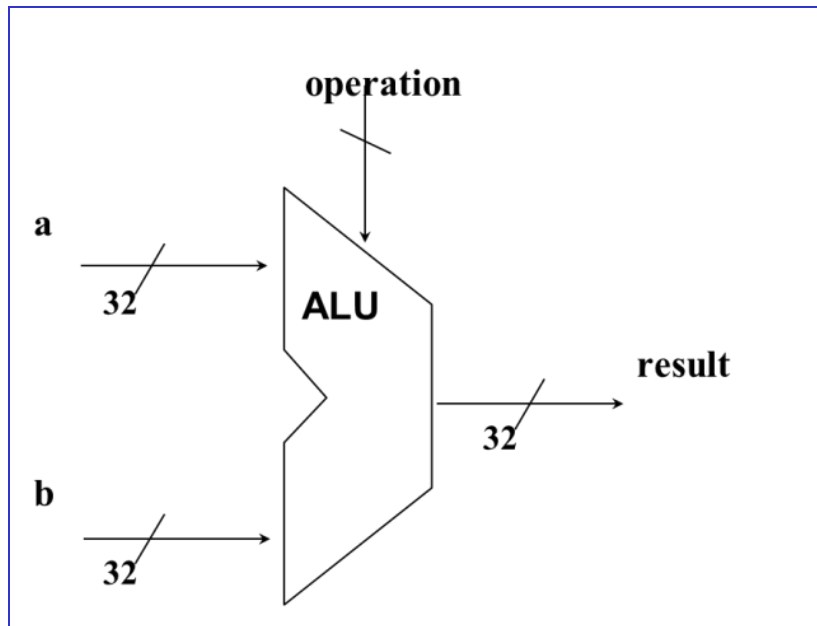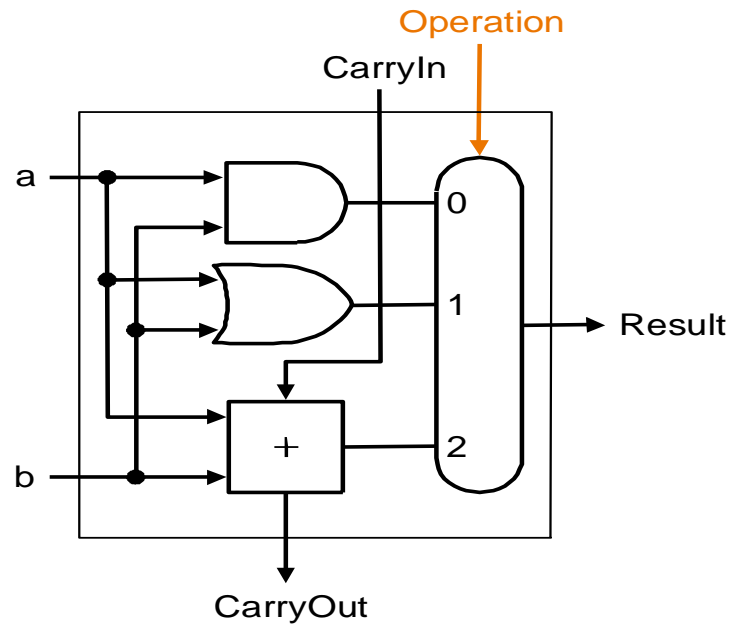
# 32-bit ALU Design (Source: Computer Organization and Design, Hennessy and Patterson)




# Primitive-Composition-Abstraction

- ❑ Fundamental paradigm in engineering
  - Primitives: AND, OR, NOT
  - Composition: build function unit (FU) using gates
  - Abstraction
    - Given its interface, can use FU
    - Functional unit (FU) become primitive
- ❑ What is hardware design
  - Hierarchically build (more and more complex) abstraction
    - † True in all engineering

# 32-bit ALU
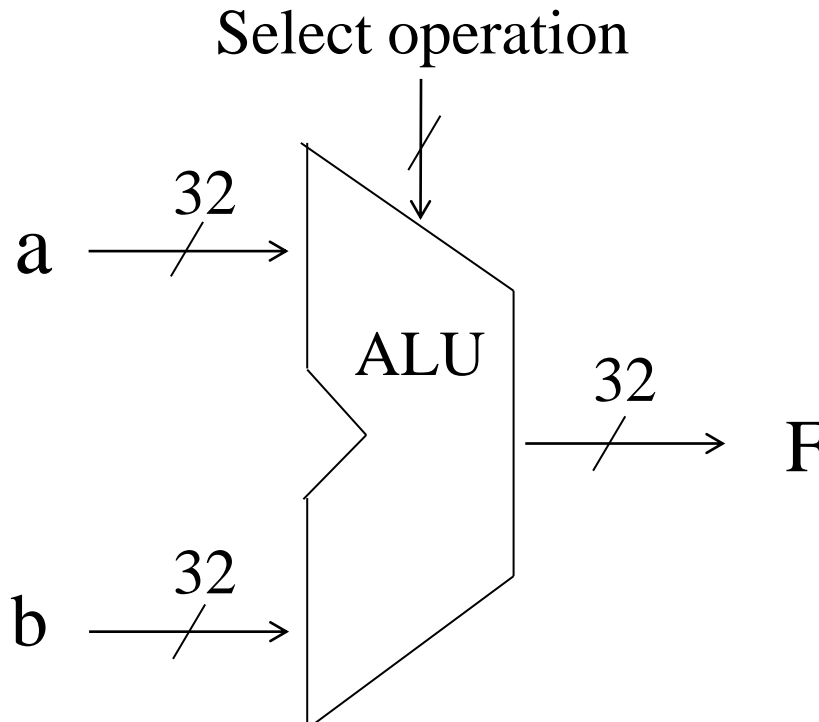
## □ Operations

- Arithmetic: add, subtract, multiply, divide
- Logical: bitwise AND, OR, NOT



# Logical Operations


## □ Bitwise AND, OR, NOT

AND	Output	0	1	0	0	1	0	0	0
	Input 1	0	1	1	0	1	0	1	0
	Input 2	0	1	0	1	1	0	0	0

OR	Output	0	1	1	1	1	0	1	0
	Input 1	0	1	1	0	1	0	1	0
	Input 2	0	1	0	1	1	0	0	0

NOT	Output	0	1	0	1	1	0	0	0
	Input	1	0	1	0	0	1	1	1

# Machine Called Computer

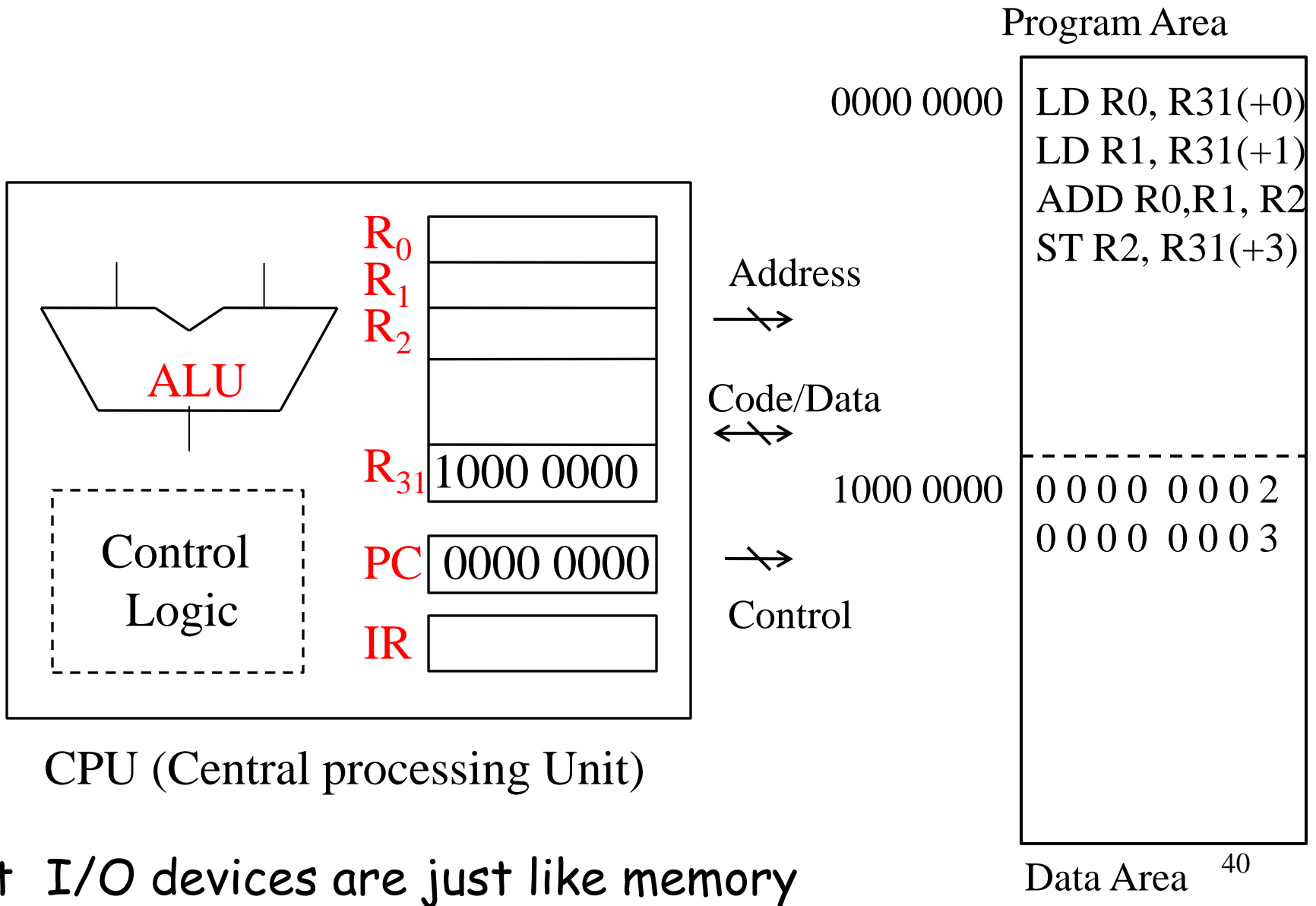



# Inside CPU

- ❑ ALU (arithmetic and logic unit)
  - Add, subtract, multiply, divide, AND, OR, NOT
  - Input: registers, output: register
- ❑ Registers
  - Storage of temporary data
- ❑ PC (program counter)
  - Address of the next instruction to execute
- ❑ IR (instruction register)
  - Instruction being executed
- ❑ Control logic
  - The rest of CPU for "fetch-decode-execute"


# Sequential Logic Design

- Storage (Registers and Memory)
- Notion of "Address"


(메모리: AND, OR, NOT 기반의 자동장치)
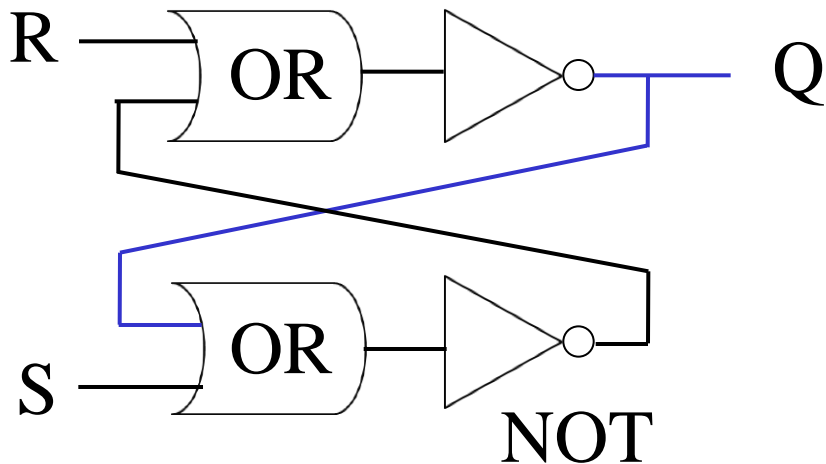
# SR Flip-Flop (구조나 동작을 암기할 필요 없음)

- Two stable states (invention of flip-flop in 1918)




S	R	Q	action
0	0	Q	hold
1	0	1	set
0	1	0	reset
1	1	not allowed	

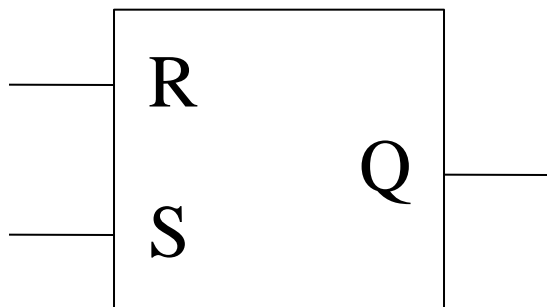


- Read Q with  $S=0, R=0$
- Write to Q
  - To store 1:  $S=1, R=0$
  - To store 0:  $S=0, R=1$

# 1-bit Storage

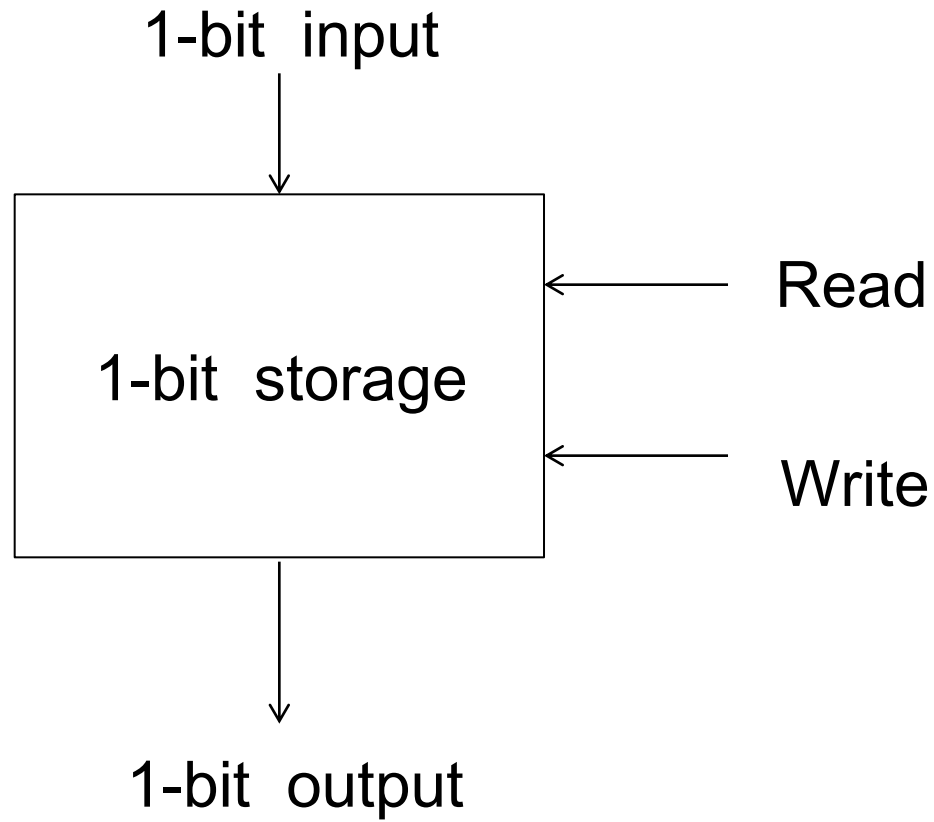
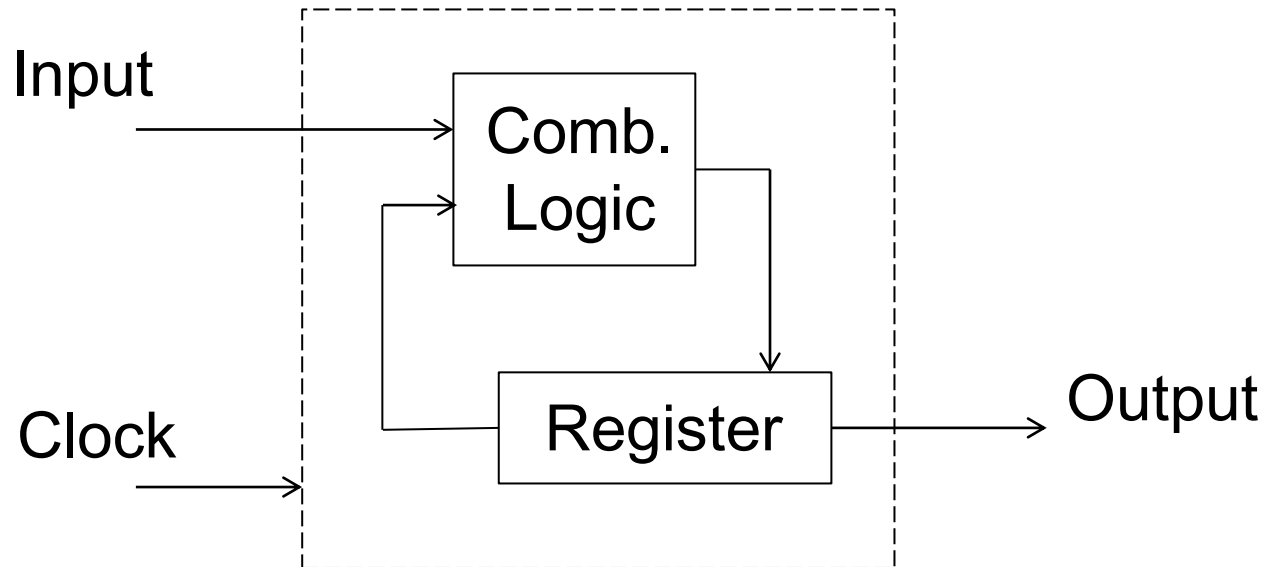
# Sequential Logic Design (복습)


- ❑ Registers (simplest ones)
- ❑ Binary counters



- † Sequential logic design more complex than comb. Logic
  - Truth table vs. state diagram
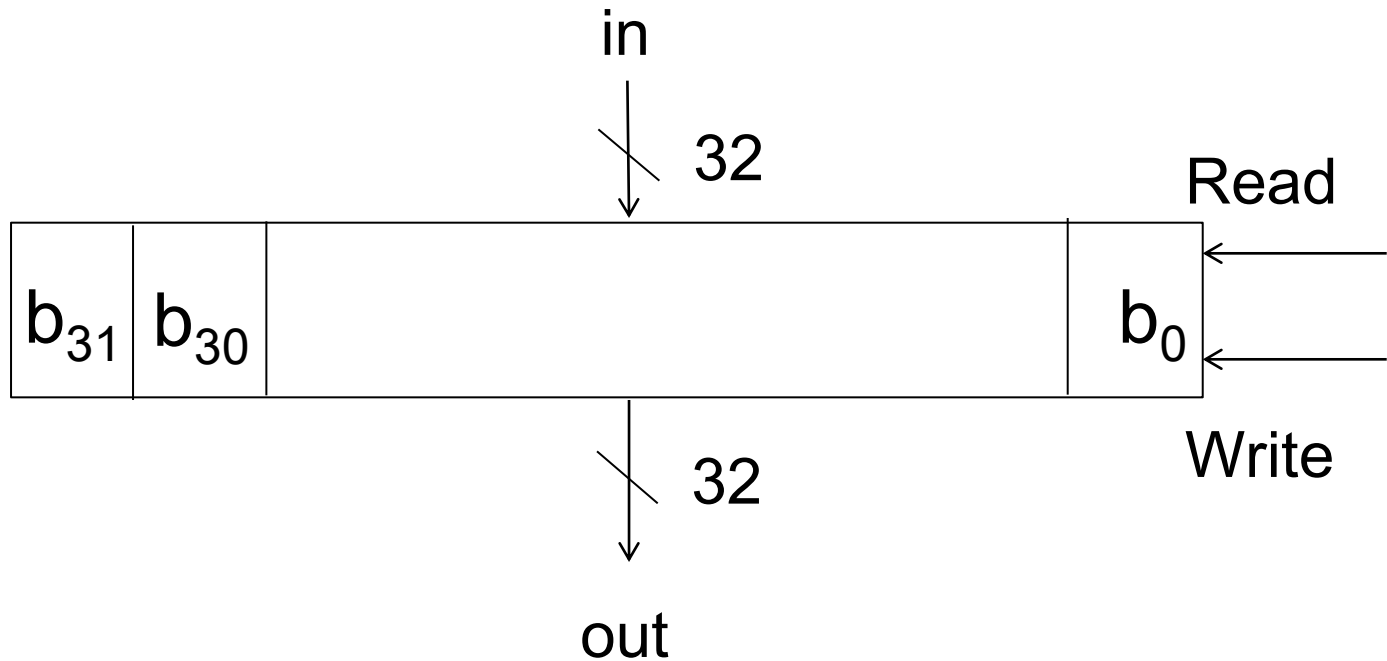
# 32-bit Storage


- Use 32 of 1-bit storages in parallel (share "address")



- Register: 32-bit storage in processor
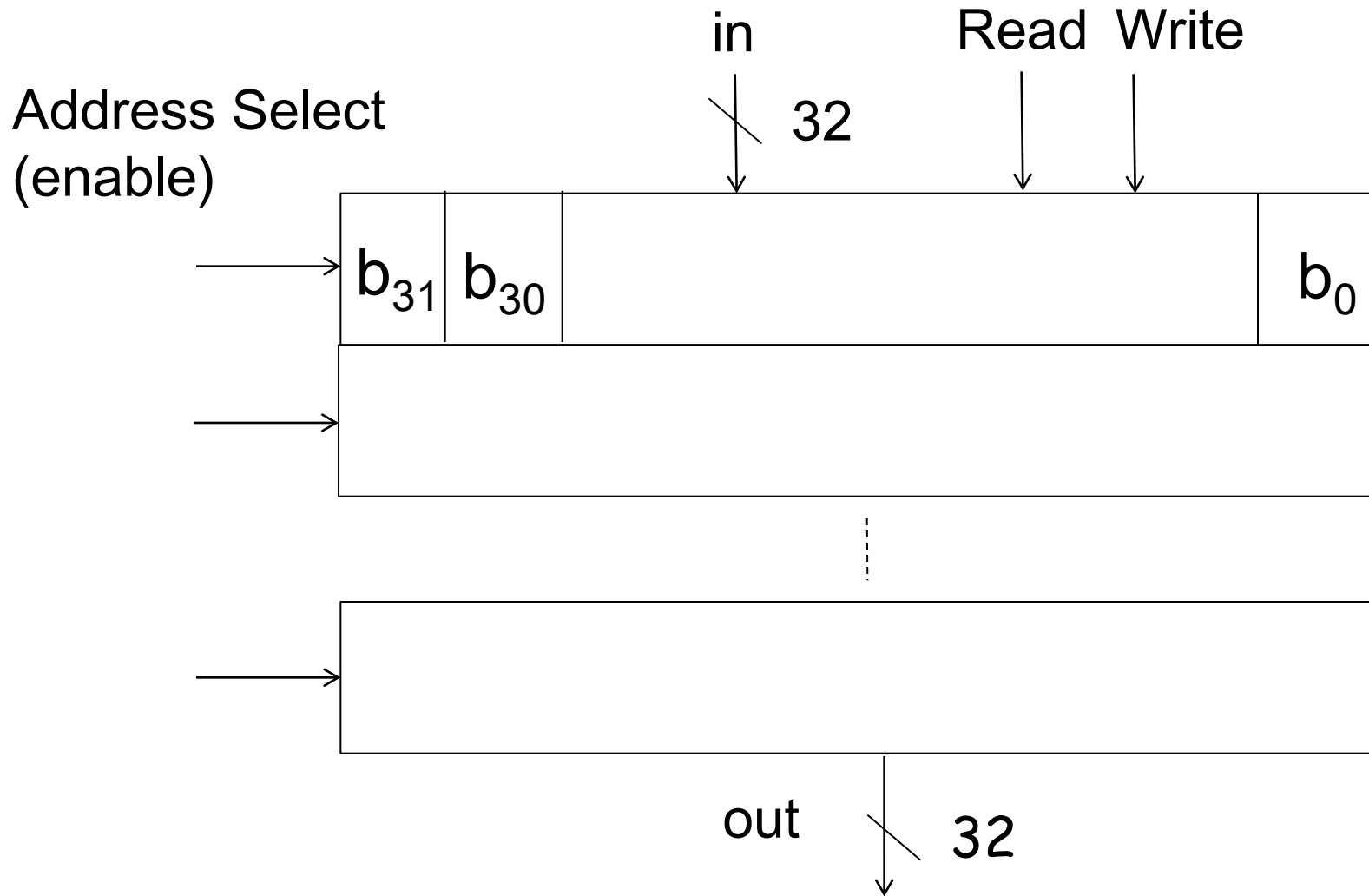
# Main Memory in 32-bit Computer

- ❑ Many locations - each has distinct address



# Meaning of Address

- ❑ Unique identifier for locations

Address from CPU

16 memory locations

0000

0001

1111






# Number of Address Bits

- ❑  $256 = 2^8$  memory locations: 8-bit address
- ❑  $64K = 2^{16}$  memory locations: 16-bit address
  - 8-bit microprocessor
- ❑  $4G = 2^{32}$  memory locations: 32-bit address
  - 32-bit processor

# 32-bit Computer

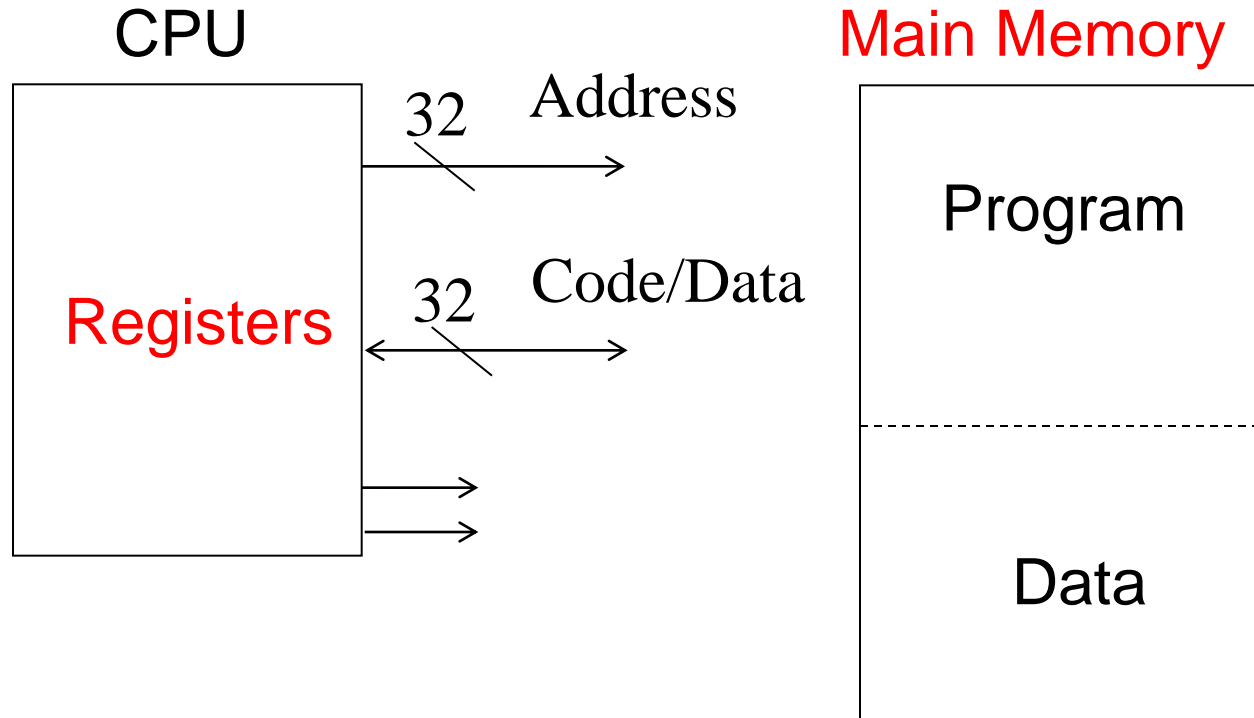

I/O device 0 (e.g., disk)

I/O device 1 (e.g., monitor)

- ❑  $4G = 2^{32}$  memory and I/O locations
- ❑ Given address, enable corresponding location

# Primitive-Composition-Abstraction

- ❑ Fundamental paradigm in engineering
  - Primitives: AND, OR, NOT
  - Composition: build function unit (FU) using gates
  - Abstraction
    - Given its interface, can use FU
    - Functional unit (FU) become primitive
- ❑ What is hardware design
  - Hierarchically build (more and more complex) abstraction
    - † True in all engineering

# Levels of Abstraction (참고자료)

(GEB by Hofstadter, AI by Winston)

---

Machine Instruction

---

Processor (Complex Functional Unit)

---

(hierarchical abstraction process)

---

Simple Functional Unit

---

Gates

---

Transistors



---

# Digital Logic Design (Combinational/Sequential Logic)

CPU, Memory  
(AND, OR, NOT 기반의 자동장치)  
(IF 개념은 곧 다시 나옴)

# Combinational and Sequential Circuits

(참고자료)

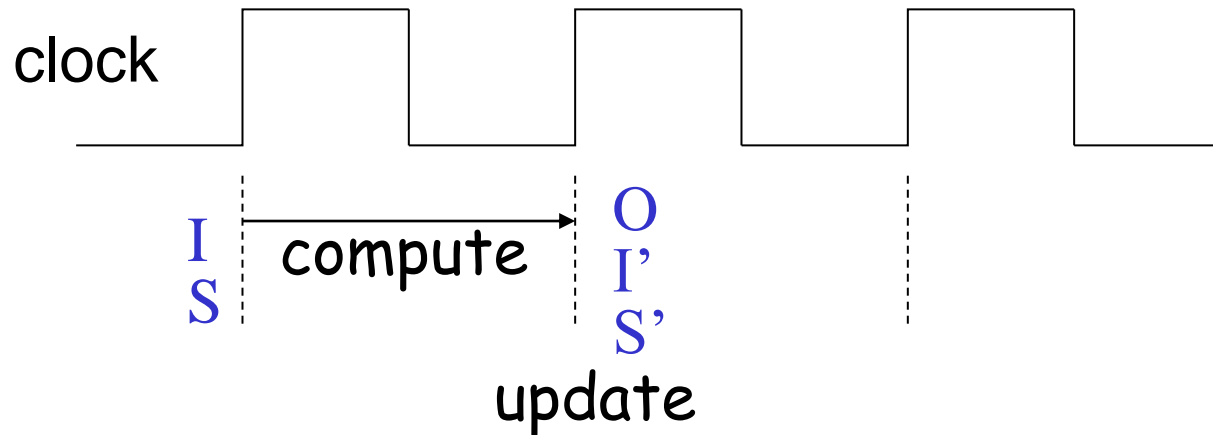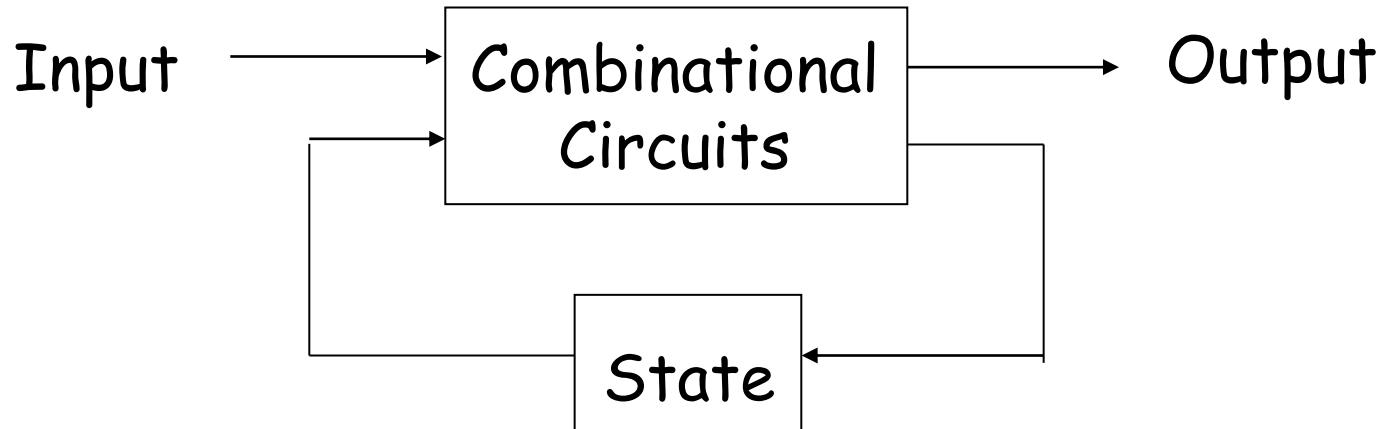

† Synchronous logic circuits

# Machine Called Computer

